

Digital Design

Lecture 7

Combinatorial Logic

Combinatorial Logic Circuit

- General Logic Block Without Memory
 - Outputs are only a function of the current inputs
 - No storage elements to remember “state”
 - There are timing delays from input to output due to gate delays

 


Fig. 4-1 Block Diagram of Combinational Circuit

Analysis Example

$$F_2 = AB + AC + BC$$

$$T_1 = A + B + C$$

$$T_2 = ABC$$

$$T_3 = F_2' T_1$$

$$F_1 = T_3 + T_2$$

Or

$$F_1 = A'BC' + A'B'C + AB'C' + ABC$$

 


Fig. 4-2 Logic Diagram for Analysis Example

Truth Table 4-1: Analysis Example

A	B	C	F_2	F_2'	T_1	T_2	T_3	F_1
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1

Truth Table 4-2: Code Conversion

Input BCD				Output Excess-3 Code			
A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

Code Conversion Karnaugh Maps

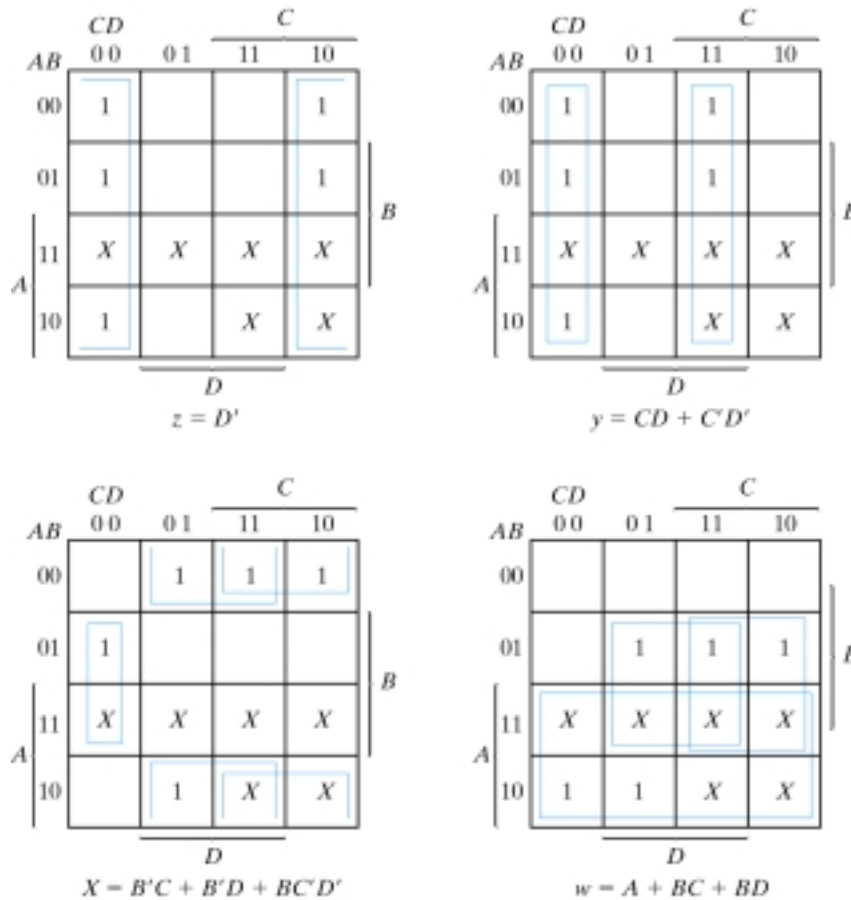


Fig. 4-3 Maps for BCD to Excess-3 Code Converter

BCD to Excess-3 Code Converter

$$z = D'$$

$$y = CD + C'D'$$
$$= CD + (C+D)'$$

$$x = B'C + BD' + BC'D'$$
$$= B'(C+D) + B(C+D)'$$

$$w = A + BC + BD$$
$$= A + B(C+D)$$


 



Fig. 4-4 Logic Diagram for BCD to Excess-3 Code Converter

Half Adder

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

$$S = x'y'z + x'yz' + xy'z' + xyz$$

 


$$S = xy + xz + yz$$


$$= xy + xy'z + x'yz$$

Fig. 4-6 Maps for Full Adder

Half Adder (cont.)

 

(a) $S = xy' + x'y$
 $C = xy$


 


(b) $S = x \oplus y$
 $C = xy$

Fig. 4-5 Implementation of Half-Adder

Full Adder

x	y	C	S
0	0	0	0
0	0	0	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	1	0
1	1	1	1

  

$$\begin{aligned}
 S &= xy + xz + yz \\
 &= xy + xy'z + x'yz
 \end{aligned}$$

Full Adder: Sum of Products

 


Fig. 4-7 Implementation of Full Adder in Sum of Products

Full Adder: Using Half Adders

 


Fig. 4-8 Implementation of Full Adder with Two Half Adders and an OR Gate

4-Bit Adder

 


Fig. 4-9 4-Bit Adder

Carry Propagation

- Carry bits must “ripple” through each stage of a multi-bit adder before the output settles down to the correct result
(two gate delays per bit)

 


Fig. 4-10 Full Adder with P and G Shown

Carry Look Ahead

 


Fig. 4-11 Logic Diagram of Carry Lookahead Generator

4-Bit Adder with Carry Look Ahead

 


Fig. 4-12 4-Bit Adder with Carry Lookahead

Binary Subtraction

$M = 1$ subtract

$V =$ overflow detect

 


Fig. 4-13 4-Bit Adder Subtractor

BCD Adder

- Carry 0110 when first adder result overflows

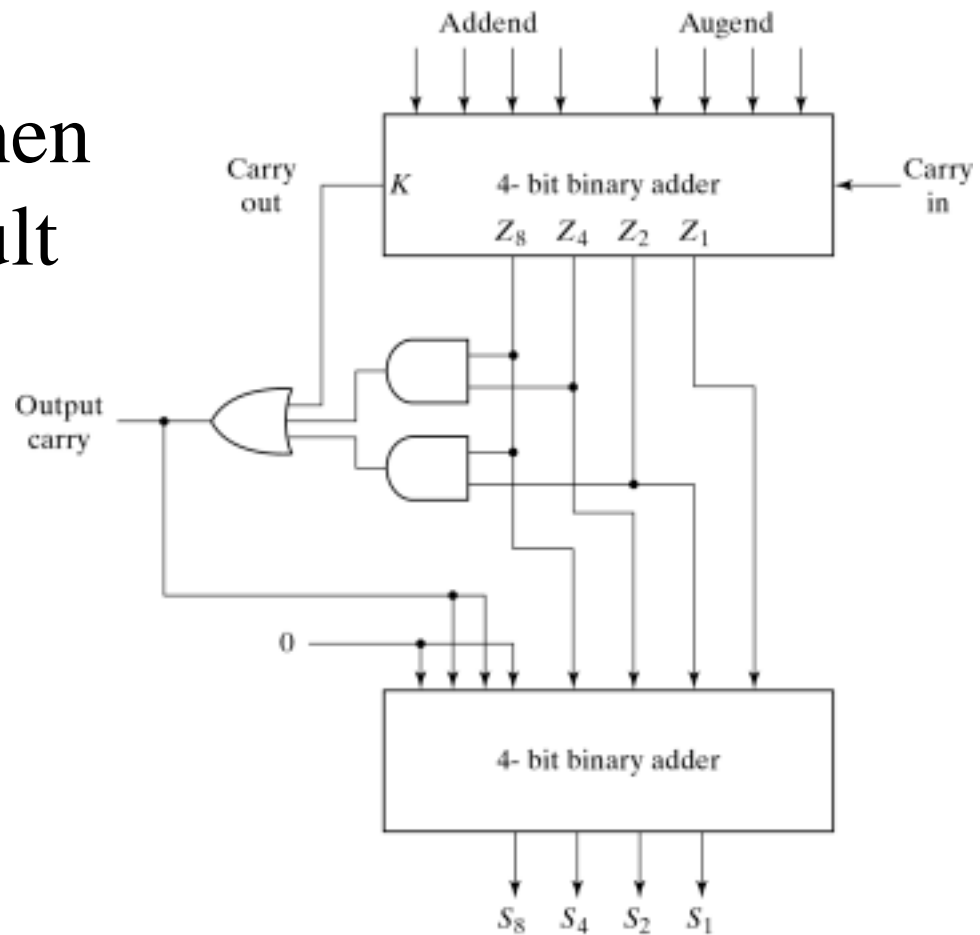


Fig. 4-14 Block Diagram of a BCD Adder