

Digital Circuit Design

Jeffrey N. Denenberg

Lecture #3

Boolean algebra
Combinational-circuit analysis

Boolean algebra

a.k.a. switching algebra

deals with Boolean values -- 0, 1

Positive-logic convention

analog voltages LOW, HIGH --> 0, 1

Negative logic -- seldom used

Signal values denoted by variables
(X, Y, FRED, etc.)

Boolean operators

Complement: X' (opposite of X)

AND: $X \cdot Y$

OR: $X + Y$

binary operators, described functionally by truth table.

X	Y	X AND Y	X	Y	X OR Y	X	NOT X
0	0	0	0	0	0	0	1
0	1	0	0	1	1	1	0
1	0	0	1	0	1		
1	1	1	1	1	1		

Huntington Postulates: 1-6 Ch. 2.2
Postulates and Theorems: Table 2-1

More definitions

Literal: a variable or its complement

$X, X', FRED', CS_L$

Expression: literals combined by
AND, OR, parentheses, complementation

$X+Y$

$P \cdot Q \cdot R$



$A + B \cdot C$

$((FRED \cdot Z') + CS_L \cdot A \cdot B' \cdot C + Q5) \cdot RESET'$

Equation: Variable = expression

$P = ((FRED \cdot Z') + CS_L \cdot A \cdot B' \cdot C + Q5) \cdot RESET'$

Logic symbols

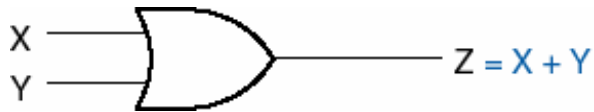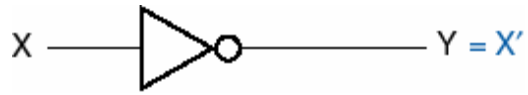

Theorems

(T1)	$X + 0 = X$	(T1')	$X \cdot 1 = X$	(Identities)
(T2)	$X + 1 = 1$	(T2')	$X \cdot 0 = 0$	(Null elements)
(T3)	$X + X = X$	(T3')	$X \cdot X = X$	(Idempotency)
(T4)	$(X')' = X$			(Involution)
(T5)	$X + X' = 1$	(T5')	$X \cdot X' = 0$	(Complements)

See Table 2-1

Proofs by perfect induction

More Theorems

<p>(T6) $X + Y = Y + X$</p> <p>(T7) $(X + Y) + Z = X + (Y + Z)$</p> <p>(T8) $X \cdot Y + X \cdot Z = X \cdot (Y + Z)$</p> <p>(T9) $X + X \cdot Y = X$</p> <p>(T10) $X \cdot Y + X \cdot Y' = X$</p> <p>(T11) $X \cdot Y + X' \cdot Z + Y \cdot Z = X \cdot Y + X' \cdot Z$</p> <p>(T11') $(X + Y) \cdot (X' + Z) \cdot (Y + Z) = (X + Y) \cdot (X' + Z)$</p>	<p>(T6') $X \cdot Y = Y \cdot X$ (Commutativity)</p> <p>(T7') $(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$ (Associativity)</p> <p>(T8') $(X + Y) \cdot (X + Z) = X + Y \cdot Z$ (Distributivity)</p> <p>(T9') $X \cdot (X + Y) = X$ (Covering)</p> <p>(T10') $(X + Y) \cdot (X + Y') = X$ (Combining)</p> <p>(Consensus)</p>
---	--

Again Table 2-1

Duality

Swap 0 & 1, AND & OR

Result: Theorems still true

Why?

Each axiom (A1-A5) has a dual (A1'-A5')

Counterexample:

<p>$X + X \cdot Y = X$ (T9)</p> <p>$X \cdot X + Y = X$ (dual)</p> <p>$X + Y = X$ (T3')</p> <p>???????????????</p>	<p>$X + (X \cdot Y) = X$ (T9)</p> <p>$X \cdot (X + Y) = X$ (dual)</p> <p>$(X \cdot X) + (X \cdot Y) = X$ (T8)</p> <p>$X + (X \cdot Y) = X$ (T3')</p> <p>parentheses, operator precedence!</p>
--	---


N-variable Theorems

(T12)	$X + X + \dots + X = X$	(Generalized idempotency)
(T12')	$X \cdot X \cdot \dots \cdot X = X$	
(T13)	$(X_1 \cdot X_2 \cdot \dots \cdot X_n)' = X_1' + X_2' + \dots + X_n'$	(DeMorgan's theorems)
(T13')	$(X_1 + X_2 + \dots + X_n)' = X_1' \cdot X_2' \cdot \dots \cdot X_n'$	
(T14)	$[F(X_1, X_2, \dots, X_n, \cdot, \cdot)]' = F(X_1', X_2', \dots, X_n', \cdot, \cdot)$	(Generalized DeMorgan's theorem)
(T15)	$F(X_1, X_2, \dots, X_n) = X_1 \cdot F(1, X_2, \dots, X_n) + X_1' \cdot F(0, X_2, \dots, X_n)$	(Shannon's expansion theorems)
(T15')	$F(X_1, X_2, \dots, X_n) = [X_1 + F(0, X_2, \dots, X_n)] \cdot [X_1' + F(1, X_2, \dots, X_n)]$	


Prove using finite induction

Most important: DeMorgan theorems

DeMorgan Symbol Equivalence

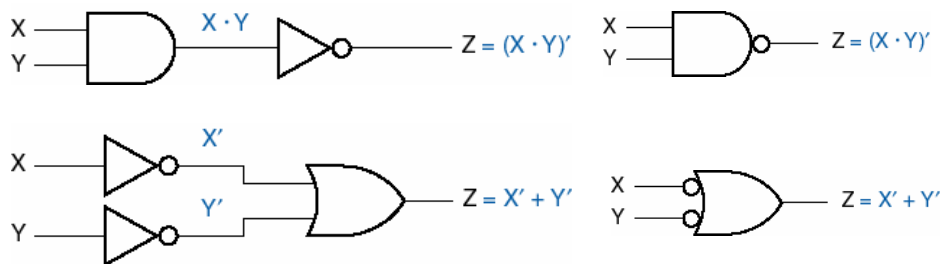


Likewise for OR

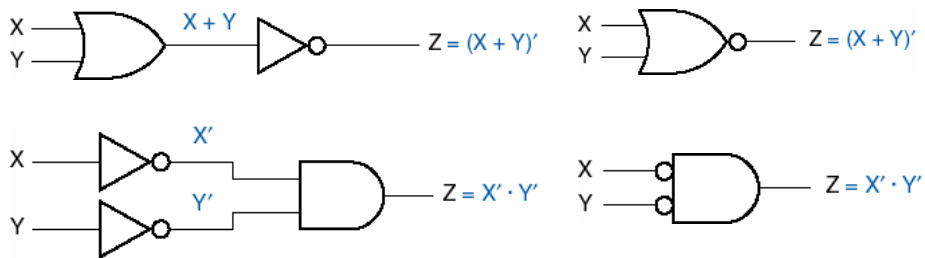

(be sure to check errata!)

DeMorgan Symbols

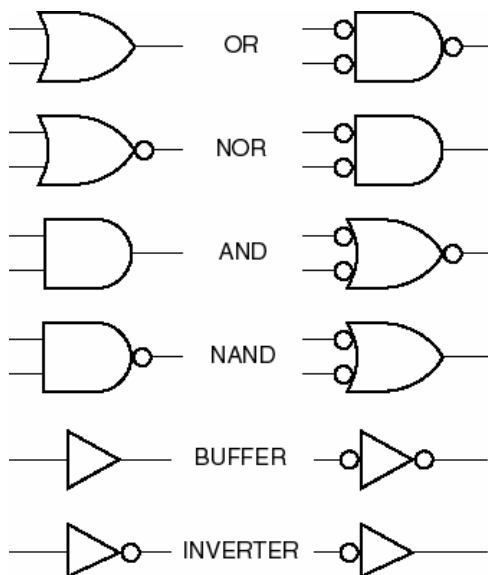

Even more definitions (Sec. 4.1.6)

Product term

Sum-of-products expression

Sum term

Product-of-sums expression

Normal term

Minterm (n variables)


Maxterm (n variables)

Truth table vs. minterms & maxterms


<i>Row</i>	X	Y	Z	F	<i>Minterm</i>	<i>Maxterm</i>
0	0	0	0	F(0,0,0)	$X' \cdot Y' \cdot Z'$	$X + Y + Z$
1	0	0	1	F(0,0,1)	$X' \cdot Y' \cdot Z$	$X + Y + Z'$
2	0	1	0	F(0,1,0)	$X' \cdot Y \cdot Z'$	$X + Y' + Z$
3	0	1	1	F(0,1,1)	$X' \cdot Y \cdot Z$	$X + Y' + Z'$
4	1	0	0	F(1,0,0)	$X \cdot Y' \cdot Z'$	$X' + Y + Z$
5	1	0	1	F(1,0,1)	$X \cdot Y' \cdot Z$	$X' + Y + Z'$
6	1	1	0	F(1,1,0)	$X \cdot Y \cdot Z'$	$X' + Y' + Z$
7	1	1	1	F(1,1,1)	$X \cdot Y \cdot Z$	$X' + Y' + Z'$

Table 2-3

Combinational analysis

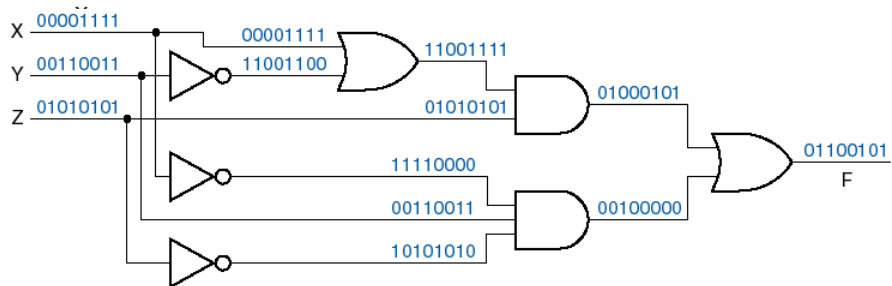


Signal expressions

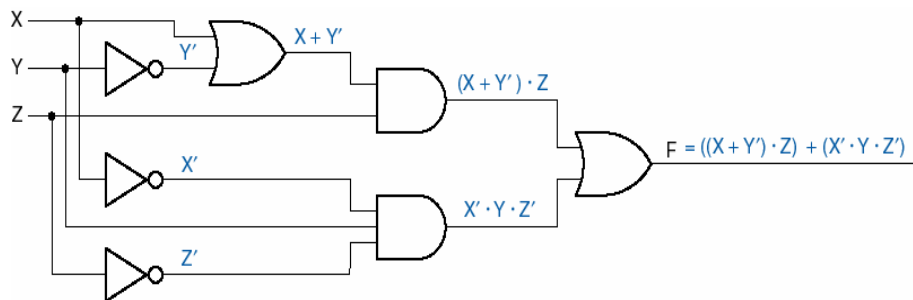

Multiply out:

$$\begin{aligned}
 F &= ((X + Y') \cdot Z) + (X' \cdot Y \cdot Z') \\
 &= (X \cdot Z) + (Y' \cdot Z) + (X' \cdot Y \cdot Z')
 \end{aligned}$$

New circuit, same function

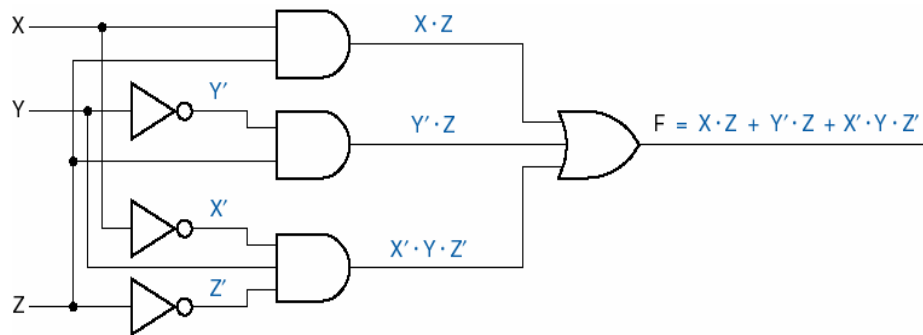

J. N. Denenberg


Boolean - Combinational Logic

17

Add out logic function

$$\begin{aligned}
 F &= ((X+Y') \cdot Z) + (X' \cdot Y \cdot Z') \\
 &= (X+Y'+X') \cdot (X+Y'+Y) \cdot (X+Y'+Z) \cdot (Z+X') \cdot (Z+Y) \cdot (Z+Z') \\
 &= 1 \cdot 1 \cdot (X+Y'+Z) \cdot (X'+Z) \cdot (Y+Z) \cdot 1 \\
 &= (X+Y'+Z) \cdot (X'+Z) \cdot (Y+Z)
 \end{aligned}$$

Circuit:

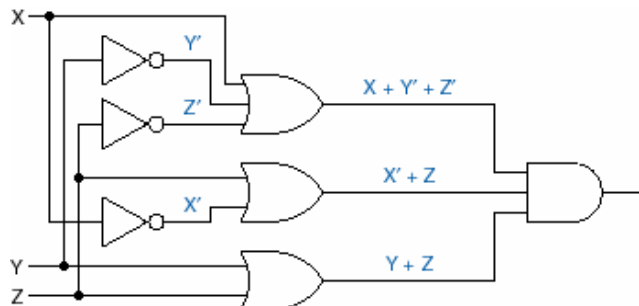


J. N. Denenberg


Boolean - Combinational Logic

18

Shortcut: Symbol substitution



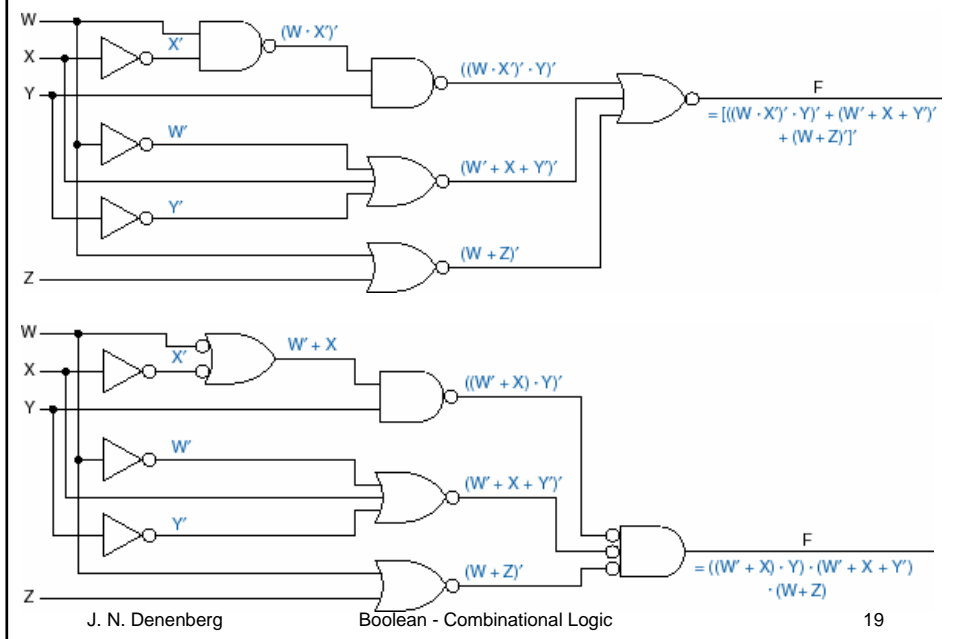


Different circuit, same function

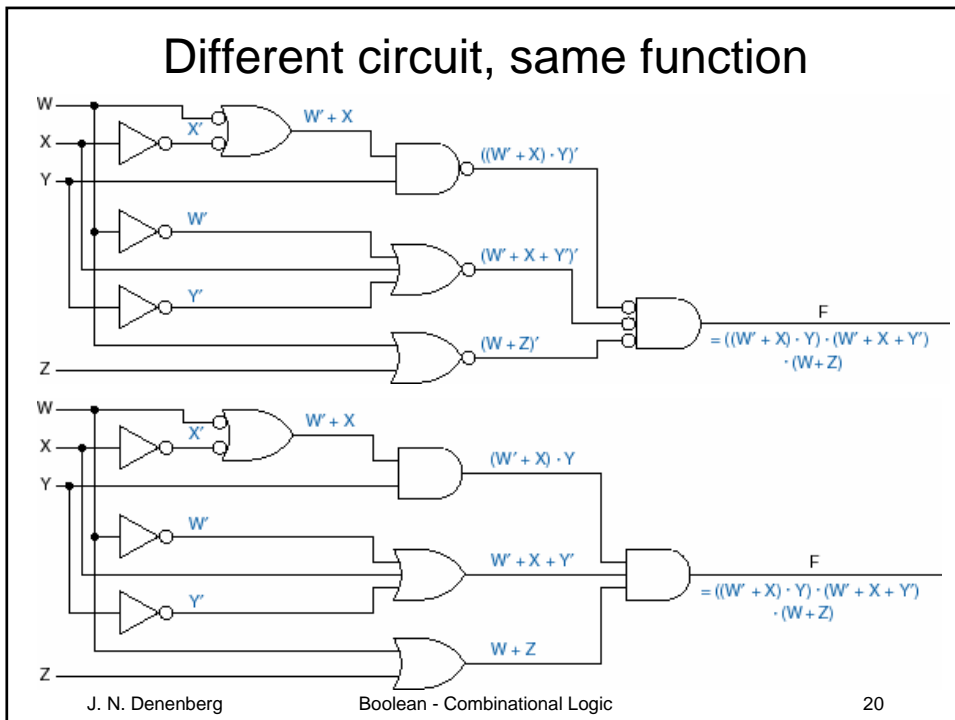

Another example
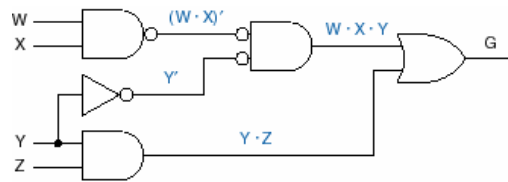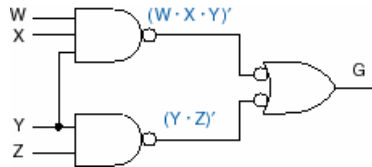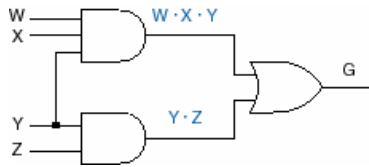
$$G(W, X, Y, Z) = W \cdot X \cdot Y + Y \cdot Z$$



This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.