

EG 32

Digital Electronics

Thought for the day

You learn from your mistakes.....

**So make as many as you can and you
will eventually know everything**

Digital Electronics

Analog signal: Signal is constantly changing levels


Digital signal: Signal is either present (1) or not (0)

Computers



Communications

Music

Why Digital?

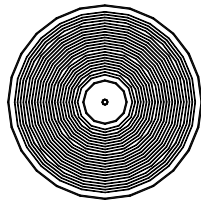

Phonograph
Record
(1/2 mile of grooves)

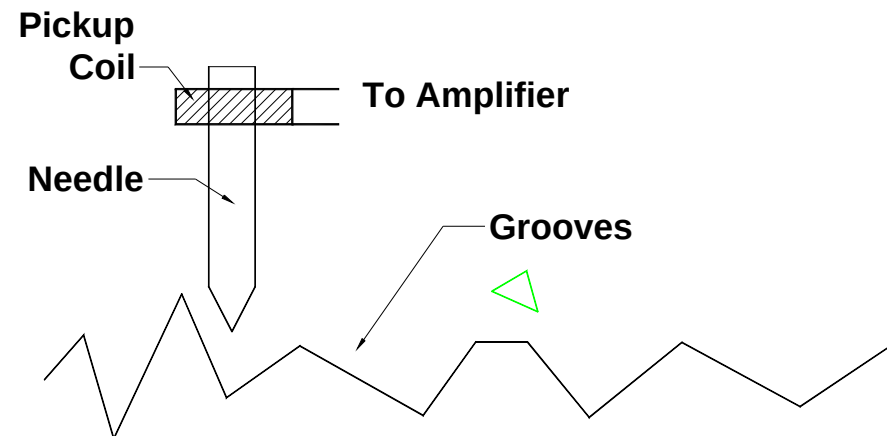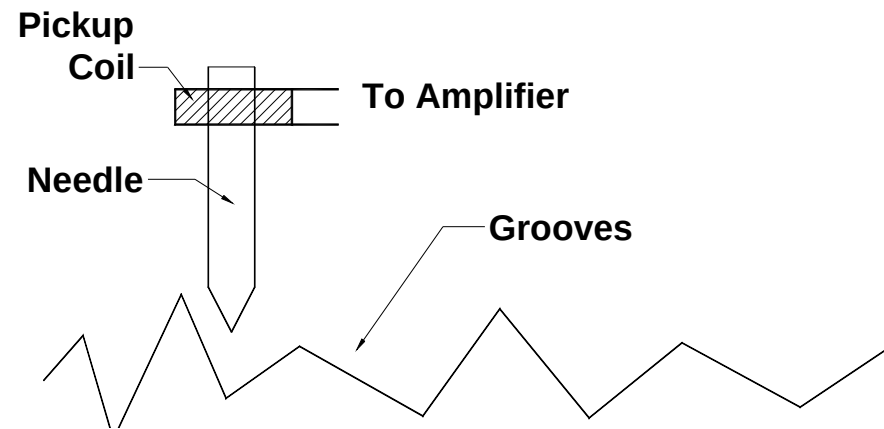

Why Digital?

- Noise:** Clarity of signal
- Storage:** Real time storage
- Programmable:** Processing is easier
- Precision:** Not dependent on component values
- Circuit Density:** Much higher than analog



Basic Binary Arithmetic

Decimal system	-	Base 10
Binary system	-	Base 2
Octal system	-	Base 8
Hexadecimal System	-	Base 16

Decimal system:

$$2745.214 = 2 \times 10^3 + 7 \times 10^2 + 4 \times 10^1 + 5 \times 10^0 + 2 \times 10^{-1} + 1 \times 10^{-2} + 4 \times 10^{-3}$$

Binary system:

$$\begin{aligned} 1011.101 &= 1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 1 \times 2^0 + 1 \times 2^{-1} + 0 \times 2^{-2} + 1 \times 2^{-3} \\ &= 8 + 0 + 2 + 1 + 0.5 + 0 + 0.125 \\ &= 11.625_{10} \end{aligned}$$

Each of the binary numbers is called a “bit”

Adding binary numbers

1 0 1 0

$$1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 0 \times 2^0 = 10$$

0 1 1 1


$$0 \times 2^3 + 1 \times 2^2 + 1 \times 2^1 + 1 \times 2^0 = 7$$

1 0 0 0 1




16


Representation of Binary Signals

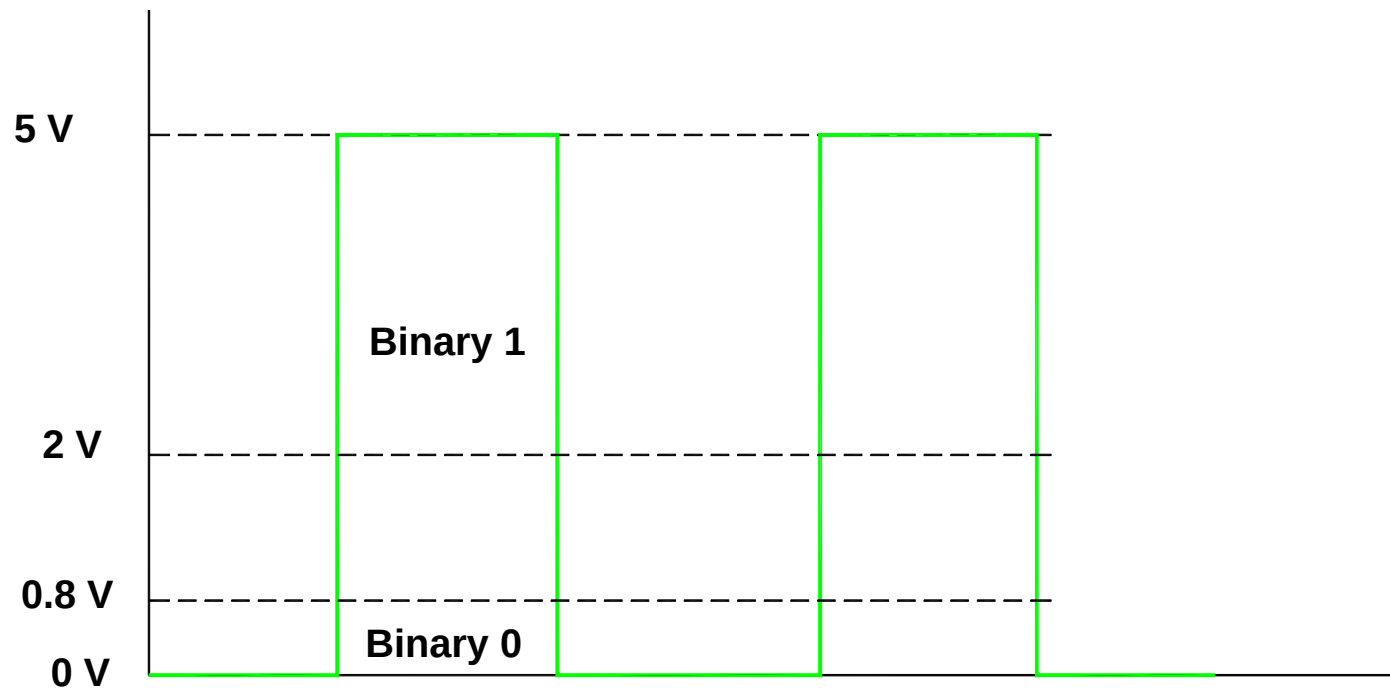

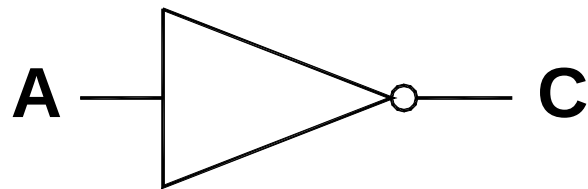
**All Logic Circuits can be
realized with just three basic
building blocks**



Inverter

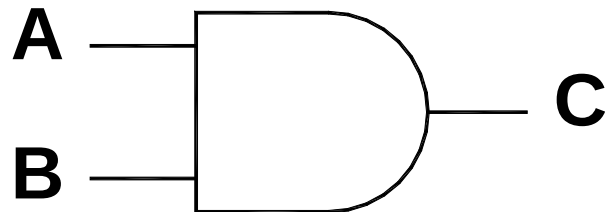

And Gate

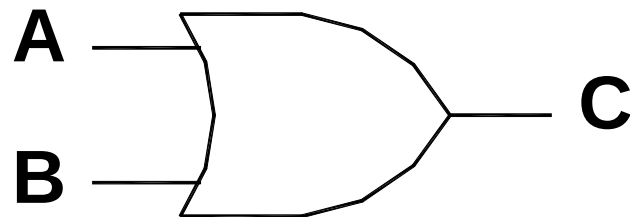


Or Gate

Truth Table

A table that lists all possible outputs for all possible inputs

AND Gate

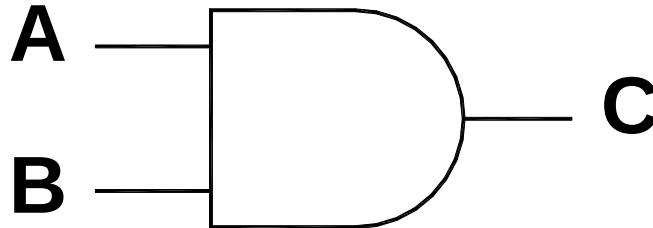

2ⁿ possible
combinations



A	B	C
0	0	0
1	0	0
0	1	0
1	1	1

Boolean expression:


$$C = A \bullet B$$

“AB”

Operation of AND Gate

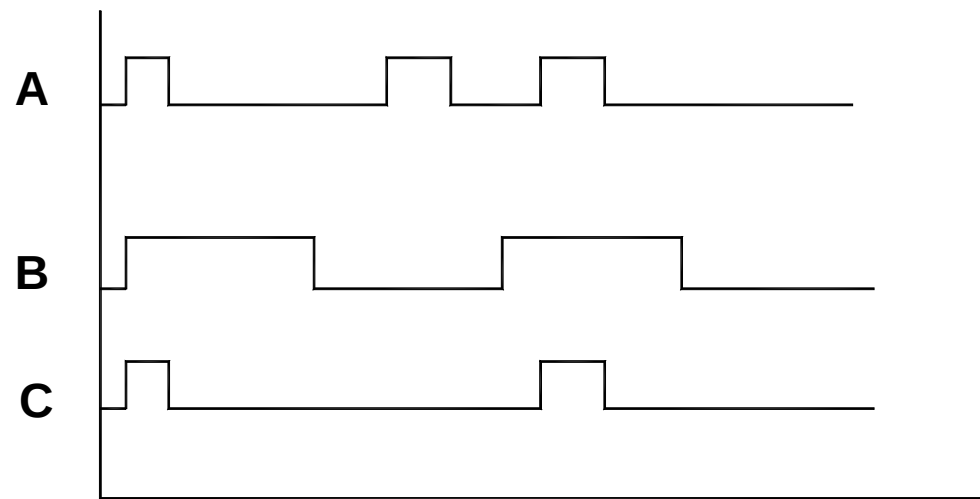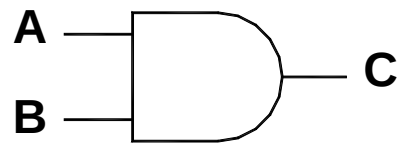

OR Gate

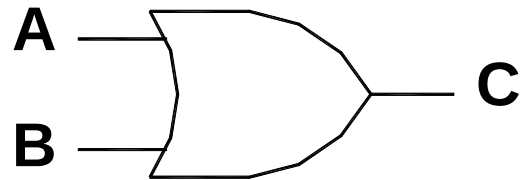


A	B	C
0	0	0
1	0	1
0	1	1
1	1	1

Boolean expression:

$$\mathbf{C = A + B}$$

Inverter
(“Not”)


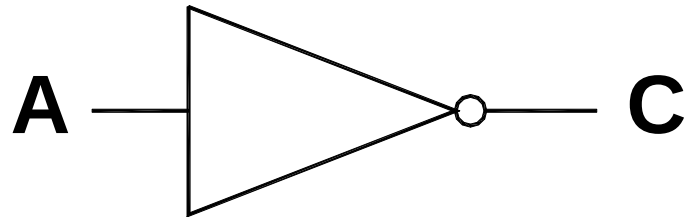


A	C
0	1
1	0

Boolean expression:

$$C = \bar{A}$$

NAND Gate

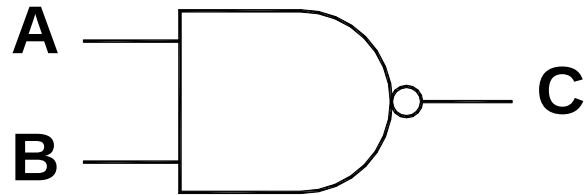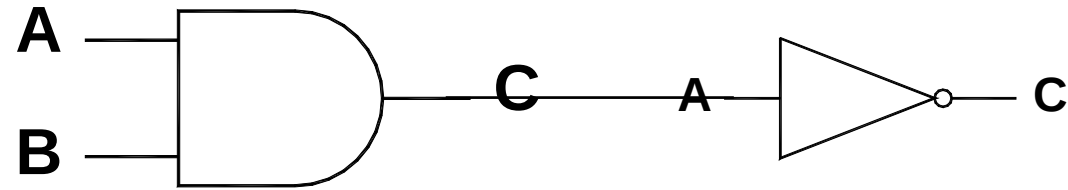



A	B	C
0	0	1
1	0	1
0	1	1
1	1	0

Boolean expression:

$$C = \overline{A \cdot B}$$

$$C = \overline{AB}$$


NOR Gate

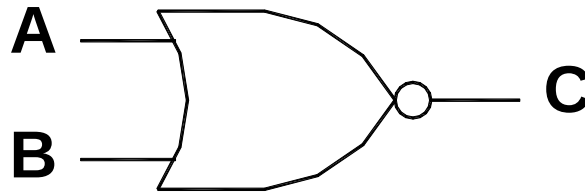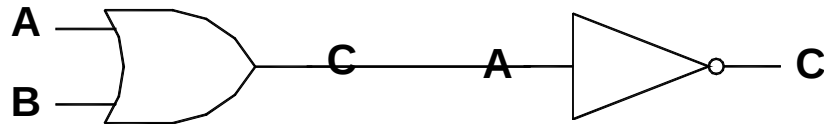

A	B	C
0	0	1
1	0	0
0	1	0
1	1	0

Boolean expression:

$$C = \overline{A + B}$$

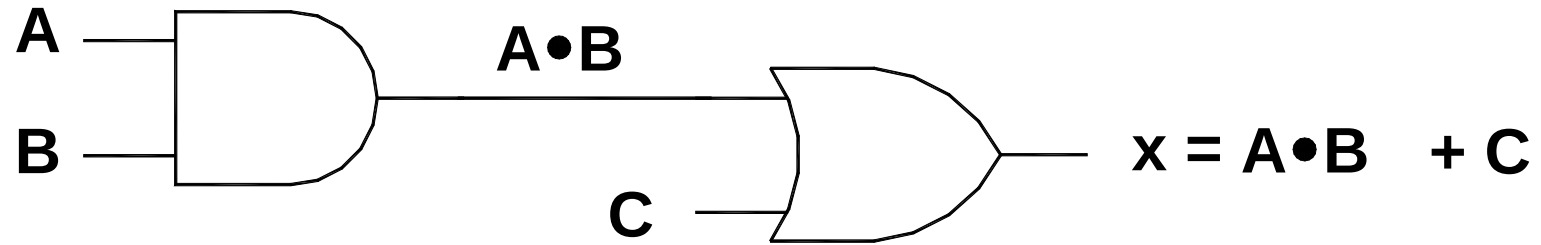


A	B	$A \bullet B$	C	$X = A \bullet B + C$
0	0	0	0	0
0	1	0	0	0
1	0	0	0	0
1	1	1	0	1
0	0	0	1	1
0	1	0	1	1
1	0	0	1	1
1	1	1	1	1

To go the other way:

Suppose we want to implement:

$$Y = AC + B\bar{C} + \bar{A}BC$$

Need a three-input OR Gate

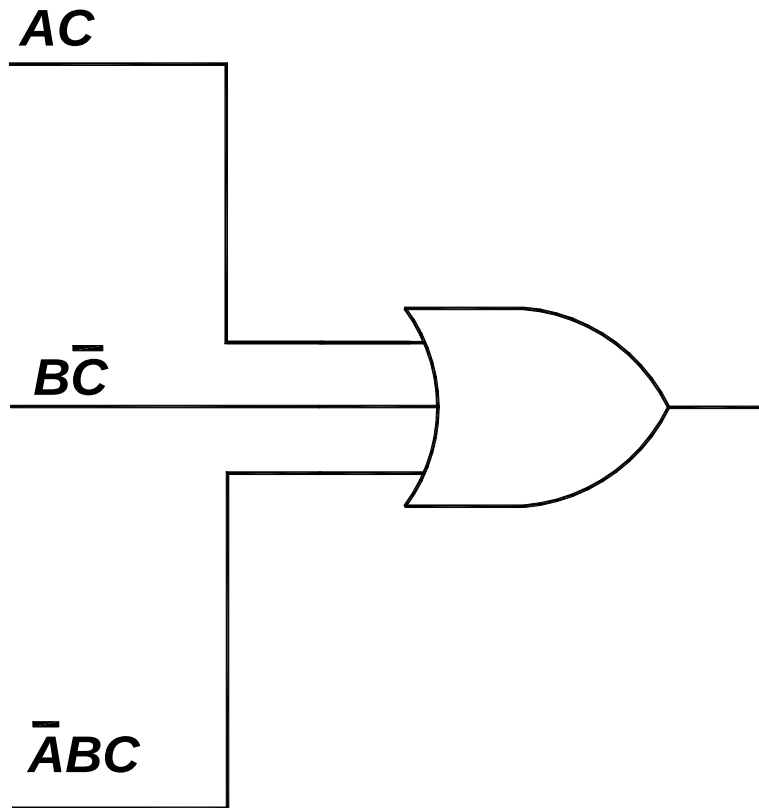


$$Y = AC + B\bar{C} + \bar{A}BC$$

Need two two-input AND Gates

Need one three-input AND Gate


Need two inverters

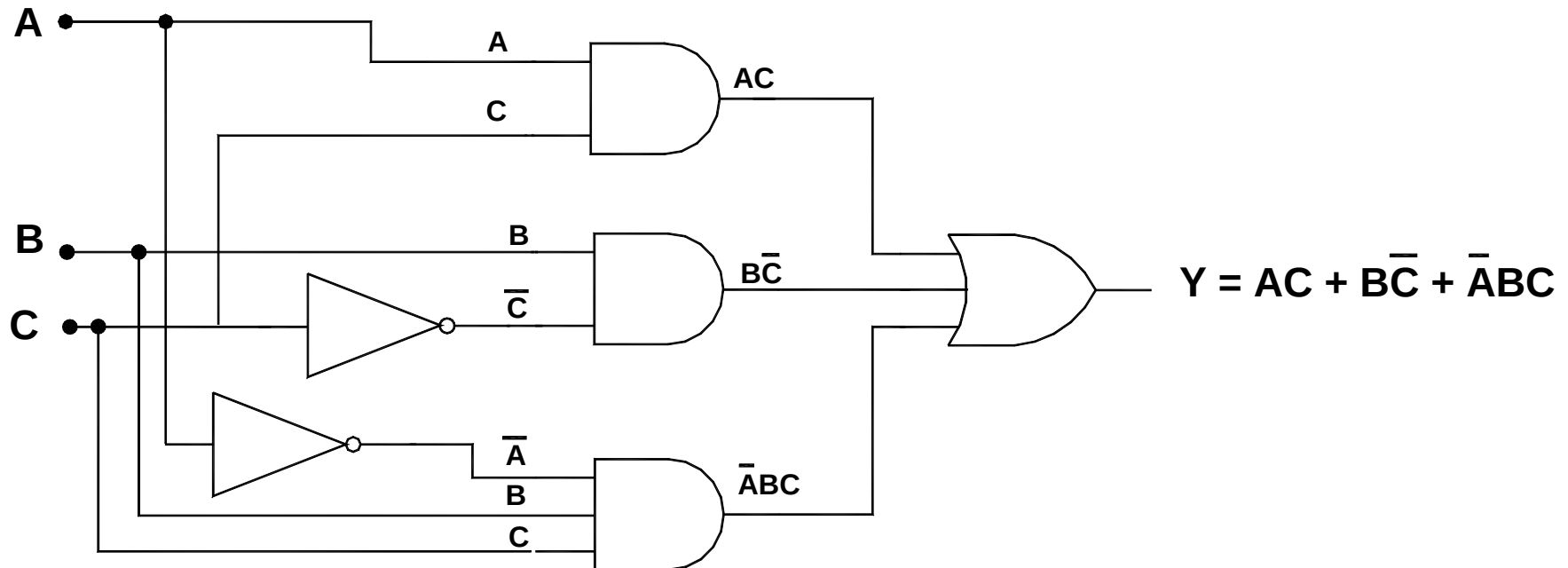

A	B	C	AC	$\bar{B}C$	$\bar{A}BC$	Y
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	1	0	1
0	1	1	0	0	1	1
1	0	0	0	0	0	0
1	0	1	1	0	0	1
1	1	0	0	1	0	1
1	1	1	1	0	0	1

Exclusive OR (XOR) Gate

XOR Gate

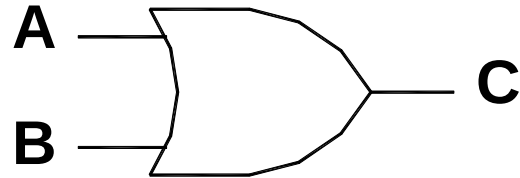

A	B	C
0	0	0
1	0	1
0	1	1
1	1	0

Boolean expression:

$$C = A + B$$

The XOR gate can be used to make a circuit that adds two one - bit binary numbers

0 + 0 = 0 no carry

1 + 0 = 1 no carry

1 + 1 = 0 1 carry

Adding binary numbers

1 0 1 0

$$1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 0 \times 2^0 = 10$$

0 1 1 1

$$0 \times 2^3 + 1 \times 2^2 + 1 \times 2^1 + 1 \times 2^0 = 7$$

1 0 0 0 1

Boolean Algebra Theorems

Single variable

$$x \bullet 0 = 0$$

$$x \bullet 1 = x$$

$$x \bullet x = x$$

$$x \bullet \overline{x} = 0$$

$$x + 0 = x$$

$$x + 1 = 1$$

$$x + x = x$$

$$x + \overline{x} = 1$$

Multiple variables

$$x + y = y + x$$

$$x \bullet y = y \bullet x$$

$$x + (y + z) = (x + y) + z = x + y + z$$

$$x(yz) = (xy)z = xyz$$

$$x(y + z) = xy + xz$$

$$(w + x)(y + z) = wy + xy + wz + xz$$

$$x + xy = x$$

$$x + \overline{x}y = x + y$$

Example:

Simplify

$$Y = A\bar{B}D + A\bar{B}\bar{D}$$

Factor out $A\bar{B}$

$$Y = A\bar{B}(D + \bar{D})$$

$$D + \bar{D} = 1$$

$$Y = A\bar{B}D + A\bar{B}\bar{D} = A\bar{B}$$

DeMorgan's Theorems

$$\overline{(x + y)} = \overline{x} \bullet \overline{y}$$

$$\overline{(x \bullet y)} = \overline{x} + \overline{y}$$

Example: Simplify

$$z = \overline{\overline{(A + C)} + \overline{(B + D)}}$$

$$z = (\overline{\overline{A}} \bullet \overline{\overline{C}}) + (\overline{\overline{B}} \bullet \overline{\overline{D}})$$

$$\overline{\overline{A}} = A, \quad \overline{\overline{D}} = D$$

$$z = A\overline{C} + \overline{B}D$$

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.