



Alexander-Sadiku

Fundamentals of Electric Circuits

Chapter 1

Basic Concepts

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

1



Basic Concepts - Chapter 1

- 1.1 Systems of Units.
- 1.2 Electric Charge.
- 1.3 Current.
- 1.4 Voltage.
- 1.5 Power and Energy.
- 1.6 Circuit Elements.

2

1.1 System of Units (1)

Six basic units

Quantity	Basic unit	Symbol
Length	meter	m
Mass	kilogram	Kg
Time	second	s
Electric current	ampere	A
Thermodynamic temperature	kelvin	K
Luminous intensity	candela	cd

3

1.1 System of Units (2)

The derived units commonly used in electric circuit theory

Quantity	Unit	Symbol
electric charge	coulomb	C
electric potential	volt	V
resistance	ohm	Ω
conductance	siemens	S
inductance	henry	H
capacitance	farad	F
frequency	hertz	Hz
force	newton	N
energy, work	joule	J
power	watt	W
magnetic flux	weber	Wb
magnetic flux density	tesla	T

Factor	Prefix	Symbol
10^9	giga	G
10^6	mega	M
10^3	kilo	k
10^{-2}	centi	c
10^{-3}	milli	m
10^{-6}	micro	μ
10^{-9}	nano	n
10^{-12}	pico	p

Decimal multiples and submultiples of SI units

4



1.2 Electric Charges

Charge is an electrical property of the atomic particles of which matter consists, measured in **coulombs (C)**.

The charge **e** on one electron is negative and equal in magnitude to **1.602×10^{-19} C** which is called as electronic charge. The charges that occur in nature are **integral multiples** of the electronic charge.

5



1.3 Current (1)

Electric current **$i = dq/dt$** . The unit of ampere can be derived as **$1 \text{ A} = 1 \text{ C/s}$** .


A **direct current (dc)** is a current that remains constant with time.

An **alternating current (ac)** is a current that varies sinusoidally with time.
(reverse direction)

6

1.3 Current (2)

The direction of current flow

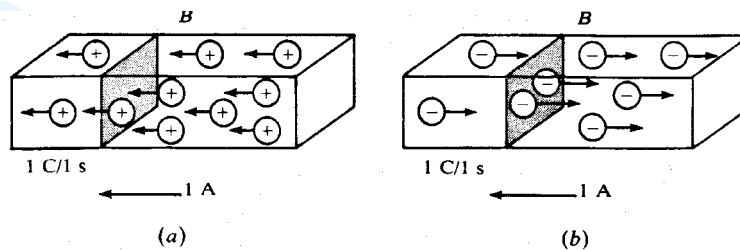

Positive ions

Negative ions

7

1.3 Current (3)

Example 1

A conductor has a constant current of 5 A.

How many electrons pass a fixed point on the conductor in one minute?

8

1.3 Current (4)

Solution

Total no. of charges pass in 1 min is given by
 $5 \text{ A} = (5 \text{ C/s})(60 \text{ s/min}) = 300 \text{ C/min}$

Total no. of electronics pass in 1 min is given

$$\frac{300 \text{ C/min}}{1.602 \times 10^{-19} \text{ C/electron}} = 1.87 \times 10^{21} \text{ electrons/min}$$

9

1.4 Voltage (1)

Voltage (or potential difference) is the **energy** required to move a **unit charge** through an element, measured in volts (V).

Mathematically, $v_{ab} = dw / dq$ (volt)

w is energy in joules (J) and q is charge in coulomb (C).

Electric voltage, v_{ab} , is always **across the circuit element** or **between two points in a circuit**.

$v_{ab} > 0$ means the potential of **a** is higher than potential of **b**.


$v_{ab} < 0$ means the potential of **a** is lower than potential of **b**.

10

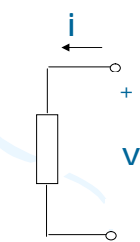1.5 Power and Energy (1)


Power is the time rate of expending or absorbing energy, measured in watts (W).

Mathematical expression: $p = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = vi$



$P = +vi$
absorbing power

Passive sign convention

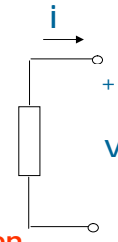

$p = vi$
supplying power

11

1.5 Power and Energy (2)

The law of conservation of energy

$$\sum p = 0$$

Energy is the capacity to do work, measured in joules (J).


Mathematical expression $w = \int_0^t p dt = \int_0^t vidt$

12

1.6 Circuit Elements (1)

Active Elements

Passive Elements

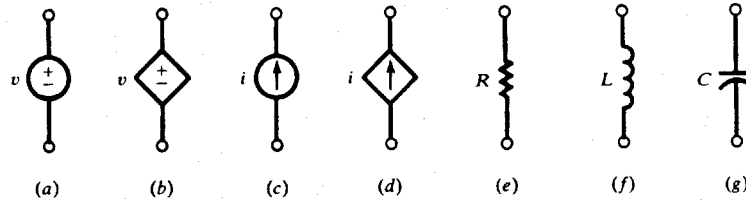

Independent sources Dependent sources

A dependent source is an active element in which the source quantity is controlled by another voltage or current.

They have four different types: VCVS, CCVS, VCCS, CCCS. Keep in mind the signs of dependent sources.

13

1.6 Circuit Elements (2)

Example 2

Obtain the voltage v in the branch shown in Figure 2.1.1P for $i_2 = 1\text{ A}$.

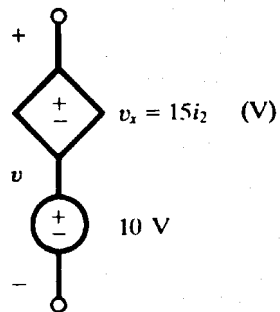



Figure 2.1.1P

14



1.6 Circuit Elements (3)

Solution

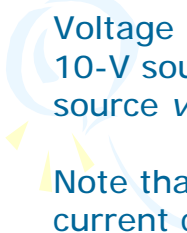

Voltage v is the sum of the current-independent 10-V source and the current-dependent voltage source v_x .

Note that the factor 15 multiplying the control current carries the units Ω .

Therefore, $v = 10 + v_x = 10 + 15(1) = 25 \text{ V}$

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.