

14.62 Find the steady-state response $v_o(t)$, for $t > 0$, in the network in Fig. P14.62.


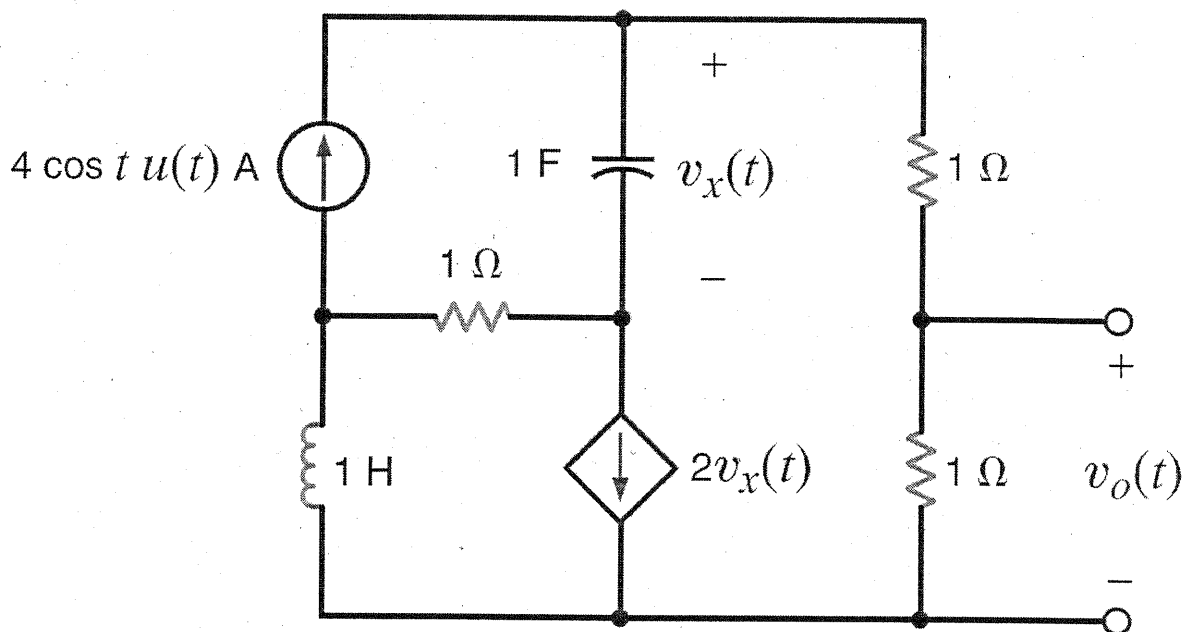


Figure P14.62

SOLUTION:

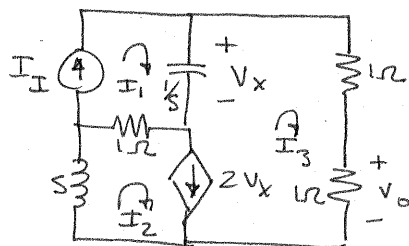

$$I_1 = I_1 \quad I_2 - I_3 = 2V_x = 2(I_1 - I_3)/s$$

$$\text{yields } I_2 = \frac{2I_1}{s} + I_3 \left(1 - \frac{2}{s}\right)$$

and

$$I_2(s+1) + I_3(2 + 1/s) - I_1(1 + 1/s) = 0$$

$$I_1 \left[\frac{2}{s}(s+1) - \frac{s+1}{s} \right] + I_3 \left[\frac{s-2}{s}(s+1) + \frac{2s+1}{s} \right] = 0 \quad V_o = (1) I_3$$

$$I_1 [2s+2-s-1] + V_o [s^2-s-2+2s+1] = 0$$

$$V_o = -I_1 (s+1) / (s^2+s-1)$$

$$\text{In steady state, } I_1 = 4 \angle 0^\circ \text{ A \& } s = j1 \Rightarrow V_o = 2.53 \angle 71.6^\circ \text{ V}$$

$$v_o(t) = 2.53 \cos(t + 71.6^\circ) \text{ V}$$