

14.24 Use Thévenin's theorem to find $v_o(t)$, $t > 0$, in the network in Fig. P14.24.


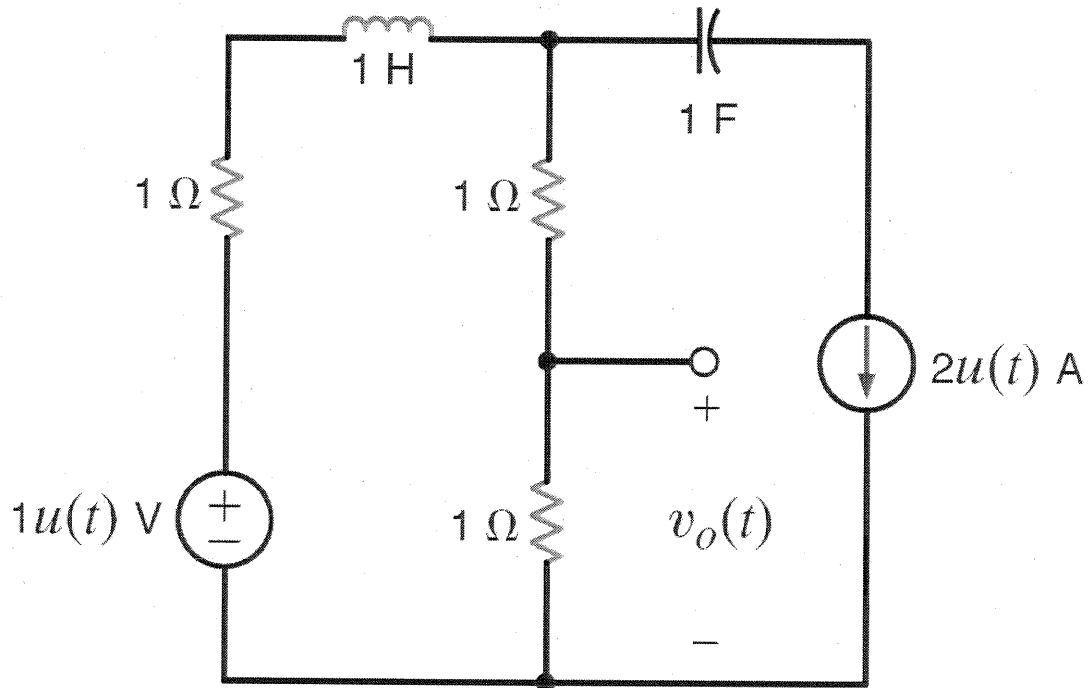


Figure P14.24


SOLUTION:

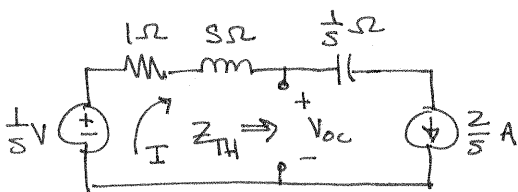

$$I = \frac{2}{s} A \quad \frac{1}{s} = (s+1)I + V_{OC}$$

$$\text{So, } V_{OC} = -\frac{(2s+1)}{s}$$

$$Z_{TH} = s + 1 \Omega$$

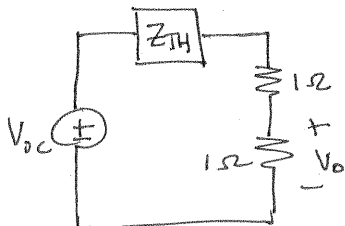

$$V_o = \frac{V_{OC} (1)}{2 + Z_{TH}} = -\frac{(2s+1)}{s} \cdot \frac{1}{s+3} = -\frac{(2s+1)}{s(s+3)}$$

$$V_o = \frac{-1/3}{s} - \frac{5/3}{s+3}$$

$$v_o(t) = \left[-\frac{1}{3} - \frac{5}{3} e^{-3t} \right] u(t) V$$