

14.5 Use Laplace transforms and nodal analysis to find $i_1(t)$ for $t > 0$ in the network shown in Fig. P14.5. Assume zero initial conditions.


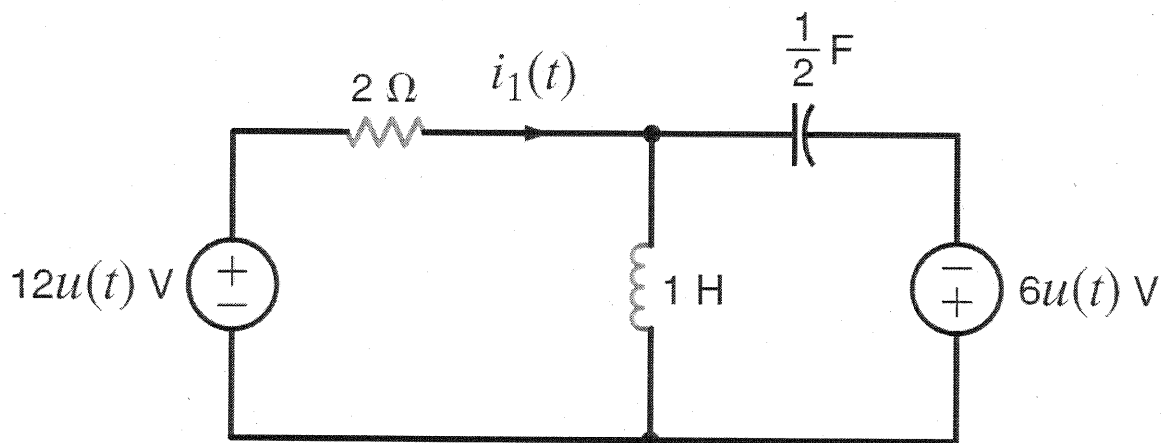


Figure P14.5

SOLUTION:

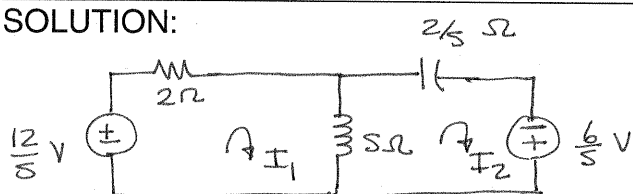

$$\frac{12}{s} = I_1 [s+2] - s I_2$$

$$\frac{6}{s} = -s I_1 + I_2 \left[s + \frac{2}{s} \right]$$

$$\text{or, } \frac{12}{s} = I_1 [s+2] - s I_2 \quad \& \quad \frac{6}{s} = -s I_1 + I_2 \left[\frac{s^2+2}{s} \right]$$

$$\text{Solve for } I_1 \text{ yields } I_1(s) = \frac{3(3s^2+4)}{s(s^2+s+2)}$$

$$I_1(s) = \frac{K_1}{s} + \frac{K_2}{s + \frac{1}{2} - j\frac{\sqrt{7}}{2}} + \frac{K_2^*}{s + \frac{1}{2} + j\frac{\sqrt{7}}{2}} \quad K_1 = 6$$

$$K_2 = \left. \frac{3(3s^2+4)}{s(s + \frac{1}{2} + j\frac{\sqrt{7}}{2})} \right|_{s = -\frac{1}{2} + j\frac{\sqrt{7}}{2}} = 3.21 \angle 62.1^\circ$$

$$i_1(t) = [6 + 6.42 e^{-t/2} \cos(\sqrt{7}t/2 + 62.1^\circ)] u(t) \text{ V} \quad \checkmark$$