
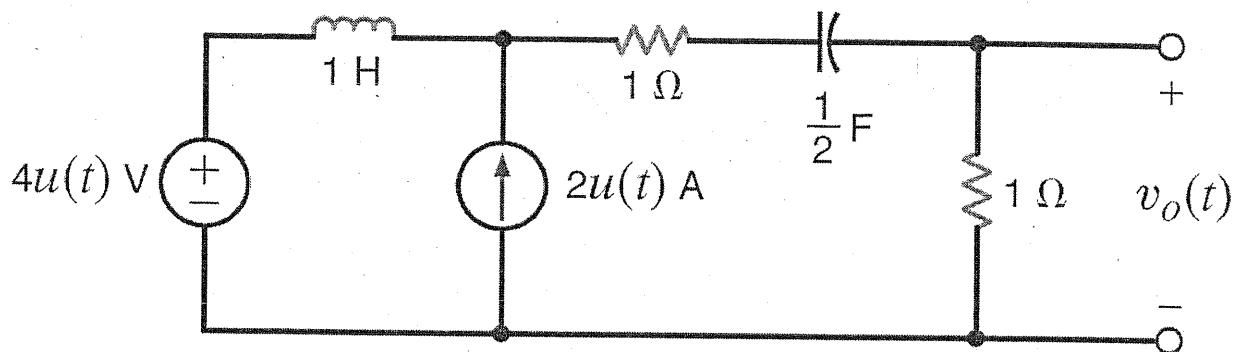


**14.6** For the network shown in Fig. P14.6, find  $v_o(t)$ ,  $t > 0$ , using node equations. **PSV**

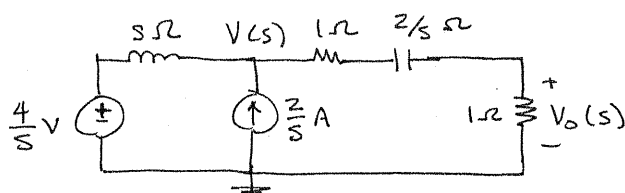

**Figure P14.6**

**SOLUTION:** at  $t=0^-$ , no excitation. So initial conditions = 0.



$$\frac{V - 4/s}{s} + \frac{V}{2 + 2/s} = \frac{2}{s}$$

$$\frac{V}{s} + \frac{Vs}{2(s+1)} = \frac{2}{s} + \frac{4}{s^2}$$

$$V \left[ s(s+1) + \frac{s^3}{2} \right] = 2s(s+1) + 4(s+1) = 2s^2 + 6s + 4$$

$$\frac{V}{2} \left[ s^3 + 2s^2 + 2s \right] = 2(s^2 + 3s + 2) \Rightarrow V = \frac{4(s+1)(s+2)}{s(s^2 + 2s + 2)}$$

$$V_o = V \left[ \frac{1}{2 + 2/s} \right] = V \left[ \frac{s}{2(s+1)} \right] = \frac{2(s+2)}{(s+1-j1)(s+1+j1)}$$

$$V_o = \frac{K_1}{s+1-j1} + \frac{K_1^*}{s+1+j1} \quad K_1 = \frac{2(1+j1)}{j2} = \sqrt{2} \angle -45^\circ$$

$$v_o(t) = \left[ \sqrt{2} e^{-t} \cos(t - 45^\circ) \right] u(t) \quad \checkmark$$