

Microelectronic Circuit Design

Third Edition - Part III

Solutions to Exercises

CHAPTER 10

Page 509

$$V_o = \sqrt{2P_o R_L} = \sqrt{2(20W)(16\Omega)} = 25.3 \text{ V} \quad A_v = \frac{V_o}{V_i} = \frac{25.3V}{0.005V} = 5.06 \times 10^3$$

$$I_o = \frac{V_o}{R_L} = \frac{25.3V}{16\Omega} = 1.58 \text{ A} \quad I_i = \frac{V_i}{R_S + R_{in}} = \frac{0.005V}{10k\Omega + 20k\Omega} = 0.167\mu\text{A} \quad A_i = \frac{I_o}{I_i} = \frac{1.58 \text{ A}}{0.167\mu\text{A}} = 9.48 \times 10^6$$

$$A_p = \frac{P_o}{P_s} = \frac{25.3V(1.58 \text{ A})}{0.005V(0.167\mu\text{A})} = 4.79 \times 10^{10} \quad \text{Checking: } A_p = (5.06 \times 10^3)(9.48 \times 10^6) = 4.80 \times 10^{10}$$

Page 510

$$(i) A_{vdB} = 20 \log(5060) = 74.1 \text{ dB} \quad A_{idB} = 20 \log(9.48 \times 10^6) = 140 \text{ dB} \quad A_{pdB} = 10 \log(4.80 \times 10^{10}) = 107 \text{ dB}$$

$$(ii) A_{vdB} = 20 \log(4 \times 10^4) = 92.0 \text{ dB} \quad A_{idB} = 20 \log(2.75 \times 10^8) = 169 \text{ dB} \quad A_{pdB} = 10 \log(1.10 \times 10^{13}) = 130 \text{ dB}$$

Page 511

(i) The constant slope region spanning a maximum input range is between $0.4 \leq v_i \leq 0.65$,

and the bias voltage V_I should be centered in this range: $V_I = \frac{0.4 + 0.65}{2} V = 0.525 \text{ V}$.

$v_i \leq 0.65 - 0.525 = 0.125 \text{ V}$ and $v_i \leq 0.525 - 0.40 = 0.125 \text{ V}$. For $v_i = 0.8 \text{ V}$, the slope is 0. $A_v = 0$.

(ii) $v_o = V_o + v_o$. For $v_i = 0$, $v_i = V_I = 0.6$, $V_o = 14 \text{ V}$ and $A_v = +40$. $V_o = A_v V_i = 40(0.01 \text{ V}) = 4 \text{ V}$

$v_o = (14.0 + 4.00 \sin 1000\pi t)$ volts $V_o = 14 \text{ V}$

Page 519

$$g_{11} = \frac{1}{20k\Omega + 76(50k\Omega)} = 0.262 \mu S \quad g_{21} = 0.262 \mu S (76)(50k\Omega) = 0.995$$

$$g_{22} = \frac{1}{50k\Omega} + \frac{1}{20k\Omega} + \frac{75}{20k\Omega} = 3.82 mS \quad g_{12} = -\frac{1}{g_{22}(20k\Omega)} = -\frac{1}{3.82mS(20k\Omega)} = -0.0131$$

$$R_{in} = \frac{1}{g_{11}} = 3.82 M\Omega \quad A = g_{21} = 0.995 \quad R_{out} = \frac{1}{g_{22}} = 262 \Omega$$

Page 520

$$(i) P = A_v A_i = A_v^2 \frac{R_s + R_{in}}{R_L}$$

$$(ii) V_o = \sqrt{2(100W)(8\Omega)} = 40 V \quad 40 = 0.001 \left(\frac{50k\Omega}{5k\Omega + 50k\Omega} \right) A \left(\frac{8\Omega}{0.5\Omega + 8\Omega} \right) \rightarrow A = 46,800$$

$$P = \frac{I_o^2 R_L}{2} = \frac{0.5\Omega}{2} \left(\frac{40V}{8\Omega} \right)^2 = 6.25 W \quad A_i = \left(\frac{40V}{8\Omega} \right) \left(\frac{5k\Omega + 50k\Omega}{0.001V} \right) = 2.75 \times 10^8$$

$$(iii) 40 = 0.001 \left(\frac{5k\Omega}{5k\Omega + 5k\Omega} \right) A \left(\frac{8\Omega}{8\Omega + 8\Omega} \right) \rightarrow A = 160,000$$

$$P = \frac{I_o^2 R_L}{2} = \frac{8\Omega}{2} \left(\frac{40V}{8\Omega} \right)^2 = 100 W! \quad A_i = \left(\frac{40V}{8\Omega} \right) \left(\frac{5k\Omega + 5k\Omega}{0.001V} \right) = 5.00 \times 10^7$$

Page 521

$$A_v(s) = \frac{300s}{(s + 5000)(s + 100)} \quad \text{Zeros at } s = 0 \text{ and } s = \infty; \text{ Poles at } s = -5000 \text{ and } s = -100.$$

Page 523

$$A_v(s) = -\frac{2\pi \times 10^6}{s + 5000\pi} = \frac{-400}{1 + \frac{s}{5000\pi}} \rightarrow A_{mid} = -400 \quad f_H = \frac{5000\pi}{2\pi} = 2.50 \text{ kHz}$$

$$BW = f_H - f_L = 2.50 \text{ kHz} - 0 = 2.50 \text{ kHz} \quad GBW = (400)(2.50 \text{ kHz}) = 1.00 \text{ MHz}$$

Page 524

$$(i) |A_v(j5)| = 50 \frac{|5^2 - 4|}{\sqrt{(5^2 - 2)^2 + 4(5^2)}} = 41.87 \quad 20 \log(41.87) = 32.4 \text{ dB}$$

$$\angle A_v(j5) = \angle(5^2 - 4) - \tan^{-1} \left[\frac{-2(5)}{5^2 - 2} \right] = 0 - (-23.5^\circ) = 23.5^\circ$$

$$|A_v(j1)| = 50 \frac{|1^2 - 4|}{\sqrt{(1^2 - 2)^2 + 4(1^2)}} = 67.08 \quad 20 \log(41.87) = 36.5 \text{ dB}$$

$$\angle A_v(j1) = \angle(1^2 - 4) - \tan^{-1} \left[\frac{-2(1)}{1^2 - 2} \right] = 180^\circ - (-63.43^\circ) = 243^\circ = -117^\circ$$

Page 524

$$(ii) A_v(j\omega) = \frac{20}{1 + j \frac{0.1\omega}{1 - \omega^2}}$$

$$|A_v(j0.95)| = \frac{20}{\sqrt{1^2 + \frac{(0.1)^2(0.95^2)}{(1 - 0.95^2)^2}}} = 14.3 \quad \angle A_v(j0.95) = \angle 20 - \tan^{-1} \left[\frac{0.1(0.95)}{1 - 0.95^2} \right] = 0 - (44.3^\circ) = -44.3^\circ$$

$$|A_v(j1)| = \frac{20}{\sqrt{1^2 + \frac{(0.1)^2(1^2)}{(1 - 1^2)^2}}} = 0 \quad \angle A_v(j1) = \angle 20 - \tan^{-1} \left[\frac{0.1(1)}{1 - 1^2} \right] = 0 - (90^\circ) = -90.0^\circ$$

$$|A_v(j1.1)| = \frac{20}{\sqrt{1^2 + \frac{(0.1)^2(1.1^2)}{(1 - 1.1^2)^2}}} = 17.7 \quad \angle A_v(j1.1) = \angle 20 - \tan^{-1} \left[\frac{0.1(1.1)}{1 - 1.1^2} \right] = 0 - (-27.6^\circ) = 27.6^\circ$$

Page 526

$$f_H = \frac{1}{2\pi (1k\Omega \parallel 100k\Omega)(200pF)} = 804 \text{ kHz}$$

Page 527

$$A_v(s) = \frac{250}{1 + \frac{250\pi}{s}} \quad A_o = 250 \quad f_L = \frac{250\pi}{2\pi} = 125 \text{ Hz} \quad f_H = \infty \quad BW = \infty - 125 = \infty$$

Page 528

$$f_L = \frac{1}{2\pi} \frac{1}{(1k\Omega \parallel 100k\Omega)(0.1\mu F)} = 15.8 \text{ Hz}$$

Page 529

$$(i) A_v(s) = \frac{-400}{\left(1 + \frac{100}{s}\right)\left(1 + \frac{s}{50000}\right)} \quad A_o = 400 \text{ or } 52 \text{ dB}$$

$$f_L = \frac{100}{2\pi} = 15.9 \text{ Hz} \quad f_H = \frac{50000}{2\pi} = 7.96 \text{ kHz} \quad BW = 7960 - 15.9 = 7.94 \text{ kHz}$$

$$(ii) \angle A_v(j0) = -90 - 0 - 0 = -90^\circ$$

$$\angle A_v(j100) = -90^\circ - \tan^{-1}\left(\frac{100}{100}\right) - \tan^{-1}\left(\frac{100}{50000}\right) = -90 - 45 - 0.57 = -136^\circ$$

$$\angle A_v(j50000) = -90^\circ - \tan^{-1}\left(\frac{50000}{100}\right) - \tan^{-1}\left(\frac{50000}{50000}\right) = -90 - 89.9 - 45 = -225^\circ$$

$$\angle A_v(j\infty) = -90 - 90 - 90 = -270^\circ$$

Page 531

The numerator coefficient should be 6×10^6 .

$$A_v(s) = 30 \frac{2 \times 10^5 s}{s^2 + 2 \times 10^5 s + 10^{14}} \quad A_o = 30$$

$$f_o = \frac{1}{2\pi} \sqrt{10^{14}} = 1.59 \text{ MHz} \quad Q = \frac{10^7}{2 \times 10^5} = 50 \quad BW = \frac{1.59 \text{ MHz}}{50} = 31.8 \text{ kHz}$$

Page 533

The transfer function should be $A_v(s) = \frac{6.4 \times 10^{12} \pi^2 s}{(s + 200\pi)(s + 80000\pi)^2}$.

$$A_v(s) = \frac{1000}{\left(1 + \frac{200\pi}{s}\right)\left(1 + \frac{s}{80000\pi}\right)^2} \quad A_o = 1000 \text{ or } 60 \text{ dB}$$

$$f_L = \frac{200\pi}{2\pi} = 100 \text{ Hz} \quad f_H = 0.644 \left(\frac{80000\pi}{2\pi}\right) = 25.8 \text{ kHz} \quad BW = 25800 - 100 = 25.7 \text{ kHz}$$

CHAPTER 11

Page 545

$$v_{id} = \frac{10V}{100} = 0.100V = 100 \text{ mV} \quad v_{id} = \frac{10V}{10^4} = 0.001 \text{ V} = 1.00 \text{ mV} \quad v_{id} = \frac{10V}{10^6} = 1.00 \times 10^{-5} \text{ V} = 10.0 \text{ } \mu\text{V}$$

Page 547

$$A_v = -\frac{360k\Omega}{68k\Omega} = -5.29 \quad v_o = -5.29(0.5V) = -2.65 \text{ V} \quad i_s = \frac{0.5V}{68k\Omega} = 7.35 \text{ } \mu\text{A} \quad i_o = -i_2 = -i_s = -7.35 \text{ } \mu\text{A}$$

Page 549

$$I_s = \frac{2V}{4.7k\Omega} = 426 \text{ } \mu\text{A} \quad I_2 = I_s = 426 \text{ } \mu\text{A} \quad A_v = -\frac{24k\Omega}{4.7k\Omega} = -5.11 \quad V_o = -5.11(2V) = -10.2 \text{ V}$$

Page 551

$$A_v = 1 + \frac{36k\Omega}{2k\Omega} = +19.0 \quad v_o = 19.0(-0.2V) = -3.80 \text{ V} \quad i_o = \frac{-3.80V}{36k\Omega + 2k\Omega} = -100 \text{ } \mu\text{A}$$

Page 552

$$(i) \quad A_v = 1 + \frac{39k\Omega}{1k\Omega} = +40.0 \quad A_{vdB} = 20 \log(40.0) = 32.0 \text{ dB} \quad R_{in} = 100k\Omega \parallel \infty = 100k\Omega$$

$$v_o = 40.0(0.25V) = 10.0 \text{ V} \quad i_o = \frac{10.0V}{39k\Omega + 1k\Omega} = 250 \text{ } \mu\text{A}$$

$$(ii) \quad A_v = 10^{\frac{54}{20}} = 501 \quad 1 + \frac{R_2}{R_1} = 501 \quad \frac{R_2}{R_1} = 500 \quad i_o = \frac{v_o}{R_2 + R_1} \quad \frac{10}{R_2 + R_1} \leq 0.1 \text{ mA}$$

$R_1 + R_2 \geq 100k\Omega$ $501R_1 \geq 100k\Omega \rightarrow R_1 \geq 200 \text{ } \Omega$ There are many possibilities.
 ($R_1 = 200 \text{ } \Omega$, $R_2 = 100 \text{ k}\Omega$), but ($R_1 = 220 \text{ } \Omega$, $R_2 = 110 \text{ k}\Omega$) is a better solution since resistor tolerances could cause i_o to exceed 0.1 mA in the first case.

Page 554

Inverting Amplifier: $A_v = -\frac{30k\Omega}{1.5k\Omega} = -20.0 \quad R_{in} = R_1 = 1.5 \text{ k}\Omega$

$$v_o = -20.0(0.15V) = -3.00 \text{ V} \quad i_o = \frac{v_o}{R_2} = \frac{-3.00V}{30k\Omega} = -100 \text{ } \mu\text{A}$$

Non - Inverting Amplifier: $A_v = 1 + \frac{30k\Omega}{1.5k\Omega} = +21.0 \quad R_{in} = \frac{v_s}{i_s} = \frac{0.15V}{0A} = \infty$

$$v_o = 21.0(0.15V) = 3.15 \text{ V} \quad i_o = \frac{v_o}{R_2 + R_1} = \frac{3.15V}{30k\Omega + 1.5k\Omega} = 100 \text{ } \mu\text{A}$$

Page 555

$$V_{o1} = 2V \left(-\frac{3k\Omega}{1k\Omega} \right) = -6V \quad V_{o2} = 4V \left(-\frac{3k\Omega}{2k\Omega} \right) = -6V \quad v_o = (-6 \sin 1000\pi t - 6 \sin 2000\pi t) V$$

The summing junction is a virtual ground: $R_{in1} = \frac{v_1}{i_1} = R_1 = 1 k\Omega$ $R_{in2} = \frac{v_2}{i_2} = R_2 = 2 k\Omega$

$$I_{o1} = \frac{V_{o1}}{R_3} = \frac{-6V}{3k\Omega} = -2mA \quad I_{o2} = \frac{V_{o2}}{R_3} = \frac{-6V}{3k\Omega} = -2mA \quad i_o = (-2 \sin 1000\pi t - 2 \sin 2000\pi t) mA$$

Page 559

$$(i) I_2 = \frac{3V}{10k\Omega + 100k\Omega} = 27.3 \mu A$$

$$(ii) A_v = -\frac{100k\Omega}{10k\Omega} = -10.0 \quad V_o = -10(3V - 5V) = 20.0 V \quad I_o = \frac{V_o - V_-}{100k\Omega} = \frac{V_o - V_+}{100k\Omega}$$

$$V_+ = V_2 \frac{R_4}{R_3 + R_4} = 5 \frac{100k\Omega}{10k\Omega + 100k\Omega} = 4.545V \quad I_o = \frac{20.0 - 4.545}{100k\Omega} = 155 \mu A \quad I_2 = \frac{5V}{10k\Omega + 100k\Omega} = 45.5 \mu A$$

$$(iii) A_v = -\frac{36k\Omega}{2k\Omega} = -18.0 \quad V_o = -18(8V - 8.25V) = 4.50 V \quad I_o = \frac{V_o - V_-}{36k\Omega} = \frac{V_o - V_+}{36k\Omega}$$

$$V_+ = V_2 \frac{R_2}{R_1 + R_2} = 8.25 \frac{36k\Omega}{2k\Omega + 36k\Omega} = 7.816V \quad I_o = \frac{4.50 - 7.816}{36k\Omega} = -92.1 \mu A$$

Page 560

$$I = \frac{V_A - V_B}{2R_1} = \frac{5.001V - 4.999V}{2k\Omega} = 1.00 \mu A$$

$$V_A = V_1 + IR_2 = 5.001V + 1.00\mu A(49k\Omega) = 5.05 V$$

$$V_B = V_2 - IR_2 = 4.999V - 1.00\mu A(49k\Omega) = 4.95 V$$

$$V_o = \left(-\frac{R_4}{R_3} \right) (V_A - V_B) = \left(-\frac{10k\Omega}{10k\Omega} \right) (5.05 - 4.95) = -0.100 V$$


Page 564

$$(i) A_v = -\frac{R_2}{R_1} = -10^{\frac{26}{20}} = -20.0 \quad R_1 = R_{in} = 10k\Omega \quad R_2 = 20R_1 = 200k\Omega$$

$$C = \frac{1}{2\pi(3kHz)(200k\Omega)} = 265 pF \quad \text{Closest values: } R_1 = 10k\Omega \quad R_2 = 200k\Omega \quad C = 270 pF$$

Page 564

$$(ii) R_{in} = R_1 = 10 \text{ k}\Omega \quad \Delta V = -\frac{I}{C} \Delta T \quad C = \frac{5V}{10\text{k}\Omega} \left(\frac{1}{10V} \right) (1\text{ms}) = 0.05 \mu\text{F}$$

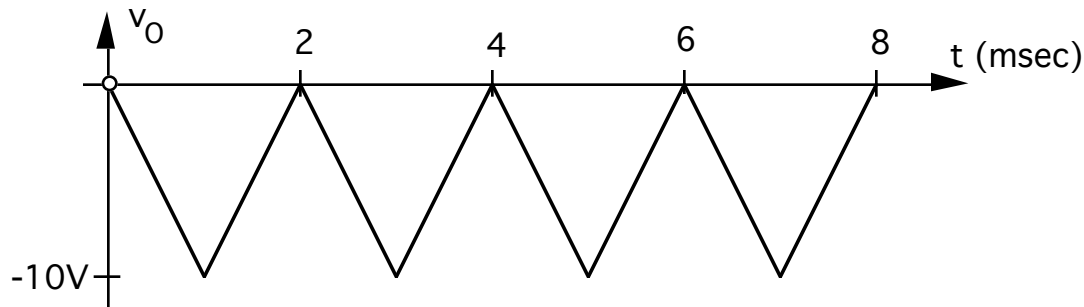**Page 567**

$$v_o = -RC \frac{dv_s}{dt} = -(20\text{k}\Omega)(0.02 \mu\text{F})(2.50\text{V})(2000\pi)(\cos 2000\pi t) = -6.28 \cos 2000\pi t \text{ V}$$

Page 569

$$(i) A_{vA} = A_{vB} = A_{vC} = -\frac{R_2}{R_1} = -\frac{68\text{k}\Omega}{2.7\text{k}\Omega} = -25.2 \quad R_{inA} = R_{inB} = R_{inC} = R_1 = 2.7 \text{ k}\Omega$$

The op-amps are ideal: $R_{outA} = R_{outB} = R_{outC} = 0$

$$(ii) A_v = A_{vA} A_{vB} A_{vC} = (-25.2)^3 = -16,000 \quad R_{in} = R_{inA} = 2.7 \text{ k}\Omega \quad R_{out} = R_{outC} = 0$$

Page 570

$$A_v = (-25.2)^3 \left(\frac{2.7\text{k}\Omega}{R_{out} + 2.7\text{k}\Omega} \right)^2 \geq 0.99(25.2)^3 \quad \left(\frac{2.7\text{k}\Omega}{R_{out} + 2.7\text{k}\Omega} \right)^2 \geq 0.99$$

$$\frac{2.7\text{k}\Omega}{R_{out} + 2.7\text{k}\Omega} \geq 0.9950 \quad R_{out} \geq 13.6 \Omega$$

Page 574

$$(i) A_v(0) = +1 \quad A_v(s) = \frac{\omega_o^2}{s^2 + s\sqrt{2}\omega_o + \omega_o^2} \quad A_v(j\omega) = \frac{\omega_o^2}{j\omega\sqrt{2}\omega_o + \omega_o^2 - \omega^2}$$

$$|A_v(j\omega_H)| = \frac{1}{\sqrt{2}} \rightarrow \frac{\omega_o^2}{\sqrt{(\omega_o^2 - \omega_H^2)^2 + 2\omega_H^2\omega_o^2}} = \frac{1}{\sqrt{2}} \rightarrow 2\omega_o^4 = \omega_o^4 + \omega_H^4 \rightarrow \omega_o = \omega_H$$

$$(ii) \frac{1}{\sqrt{2}} = \sqrt{\frac{C_1}{C_2}} \frac{\sqrt{R^2}}{2R} \rightarrow C_1 = 2C_2 \rightarrow C_2 = \frac{1}{\sqrt{2}(2.26\text{k}\Omega)(20000\pi)} = 4.98\text{nF}$$

$$C_2 = 0.005 \mu\text{F} \quad C_1 = 0.01 \mu\text{F}$$

Page 574

(iii) To decrease the cutoff frequency from 5kHz to 2 kHz, we must increase the resistances by a factor of $\frac{5\text{kHz}}{2\text{kHz}} = 2.50 \rightarrow R_1 = R_2 = 2.50(2.26\text{k}\Omega) = 5.65 \text{ k}\Omega$

$$(iv) \frac{1}{\sqrt{2}} = \sqrt{\frac{C}{C} \frac{\sqrt{R_1 R_2}}{R_1 + R_2}} \rightarrow R_1^2 + 2R_1 R_2 + R_2^2 = 2R_1 R_2 \rightarrow R_1^2 = -R_2^2 \quad \text{-- can't be done!}$$

$$Q = \frac{\sqrt{R_1 R_2}}{R_1 + R_2} \quad \frac{dQ}{dR_2} = \frac{1}{(R_1 + R_2)^2} \left[\frac{R_1(R_1 + R_2)}{2\sqrt{R_1 R_2}} - \sqrt{R_1 R_2} \right] = 0 \rightarrow R_2 = R_1 \rightarrow Q_{\max} = \frac{1}{2}$$

Page 575

$$S_{C_1}^Q = \frac{C_1}{Q} \frac{dQ}{dC_1} = \frac{C_1}{Q} \left[\frac{1}{2\sqrt{C_1 C_2}} \frac{\sqrt{R_1 R_2}}{R_1 + R_2} \right] = \frac{C_1}{Q} \frac{Q}{2C_1} = 0.5$$

$$S_{R_2}^Q = \frac{R_2}{Q} \frac{dQ}{dR_2} \quad R_1 = R_2 \rightarrow Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}} \rightarrow S_{R_2}^Q = 0$$

Page 577

$$(i) |A_v(j\omega_o)| = K \left| \frac{-\omega_o^2}{-\omega_o^2 + j(3-K)\omega_o^2 + \omega_o^2} \right| = \frac{K}{3-K} \quad A_v(j\omega_o) = \frac{K}{3-K} \angle 90^\circ$$

$$(ii) f_o = \frac{1}{2\pi \sqrt{10\text{k}\Omega(20\text{k}\Omega)(0.0047\mu\text{F})(0.001\mu\text{F})}} = 5.19 \text{ kHz}$$

$$Q = \left[\sqrt{\frac{10\text{k}\Omega}{20\text{k}\Omega}} \frac{4.7\text{nF} + 1.0\text{nF}}{\sqrt{4.7\text{nF}(1.0\text{nF})}} + (1-2) \sqrt{\frac{20\text{k}\Omega(1.0\text{nF})}{10\text{k}\Omega(4.7\text{nF})}} \right]^{-1} = 0.829$$

$$(iii) S_K^Q = \frac{K}{Q} \frac{dQ}{dK} \quad Q = \frac{1}{3-K} \quad \frac{dQ}{dK} = \frac{-1}{(3-K)^2} (-1) = Q^2 \quad S_K^Q = \frac{K}{Q} \frac{dQ}{dK} = KQ$$

$$Q = \frac{1}{3-K} \rightarrow KQ = 3Q - 1 \quad S_K^Q = 3Q - 1 = 1.12$$

Page 578

$$R_{th} = 2\text{k}\Omega \parallel 2\text{k}\Omega = 1\text{k}\Omega \quad f_o = \frac{1}{2\pi \sqrt{1\text{k}\Omega(82\text{k}\Omega)(0.02\mu\text{F})(0.02\mu\text{F})}} = 879 \text{ Hz} \quad Q = \frac{1}{2} \sqrt{\frac{82\text{k}\Omega}{1\text{k}\Omega}} = 4.53$$

Page 582

$$(ii) |A_{BP}(j\omega_o)| = KQ = \frac{R_2}{R_1} \quad 10 = \frac{294k\Omega}{R_1} \rightarrow R_1 = 29.4 k\Omega$$

$$(iii) f_o = \frac{1}{2\pi RC} = \frac{1}{2\pi(40.2k\Omega)(2nF)} = 1.98 kHz \quad BW = \frac{1}{2\pi R_2 C} = \frac{1}{2\pi(402k\Omega)(2nF)} = 198 Hz$$

$$A_{BP}(j\omega_o) = -\frac{R_2}{R_1} = -\frac{402k\Omega}{20.0k\Omega} = -20.1$$

(iv) Blindly using the equations at the top of page 580 yields

$$f_o^{\min} = \frac{1}{2\pi RC} = \frac{1}{2\pi(1.01)(29.4k\Omega)(1.02)(2.7nF)} = 1946 Hz$$

$$f_o^{\max} = \frac{1}{2\pi RC} = \frac{1}{2\pi(0.99)(29.4k\Omega)(0.98)(2.7nF)} = 2067 Hz$$

$$BW^{\min} = \frac{1}{2\pi R_2 C} = \frac{1}{2\pi(1.01)(294k\Omega)(1.02)(2.7nF)} = 195 Hz$$

$$BW^{\max} = \frac{1}{2\pi R_2 C} = \frac{1}{2\pi(0.99)(294k\Omega)(0.98)(2.7nF)} = 207 Hz$$

$$A_{BP}^{\min} = -\frac{R_2}{R_1} = -\frac{294k\Omega(1.01)}{14.7k\Omega(0.99)} = -20.4 \quad A_{BP}^{\max} = -\frac{R_2}{R_1} = -\frac{294k\Omega(0.99)}{14.7k\Omega(1.01)} = -19.6$$

The W/C results are similar if R and C are not the same for example where $\omega_o = \frac{1}{\sqrt{R_A R_B C_A C_B}}$.

Page 583

$$(i) - (a) R_1 = R_2 = 5(2.26k\Omega) = 11.3 k\Omega \quad C_1 = \frac{0.02\mu F}{5} = 0.004 \mu F \quad C_2 = \frac{0.01\mu F}{5} = 0.002 \mu F$$

$$f_o = \frac{1}{2\pi\sqrt{(11.3k\Omega)(11.3k\Omega)(0.004\mu F)(0.002\mu F)}} = 4980 Hz$$

$$Q = \sqrt{\frac{11.3k\Omega}{11.3k\Omega} \frac{\sqrt{(0.004\mu F)(0.002\mu F)}}{0.004\mu F + 0.002\mu F}} = 0.471$$

$$(b) R_1 = R_2 = 0.885(2.26k\Omega) = 2.00 k\Omega \quad C_1 = \frac{0.02\mu F}{0.885} = 0.0226 \mu F \quad C_2 = \frac{0.01\mu F}{0.885} = 0.0113 \mu F$$

$$f_o = \frac{1}{2\pi\sqrt{(2.00k\Omega)(2.00k\Omega)(0.0226\mu F)(0.0113\mu F)}} = 4980 Hz$$

$$Q = \sqrt{\frac{2.00k\Omega}{2.00k\Omega} \frac{\sqrt{(0.0226\mu F)(0.0113\mu F)}}{0.0226\mu F + 0.0113\mu F}} = 0.471$$

Page 583

$$(ii) f_o = \frac{1}{2\pi\sqrt{(1k\Omega)(82k\Omega)(0.02\mu F)(0.02\mu F)}} = 879 \text{ Hz} \quad Q = \sqrt{\frac{82k\Omega}{1k\Omega} \frac{\sqrt{(0.02\mu F)(0.02\mu F)}}{0.02\mu F + 0.02\mu F}} = 4.53$$

The values of the resistors are unchanged. $C_1 = C_2 = \frac{0.02\mu F}{4} = 0.005 \mu F$

$$f_o = \frac{1}{2\pi\sqrt{(1k\Omega)(82k\Omega)(0.005\mu F)(0.005\mu F)}} = 3520 \text{ Hz} \quad Q = \sqrt{\frac{82k\Omega}{1k\Omega} \frac{\sqrt{(0.005\mu F)(0.005\mu F)}}{0.005\mu F + 0.005\mu F}} = 4.53$$

Page 585

The diode will conduct and pull the output up to $v_o = v_s = 1.0 \text{ V}$. $v_1 = v_o + v_D = 1.0 + 0.6 = 1.6 \text{ V}$

For a negative input, there is no path for current through R, so $v_o = 0 \text{ V}$. The op - amp sees a -1V input so the output will limit at the negative power supply: $v_o = -10 \text{ V}$.

The diode has a 10 - V reverse bias across it, so $V_Z > 10 \text{ V}$.

Page 587

(i) $v_s = 2 \text{ V}$: Diode D_1 conducts, and D_2 is off. The negative input is a virtual ground.

$v_1 = -v_{D2} = -0.6 \text{ V}$. The current in R is 0, so $v_o = 0 \text{ V}$.

$v_s = -2 \text{ V}$: Diode D_2 conducts, and D_1 is off. The negative input is a virtual ground.

$$v_o = -\frac{R_2}{R_1}v_s = -\frac{68k\Omega}{22k\Omega}(-2V) = +6.18 \text{ V} \quad v_1 = v_o + v_{D1} = 6.78 \text{ V}.$$

$v_s = \frac{15V}{-3.09} = -4.85 \text{ V}$ $v_1 = v_o + v_{D1} = 6.78 \text{ V}$. When $v_o = 15 \text{ V}$, $v_{D2} = -15.6 \text{ V}$, so $V_Z = 15.6 \text{ V}$.

$$(ii) v_o = \frac{20k\Omega}{20k\Omega} \left(\frac{10.2k\Omega}{3.24k\Omega} \right) \frac{2V}{\pi} = 2.00 \text{ V}$$

Page 589

$$V_- = -\frac{R_1}{R_1 + R_2}V_{EE} = -\frac{1k\Omega}{1k\Omega + 9.1k\Omega}10V = -0.990 \text{ V} \quad V_+ = \frac{1k\Omega}{1k\Omega + 9.1k\Omega}10V = +0.990 \text{ V}$$

$$V_n = 0.990V - (-0.990V) = 1.98 \text{ V}$$

Page 591

$$T = 2(10k\Omega)(0.001\mu F) \ln\left(\frac{1+0.5}{1-0.5}\right) = 21.97\mu s \quad f = \frac{1}{T} = 45.5 \text{ kHz}$$

Page 594

$$\beta = -\frac{22k\Omega}{22k\Omega + 18k\Omega} = 0.550 \quad T = (11k\Omega)(0.002\mu F) \ln \left[\frac{1 + \frac{0.7}{5}}{1 - 0.550} \right] = 20.4 \mu s$$

$$T_r = (11k\Omega)(0.002\mu F) \ln \left[\frac{1 + 0.55 \left(\frac{5V}{5V} \right)}{1 - \frac{0.7}{5}} \right] = 13.0 \mu s$$

CHAPTER 12

Page 612

$$(i) A_{ideal} = \frac{1}{\beta} = 100 \quad A_v = \frac{A}{1 + A\beta} = \frac{10^5}{1 + 10^5(0.01)} = 99.90$$

$$v_o = 99.9(0.1V) = 9.99 V \quad v_{id} = \frac{v_o}{A} = \frac{9.99V}{10^5} = 99.9 \mu V$$

(ii) Values taken from OP - 27 specification sheet (www.jaegerblalock.com or www.analog.com)

(iii) Values taken from OP - 27 specification sheet

Page 613

$$A_v = \frac{-R_2}{R_1} \frac{A\beta}{1 + A\beta} \quad FGE = \frac{\left(\frac{-R_2}{R_1}\right) - \left(\frac{-R_2}{R_1} \frac{A\beta}{1 + A\beta}\right)}{\left(\frac{-R_2}{R_1}\right)} = 1 - \frac{A\beta}{1 + A\beta} = \frac{1}{1 + A\beta}$$

Page 614

$$FGE = \frac{1}{1 + A\beta} = \frac{1}{1 + 10^4 \left(\frac{1k\Omega}{1k\Omega + 39k\Omega}\right)} = 3.98 \times 10^{-3} \text{ or } 0.398 \% \quad FGE \cong \frac{1}{A\beta} = 0.40 \%$$

Page 615

Values taken from OP - 77 specification sheet (www.jaegerblalock.com or www.analog.com)

Page 616

$$A \cong \frac{R_o}{\beta R_{out}} = \frac{50\Omega}{(0.025)(0.1\Omega)} = 20,000$$

Page 617

$$(i) A_v = \frac{A}{1 + A\beta} = \frac{10^4}{1 + 10^4(0.025)} = +39.8$$

$$(ii) A_v^{max} = \frac{(39k\Omega + 1k\Omega)(1.05)}{1k\Omega(0.95)} = 44.2 \quad A_v^{max} = \frac{(39k\Omega + 1k\Omega)(0.95)}{1k\Omega(1.05)} = 36.2$$

$$GE = 44.2 - 40.0 = 4.20 \quad FGE = \frac{4.20}{40} = 10.5 \% \quad GE = 36.2 - 40.0 = -3.80 \quad FGE = \frac{-3.80}{40} = -9.5 \%$$

Page 618

$$A \cong \frac{R_o}{\beta R_{out}} = \frac{200\Omega}{(0.01)(0.1\Omega)} = 200,000 \quad A_{dB} = 20 \log(2 \times 10^5) = 106 \text{ dB}$$

Page 619

Values taken from op - amp specification sheets (www.jaegerblalock.com or www.analog.com)

Page 620

$$R_{in} = R_{id}(1 + A\beta) = 1M\Omega \left[1 + 10^4 \left(\frac{10k\Omega}{10k\Omega + 390k\Omega} \right) \right] = 251 \text{ M}\Omega$$

$$i_- = -\frac{v_s}{R_{in}} = -\frac{1V}{251 \text{ M}\Omega} = -3.98 \text{ nA} \quad i_1 = \frac{\beta v_o}{R_1} = \frac{A\beta}{1 + A\beta} \left(\frac{v_s}{R_1} \right) \cong \left(\frac{1V}{10k\Omega} \right) = 100 \text{ }\mu\text{A} \quad |i_1| \gg |i_-|$$

$$\text{More exactly, } i_1 = \frac{\beta v_o}{R_1} = \frac{A\beta}{1 + A\beta} \left(\frac{v_s}{R_1} \right) = \frac{10^4(0.025)}{1 + 10^4(0.025)} \left(\frac{1V}{10k\Omega} \right) = 99.6 \text{ }\mu\text{A}$$

Page 621

$$R_{in} = R_1 + R_{id} \left\| \frac{R_2}{1 + A} = 1k\Omega + 1M\Omega \left\| \frac{100k\Omega}{1 + 10^5} = 1001 \text{ }\Omega \quad R_{in}^{ideal} = R_1 = 1000 \text{ }\Omega \quad 1 \text{ }\Omega \text{ or } 0.1 \%$$

Page 622

Values taken from op - amp specification sheets (www.jaegerblalock.com or www.analog.com)

Page 626

$$v_o = A \left(v_{id} + \frac{v_{ic}}{CMRR} \right)$$

$$v_o^{\min} = A \left(v_{id} + \frac{v_{ic}}{CMRR} \right) = 2500 \left(0.002 - \frac{5.000}{10^4} \right) = 3.750 \text{ V}$$

$$v_o^{\max} = A \left(v_{id} + \frac{v_{ic}}{CMRR} \right) = 2500 \left(0.002 + \frac{5.000}{10^4} \right) = 6.250 \text{ V}$$

Page 627

$$A_v = \frac{A \left(1 + \frac{1}{2CMRR} \right)}{1 + A \left(1 - \frac{1}{2CMRR} \right)} = \frac{10^4 \left(1 + \frac{1}{2 \times 10^4} \right)}{1 + 10^4 \left(1 - \frac{1}{2 \times 10^4} \right)} = 1.000 \quad A_v = \frac{10^3 \left(1 + \frac{1}{2 \times 10^3} \right)}{1 + 10^3 \left(1 - \frac{1}{2 \times 10^3} \right)} = 1.000$$

Page 628

$$GE = FGE (A_v) \leq 5 \times 10^{-5} (1) = 5 \times 10^{-5} \quad \text{Worst case occurs for negative CMRR: } GE \cong \frac{1}{A} + \frac{1}{CMRR}$$

$$\text{If both terms make equal contributions: } A = CMRR = \frac{1}{2.5 \times 10^{-5}} = 4 \times 10^4 \text{ or } 92 \text{ dB}$$

$$\text{For other cases: } CMRR = \left(5 \times 10^{-5} - \frac{1}{A}\right)^{-1} \quad \text{or} \quad A = \left(5 \times 10^{-5} - \frac{1}{CMRR}\right)^{-1}$$

$$A = 100 \text{ dB} \quad CMRR = \left(5 \times 10^{-5} - \frac{1}{10^5}\right)^{-1} = 2.5 \times 10^4 \text{ or } 88 \text{ dB}$$

$$CMRR = 100 \text{ dB} \quad A = \left(5 \times 10^{-5} - \frac{1}{10^5}\right)^{-1} = 2.5 \times 10^4 \text{ or } 88 \text{ dB}$$

Page 630

Values taken from op - amp specification sheets (www.jaegerblalock.com or www.analog.com)

Page 631

$$(i) |V_o| \leq 50(0.002V) \rightarrow -0.100 V \leq V_o \leq +0.100 V$$

(ii) Values taken from op - amp specification sheets (www.jaegerblalock.com or www.analog.com)

Page 633

Values taken from op - amp specification sheets (www.jaegerblalock.com or www.analog.com)

Page 634

$$(i) R = 39k\Omega \parallel 1k\Omega = 975 \Omega$$

$$(ii) v_o(t) = V_{OS} + \frac{V_{OS}}{RC}t + \frac{I_{B2}}{C}t \quad 1.5mV + \frac{1.5mV}{10k\Omega(100pF)}t + \frac{100nA}{100pF}t = 15V \rightarrow t = 6.00 ms$$

Page 636

Values taken from op - amp specification sheets (www.jaegerblalock.com or www.analog.com)

Page 637

Values taken from op - amp specification sheets (www.jaegerblalock.com or www.analog.com)

Page 638

$$R_{EQ} = R_L \parallel (R_2 + R_1) \geq \frac{20V}{5mA} = 4k\Omega \quad R_1 + R_2 \geq \left(\frac{1}{4k\Omega} - \frac{1}{5k\Omega} \right)^{-1} = 20k\Omega$$

Including 5% tolerances, $R_1 + R_2 \geq 21k\Omega$ $A_v = 10 \rightarrow R_2 = 9R_1$

A few possibilities : 27 k Ω and 3 k Ω , 270 k Ω and 30 k Ω , 180 k Ω and 20 k Ω , etc.

Page 640

$$(i) A_o = 10^{\frac{100}{20}} = 10^5 \quad \omega_B = \frac{\omega_T}{A_o} = \frac{2\pi(5 \times 10^6)}{10^5} = \frac{10^7 \pi}{10^5} = 100\pi \quad f_B = \frac{100\pi}{2\pi} = 50 \text{ Hz} \quad A_v(s) = \frac{10^7 \pi}{s + 100\pi}$$

$$(ii) A_v(s) = \frac{\omega_T}{s + \frac{\omega_T}{A_o}} = \frac{2\pi \times 10^6}{s + \frac{2\pi \times 10^6}{2 \times 10^5}} = \frac{2\pi \times 10^6}{s + 10\pi}$$

Page 643

$$(i) A_o = 10^{\frac{90}{20}} = 31600 \quad f_B = \frac{f_T}{A_o} = \frac{5 \times 10^6}{31600} = 158 \text{ Hz} \quad A_v(s) = \frac{2\pi(5 \times 10^6)}{s + 2\pi(158)} = \frac{10^7 \pi}{s + 316\pi}$$

$$f_H \cong \beta f_T = 0.01(5 \text{ MHz}) = 50 \text{ kHz} \quad A_v(s) = \frac{2\pi(5 \times 10^6)}{s + 2\pi(5 \times 10^4)} = \frac{10^7 \pi}{s + 10^5 \pi}$$

$$(ii) \text{ For } \omega_H \gg \omega_B : A\beta = \frac{\omega_T}{s + \omega_B} \beta \cong \frac{\beta \omega_T}{j\omega_H} = \frac{1}{j} = -j1 \quad \text{since } \omega_H = \beta \omega_T$$

Page 645

$$(i) A_o = 10^{\frac{90}{20}} = 31600 \quad f_B = \frac{f_T}{A_o} = \frac{5 \times 10^6}{31600} = 158 \text{ Hz} \quad A_v(s) = \frac{2\pi(5 \times 10^6)}{s + 2\pi(158)} = \frac{10^7 \pi}{s + 316\pi}$$

$$f_H \cong \beta f_T = \frac{5 \text{ MHz}}{1 + 10^{\frac{50}{20}}} = 15.8 \text{ kHz} \quad A_v(s) = \frac{2\pi(5 \times 10^6)}{s + 2\pi(15.8 \times 10^3)} = \frac{10^7 \pi}{s + 3.16 \times 10^4 \pi}$$

$$(ii) f_H \cong \beta f_T = 1(5 \text{ MHz}) = 5 \text{ MHz} \quad f_H \cong \beta f_T = \frac{1}{2}(5 \text{ MHz}) = 2.5 \text{ MHz}$$

Page 647

$$A_v(0) = 50(25) = 1250 \quad |A_v(\omega_H)| = \frac{1250}{\sqrt{2}} = 884$$

$$\left[1 + \frac{\omega_H^2}{(10000\pi)^2}\right] \left[1 + \frac{\omega_H^2}{(20000\pi)^2}\right] = 2 \rightarrow (\omega_H^2)^2 + 4.935 \times 10^9 \omega_H^2 - 3.896 \times 10^{18} = 0$$

$$\omega_H^2 = 6.925 \times 10^8 \rightarrow \omega_H = 26.3 \times 10^3 \rightarrow f_H = \frac{26.3 \times 10^3}{2\pi} = 4190 \text{ Hz}$$

Page 648

$$(i) \quad A_v(0) = -100(66.7)(50) = -3.34 \times 10^5 \quad |A_v(\omega_H)| = \frac{-3.34 \times 10^5}{\sqrt{2}} = -2.36 \times 10^5$$

$$\left[1 + \frac{\omega_H^2}{(10000\pi)^2}\right] \left[1 + \frac{\omega_H^2}{(15000\pi)^2}\right] \left[1 + \frac{\omega_H^2}{(20000\pi)^2}\right] = 2$$

$$\omega_H^6 + 7.156 \times 10^9 \omega_H^4 + 1.486 \times 10^{10} \omega_H^2 - 8.562 \times 10^{27} = 0$$

$$\text{Using MATLAB, } \omega_H = 21.7 \times 10^3 \rightarrow f_H = \frac{21.7 \times 10^3}{2\pi} = 3450 \text{ Hz}$$

$$(ii) \quad A_v(0) = (-30)^3 = -2.70 \times 10^4 \quad f_H = (33.3 \text{ kHz}) \sqrt[3]{2^{\frac{1}{3}} - 1} = 17.0 \text{ kHz}$$

Page 653

$$V_M \leq \frac{SR}{\omega} = \frac{5 \times 10^5 \text{ V/s}}{2\pi(20 \text{ kHz})} = 3.98 \text{ V} \quad f_M = \frac{SR}{2\pi V_{FS}} = \frac{5 \times 10^5 \text{ V/s}}{2\pi(10 \text{ V})} = 7.96 \text{ kHz}$$

Page 657

$$A_{v1} = 1 + \frac{130 \text{ k}\Omega}{22 \text{ k}\Omega} = 6.909 \quad v_{O1} = 0.001(6.909) = 6.91 \text{ mV} \quad v_{O2} = 0.001V(6.909)^2 = 47.7 \text{ mV}$$

$$v_{O3} = 0.001(6.909)^3 = 330 \text{ mV} \quad v_{O4} = 0.001V(6.909)^4 = 2.28 \text{ V} \quad v_{O5} = 0.001V(6.909)^5 = 15.7 \text{ V}$$

$$v_{O5} > 15 \text{ V} \rightarrow v_{O5} = 15 \text{ V} \quad v_{O6} = 15V(6.909) = 104 \text{ V} \quad v_{O6} > 15 \text{ V} \rightarrow v_{O6} = 15 \text{ V}$$

CHAPTER 13

Page 671

(i) (a) At the Q-point : $\beta_F = \frac{I_C}{I_B} = \frac{1.5mA}{15\mu A} = 100$ (b) $I_S = \frac{I_C}{\exp\left(\frac{V_{BE}}{V_T}\right)} = \frac{1.5mA}{\exp\left(\frac{0.700V}{0.025V}\right)} = 1.04 fA$

(c) $R_{in} = \frac{v_{be}}{i_b} = \frac{8mV}{5\mu A} = 1.6 k\Omega$ (d) With the given applied signal, the smallest value of v_{CE} is

$v_{CE}^{\min} = 5V - 0.5mA(3.3k\Omega) = 3.35 V$ which exceeds $v_{BE} = 0.708 V$.

(ii) (a) $v_{DS} = 10 - 3300i_{DS}$

(b) Using the peak - to - peak voltage swings, $A_v = \frac{v_{ds}}{v_{gs}} = \frac{2.7 - 6.7 V}{4.0 - 3.0 V} = -4.0$.

Note that there is some distortion in this amplifier since the negative output voltage excursion is larger than the positive output change.

(c) $v_{DS}^{\min} = 2.7V$ with $v_{GS} - V_{TN} = 4 - 1 = 3V$, so the transistor has entered the triode region.

(d) Choose two points on the i - v characteristics. For example,

$$1.56mA = \frac{K_n}{2}(3.5 - V_{TN})^2 \quad \text{and} \quad 1.0mA = \frac{K_n}{2}(3.0 - V_{TN})^2.$$

Solving for K_n and V_{TN} yields $500 \frac{\mu A}{V^2}$ and 1 V respectively.

Page 673

(i) $V_{EQ} = \frac{10k\Omega}{10k\Omega + 30k\Omega} 12V = 3.00V$ $R_{EQ} = 10k\Omega \parallel 30k\Omega = 7.5k\Omega$

$$I_C = \beta_F I_B = \beta_F \frac{V_{EQ} - V_{BE}}{R_{EQ} + (\beta_F + 1)R_4} = 100 \frac{3.0V - 0.7V}{7.5k\Omega + (101)(1.5k\Omega)} = 1.45 mA$$

$$V_{CE} = 12 - 4300I_C - 1500I_E = 12 - 4300(1.45mA) - 1500\left(\frac{101}{100}\right)(1.45mA) = 3.57 V$$

(ii) $v_c(t) = V_C + v_c = (5.8 - 1.1\sin 2000\pi t) V$ $v_e(t) = V_E + 0 = 1.45mA(1.5k\Omega) = 2.2 V$

$$|i_c| = \frac{1.1V}{4.3k\Omega} = 0.256mA \quad \angle i_c = 180^\circ \quad i_c(t) = -0.26\sin 2000\pi t mA$$

(iii) $X_C = \frac{1}{\omega C} = \frac{1}{2000\pi(500\mu F)} = 0.318 \Omega$

Page 676

$$R_B = 20k\Omega \parallel 62k\Omega = 15.1 k\Omega \quad R_L = 8.2k\Omega \parallel 100k\Omega = 7.58 k\Omega$$

Page 680

$$(i) r_d = \frac{V_T}{I_D + I_S} \quad r_d = \frac{0.025V}{1fA} = 25.0 \text{ T}\Omega \quad r_d = \frac{0.025V}{50\mu A} = 500 \Omega$$

$$r_d = \frac{0.025V}{2mA} = 12.5 \Omega \quad r_d = \frac{0.025V}{3A} = 8.33 \text{ m}\Omega$$

$$(ii) r_d = \frac{0.025V}{1.5mA} = 16.7 \Omega \quad \frac{kT}{q} = \left(8.62 \times 10^{-5} \frac{V}{K}\right)(373K) = 0.0322 \text{ V} \quad r_d = \frac{0.0322V}{1.5mA} = 21.5 \Omega$$

Page 685

$$(i) g_m = 40I_C = 40(50\mu A) = 2.00 \text{ mS} \quad r_\pi = \frac{\beta_o}{g_m} = \frac{75}{2\text{mS}} = 37.5 \text{ k}\Omega$$

$$r_o = \frac{V_A + V_{CE}}{I_C} = \frac{60V + 5V}{50\mu A} = 1.30 \text{ M}\Omega \quad \mu_f = g_m r_o = 2\text{mS}(1.30 \text{ M}\Omega) = 2600$$

$$(ii) g_m = 40I_C = 40(250\mu A) = 10.0 \text{ mS} \quad r_\pi = \frac{\beta_o}{g_m} = \frac{50}{10\text{mS}} = 5.00 \text{ k}\Omega$$

$$r_o = \frac{V_A + V_{CE}}{I_C} = \frac{75V + 15V}{250\mu A} = 360 \text{ k}\Omega \quad \mu_f = g_m r_o = 10\text{mS}(360\text{k}\Omega) = 3600$$

(iii) The slope of the output characteristics is zero, so $V_A = \infty$ and $r_o = \infty$.

$$\beta_{FO} = \frac{\beta_F}{1 + \frac{V_{CE}}{V_A}} = \beta_F = \frac{I_C}{I_B} = \frac{1.5mA}{15\mu A} = 100 \quad g_m = \frac{\Delta i_C}{\Delta v_{BE}} = \frac{0.5mA}{8mV} = 62.5 \text{ mS}$$

$$\beta_o = \frac{\Delta i_C}{\Delta i_B} = \frac{500\mu A}{5\mu A} = 100 \quad r_\pi = \frac{\beta_o}{g_m} = \frac{100}{62.5\text{mS}} = 1.60 \text{ k}\Omega$$

Page 692

$$A_{vt} = -g_m R_L = -9.80\text{mS}(18\text{k}\Omega) = -176$$

Page 695

Assume the Q - point remains constant.

$$(a) R_L^{\max} = 19.8k\Omega \quad R_L^{\min} = 16.2k\Omega \quad R_E^{\max} = 3.30k\Omega \quad R_L^{\min} = 2.70k\Omega$$

$$R_{iB}^{\max} = 10.2k\Omega + 101(3.3k\Omega) = 344k\Omega \quad R_{iB}^{\min} = 10.2k\Omega + 101(2.7k\Omega) = 283k\Omega$$

$$A_v^{\min} = -\frac{9.80mS(16.2k\Omega)}{1 + 9.80mS(3.30k\Omega)} \left(\frac{104k\Omega \parallel 344k\Omega}{1k\Omega + 104k\Omega \parallel 344k\Omega} \right) = -4.70$$

$$A_v^{\max} = -\frac{9.80mS(19.8k\Omega)}{1 + 9.80mS(2.70k\Omega)} \left(\frac{104k\Omega \parallel 283k\Omega}{1k\Omega + 104k\Omega \parallel 283k\Omega} \right) = -6.98$$

$$(b) r_{\pi} = \frac{125}{9.80mS} = 12.8k\Omega \quad R_{iB} = 12.8k\Omega + 126(3.0k\Omega) = 391k\Omega$$

$$A_v = -\frac{9.80mS(18k\Omega)}{1 + 9.80mS(3.00k\Omega)} \left(\frac{104k\Omega \parallel 391k\Omega}{1k\Omega + 104k\Omega \parallel 391k\Omega} \right) = -5.73$$

$$(c) V_{CE} = 12V - 22k\Omega I_C - 13k\Omega I_E = 12V - 0.275mA \left(22k\Omega + \frac{101}{100} 13k\Omega \right) = 2.34V$$

$$g_m = 40(0.275mA) = 11.0mS \quad r_{\pi} = \frac{100}{11.0mS} = 9.09k\Omega$$

$$R_{iB} = 9.09k\Omega + 101(3.0k\Omega) = 312k\Omega \quad A_v = -\frac{11.0mS(18k\Omega)}{1 + 11.0mS(3.00k\Omega)} \left(\frac{104k\Omega \parallel 312k\Omega}{1k\Omega + 104k\Omega \parallel 312k\Omega} \right) = -5.75$$

Page 697

$$(i) R_{iB}^{\max} = 10.2k\Omega + 101(1k\Omega) = 111k\Omega \quad R_{E2} = 13k\Omega - 1k\Omega = 12k\Omega$$

$$A_v = -\frac{9.80mS(18k\Omega)}{1 + 9.80mS(1.00k\Omega)} \left(\frac{104k\Omega \parallel 111k\Omega}{1k\Omega + 104k\Omega \parallel 111k\Omega} \right) = -16.0$$

(ii) The reference to C_2 should be C_3 . $A_v = -159$ as calculated in the Ex. 13.4.

$$(iii) V_T = \left(\frac{1.38 \times 10^{-23} V}{1.602 \times 10^{-19} K} \right) (273K + 27K) = 25.84mV \quad I_S = \frac{I_C}{\exp\left(\frac{V_{BE}}{V_T}\right)} = \frac{245\mu A}{\exp\left(\frac{0.700V}{0.02584V}\right)} = 0.421fA$$

(iv) From Ex. 13.3, $R_{iB} = 313k\Omega$, and $r_{\pi} = 10.2k\Omega$.

Page 700

$$(i) R_{iC} = 320k\Omega \left[1 + \frac{100(2k\Omega)}{(1k\Omega \parallel 104k\Omega) + 10.2k\Omega + 2k\Omega} \right] = 4.85 M\Omega \quad \mu_f R_E = 3140(2k\Omega) = 6.28 M\Omega$$

$$R_{iC} < \mu_f R_E \quad R_{out} = 4.85 M\Omega \parallel 22k\Omega = 21.9 k\Omega$$

$$(ii) \lim_{R_E \rightarrow \infty} R_{iC} = \lim_{R_E \rightarrow \infty} r_o \left(1 + \frac{\beta_o R_E}{R_{th} + r_\pi + R_E} \right) = r_o \left(1 + \frac{\beta_o R_E}{R_E} \right) = (\beta_o + 1)r_o$$

Page 704

$$(i) (a) g_m = \sqrt{2K_n I_D (1 + \lambda V_{DS})} = \sqrt{2(1mA/V^2)(0.25mA)[1 + 0.02(5)]} = 1.73 mS$$

$$r_o = \frac{\frac{1}{\lambda} + V_{DS}}{I_D} = \frac{50V + 5V}{250\mu A} = 220 k\Omega \quad \mu_f = g_m r_o = 0.742mS(220k\Omega) = 163$$

$$g_m = \sqrt{2K_n I_D (1 + \lambda V_{DS})} = \sqrt{2(1mA/V^2)(5mA)[1 + 0.02(10)]} = 3.46 mS$$

$$r_o = \frac{\frac{1}{\lambda} + V_{DS}}{I_D} = \frac{50V + 10V}{5mA} = 12 k\Omega \quad \mu_f = g_m r_o = 3.46mS(12k\Omega) = 41.5$$

(b) The slope of the output characteristics is zero, so $\lambda = 0$ and $r_o = \infty$.

$$\text{For the positive change in } v_{gs}, g_m = \frac{\Delta i_D}{\Delta v_{GS}} \cong \frac{2.1V}{0.5V} = 1.3 mS$$

$$(ii) |v_{gs}| \leq 0.2(V_{GS} - V_{TN}) = 0.2\sqrt{\frac{2I_D}{K_n}} = 0.2\sqrt{\frac{2(25mA)}{2.0mA/V^2}} = 1.00 V \quad |v_{be}| \leq 0.005 V$$

Page 705

$$\eta = \frac{\gamma}{2\sqrt{V_{SB} + 2\phi_F}} = \frac{0.75}{2\sqrt{0 + 0.6}} = 0.48 \quad \eta = \frac{0.75}{2\sqrt{3 + 0.6}} = 0.20$$

Page 713

$$(i) V_{EQ} = \frac{1.5M\Omega}{1.5M\Omega + 2.2M\Omega} 12V = 4.87V \quad R_{EQ} = 1.5M\Omega \parallel 2.2M\Omega = 892k\Omega$$

Neglect λ in hand calculations of the Q-point.

$$4.87 = V_{GS} + 12000I_D \quad 4.87 = V_{GS} + 12000\left(\frac{5 \times 10^{-4}}{2}\right)(V_{GS} - 1)^2$$

$$3V_{GS}^2 - 5V_{GS} - 1.87 = 0 \rightarrow V_{GS} = 1.981V \quad I_D = 241 \mu A$$

$$V_{DS} = 12 - 22000I_D - 12000I_D = 3.81V \quad Q\text{-point} : (241 \mu A, 3.81V)$$

$$(ii) A_{v_{dB}} = 20 \log(4.50) = 13.1 dB$$

Page 714

$$V_{DS} \geq V_{GS} - V_{TH} = 1.981V - 1V = 0.981V$$

Page 717

$$V_{GS} - V_{TN} \cong \sqrt{\frac{2(241\mu A)}{2 \times 10^{-3}}} = 0.491V \quad A_v^{CS} \cong -\frac{12V}{0.491V} = -24.4 \quad M = \frac{K_{n2}}{K_{n1}} = \frac{2 \times 10^{-3}}{5 \times 10^{-4}} = 4$$

Page 720

$$R_{in}^{CS} = 680k\Omega \parallel 1.0M\Omega = 405k\Omega \quad V_{EQ} = \frac{680k\Omega}{680k\Omega + 1M\Omega} 12V = 4.86V$$

Page 725

$$\text{The gain is proportional to } R_L : R_L = 10k\Omega \parallel 220k\Omega = 9.57k\Omega \quad A_v^{CE} = -36.1 \left(\frac{9.57k\Omega}{9.540k\Omega} \right) = -36.8$$

Page 726

$$(i) \mu_f = g_m r_o = 9.56mS(225k\Omega) = 2150$$

$$(ii) v_{be} = v_i \left(\frac{R_{in}^{CE}}{R_I + R_{in}^{CE}} \right) \left(\frac{1}{1 + g_m R_E} \right) \quad v_i \leq 5mV \left(\frac{0.33k\Omega + 14.2k\Omega}{14.2k\Omega} \right) [1 + 9.56mS(0.15k\Omega)] = 12.4mV$$

$$v_o \leq 12.4mV(36.1) = 0.450V$$

$$(iv) R_{in}^{CE} = 100k\Omega \parallel 6.8k\Omega = 6.37k\Omega \quad R_{out}^{CE} = 10k\Omega \parallel 225k\Omega = 9.57k\Omega$$

$$A_v^{CE} = -g_m R_L \left(\frac{R_{in}^{CE}}{R_I + R_{in}^{CE}} \right) = -9.56mS(9.57k\Omega \parallel 220k\Omega) \left(\frac{6.37k\Omega}{0.33k\Omega + 6.37k\Omega} \right) = -83.4$$

Page 730

(i) The gain is proportional to R_L .

$$R_L = 300k\Omega \parallel R_{out}^{CS} = 300k\Omega \parallel 28.4k\Omega = 25.9k\Omega \quad A_v^{CS} = -6.85 \left(\frac{25.9k\Omega}{27.3k\Omega} \right) = -6.50$$

The corrected gain agrees more closely with the value from SPICE.

$$(ii) \mu_f = g_m r_o = 0.515mS(258k\Omega) = 133$$

$$(iii) v_{gs} = v_i \left(\frac{R_{in}^{CS}}{R_I + R_{in}^{CS}} \right) \left(\frac{1}{1 + g_m R_S} \right) \quad v_{gs} \leq 0.2(V_{GS} - V_{TN})$$

$$v_i \leq 0.2(1V) \left(\frac{10k\Omega + 1M\Omega}{1M\Omega} \right) [1 + 0.515mS(2k\Omega)] = 410 mV \quad v_o \leq 410mV(6.85) = 2.81 V$$

$$(iv) A_v^{CS} = - \left(\frac{R_{in}^{CS}}{R_I + R_{in}^{CS}} \right) \left(\frac{g_m R_L}{1 + g_m R_S} \right) = - \left(\frac{1M\Omega}{10k\Omega + 1M\Omega} \right) \left[\frac{0.515mS(30k\Omega \parallel 300k\Omega)}{1 + 0.515mS(32k\Omega)} \right] = -0.796$$

The calculation is slightly larger than the SPICE value since it neglects R_{out}^{CS} .

Page 734

$$(i) P_D = I_C V_{CE} + I_B V_{BE} = 239\mu A(3.67V) + \frac{239\mu A}{65}(0.7V) = 0.880 mW$$

$$P_S = I_C V_{CC} + I_E V_{EE} = 239\mu A(5V) + 239\mu A \left(1 + \frac{1}{65} \right) (5V) = 2.41 mW$$

$$(i) P_D = I_D V_{DS} = 250\mu A(4.5V) = 1.13 mW$$

$$P_S = I_D V_{DD} + I_S V_{SS} = 250\mu A(10V) + 250\mu A(10V) = 5.00 mW$$

Page 735

$$(a) V_M \leq \min [I_C R_C, (V_{CE} - V_{BE})] = \min [239\mu A(10k\Omega), (3.67 - 0.7)V] = 2.39 V$$

Limited by the voltage drop across R_C .

$$(b) V_M \leq \min [I_D R_D, (V_{DS} - V_{DSSAT})] = \min [250\mu A(30k\Omega), (4.50 - 1)V] = 3.50 V$$

Limited by the value of V_{DS} .

CHAPTER 14

Page 754

$$R_B = 160k\Omega \parallel 300k\Omega = 104k\Omega \quad R_E = 3.00k\Omega \quad R_L = 100k\Omega \parallel 22k\Omega = 18.0k\Omega$$

$$R_G = 1.5M\Omega \parallel 2.2M\Omega = 892k\Omega \quad R_S = 2.00k\Omega \quad R_L = 100k\Omega \parallel 22k\Omega = 18.0k\Omega$$

Page 761

$$(i) A_v^{CE} = -\frac{0.838V}{0.150} = -5.59$$

$$(ii) R_{iB} = 10.2k\Omega + 101(1.0k\Omega) = 111k\Omega$$

$$A_v^{CE} = -\frac{9.80mS(18k\Omega)}{1 + 9.80mS(1k\Omega)} \left(\frac{104k\Omega \parallel 111k\Omega}{2k\Omega + 104k\Omega \parallel 111k\Omega} \right) = -15.8 \quad R_4 = 13k\Omega - 1k\Omega = 12k\Omega$$

$$A_v^{CS} = -\frac{0.491mS(18k\Omega)}{1 + 0.491mS(1k\Omega)} \left(\frac{892k\Omega}{2k\Omega + 892k\Omega} \right) = -5.91 \quad R_4 = 12k\Omega - 1k\Omega = 11k\Omega$$

$$(iii) R_{iB} = 10.2k\Omega$$

$$A_v^{CE} = -9.80mS(18k\Omega) \left(\frac{104k\Omega \parallel 10.2k\Omega}{2k\Omega + 104k\Omega \parallel 10.2k\Omega} \right) = -145$$

$$A_v^{CS} = -0.491mS(18k\Omega) \left(\frac{892k\Omega}{2k\Omega + 892k\Omega} \right) = -8.82$$

$$(iv) V_T = \left(\frac{1.38 \times 10^{-23} V}{1.602 \times 10^{-19} K} \right) (273K + 27K) = 25.84mV \quad I_S = \frac{I_C}{\exp\left(\frac{V_{BE}}{V_T}\right)} = \frac{245\mu A}{\exp\left(\frac{0.700V}{0.02584V}\right)} = 0.421fA$$

$$(v) g_m R_L = -9.80mS(18k\Omega) = -176, A_v^{CE} \cong -\frac{18k\Omega}{3k\Omega} = -9.00$$

$$g_m R_L = -0.491mS(18k\Omega) = -8.84, A_v^{CE} \cong -\frac{18k\Omega}{2k\Omega} = -9.00$$

$$(vi) \text{ The exercise should refer to Fig. 14.2. } R_{iB} = 10.2k\Omega + 101(3.0k\Omega) = 313k\Omega$$

$$R_m^{CE} = R_B \parallel R_{iB} = 104k\Omega \parallel 313k\Omega = 78.1k\Omega \quad R_m^{CS} = R_G = 892k\Omega \quad R_m^{CE} > r_\pi$$

Page 761

$$(i) A_{vt} = \frac{2k\Omega + 892k\Omega}{892k\Omega} 0.956 = 0.958 \quad \frac{(0.491ms)R_L}{1 + (0.491ms)R_L} = 0.958 \rightarrow R_L = 46.5k\Omega$$

$$R_6 \parallel 100k\Omega = 46.5k\Omega \rightarrow R_6 = 86.9k\Omega$$

$$(ii) R_{iB} = 10.2k\Omega + 101(13k\Omega) = 1.32M\Omega \quad R_{in}^{CC} = 104k\Omega \parallel 1.32M\Omega = 96.4k\Omega$$

$$A_v^{CE} = -\frac{9.80mS(13k\Omega)}{1 + 9.80mS(13k\Omega)} \left(\frac{96.4k\Omega}{2k\Omega + 96.4k\Omega} \right) = +0.972$$

$$A_v^{CS} = -\frac{0.491mS(12k\Omega)}{1 + 0.491mS(12k\Omega)} \left(\frac{892k\Omega}{2k\Omega + 892k\Omega} \right) = +0.853$$

$$(iv) \text{BJT: } g_m R_L = 9.80mS(11.5k\Omega) = 113 \quad \text{FET: } g_m R_L = 0.491mS(10.7k\Omega) = 5.25$$

Page 767

$$v_i \leq 0.005V(1 + g_m R_L) \frac{R_I + R_B \parallel R_{iB}}{R_B \parallel R_{iB}} = 0.005V[1 + 9.8mS(11.5k\Omega)] \frac{2k\Omega + 95.4k\Omega}{95.4k\Omega} = 0.580V$$

$$v_i \leq 0.2(V_{GS} - V_{TN})(1 + g_m R_L) \frac{R_I + R_G}{R_G} = 0.2(0.982)[1 + 0.491mS(10.7k\Omega)] \frac{2k\Omega + 892k\Omega}{892k\Omega} = 1.23V$$

Page 769

$$R_{out}^{CD} = R_6 \parallel \frac{1}{g_m} \quad 12k\Omega \parallel \frac{1}{g_m} = 120\Omega \rightarrow g_m = 8.25mS \quad 8.25mS = \sqrt{2(500\mu A/V^2)} I_D \rightarrow I_D = 68.1mA$$

$$g_m = \frac{2I_D}{V_{GS} - V_{TN}} \quad V_{GS} - V_{TN} = \frac{2(68.1mA)}{8.25mS} = 16.5V$$

If one neglects R_6 , $I_D = 69.4mA$ and $V_{GS} - V_{TN} = 16.8V$

Page 774

$$\text{BJT: } v_i \leq 0.005V(1 + g_m R_I) \frac{R_I + R_6}{R_6} = 0.005V[1 + 9.8mS(2k\Omega)] \left(\frac{2k\Omega + 13k\Omega}{13k\Omega} \right) = 119mV$$

$$\text{Neglecting } R_6, v_i \leq 0.005V(1 + g_m R_I) = 0.005V[1 + 9.8mS(2k\Omega)] = 103mV$$

$$\text{FET: } v_i \leq 0.2(V_{GS} - V_{TN})(1 + g_m R_I) \frac{R_I + R_6}{R_6} = 0.2(0.982)[1 + 0.491mS(2k\Omega)] \frac{2k\Omega + 12k\Omega}{12k\Omega} = 454mV$$

$$\text{Neglecting } R_6, v_i \leq 0.2(V_{GS} - V_{TN})(1 + g_m R_I) = 0.2(0.982)[1 + 0.491mS(2k\Omega)] = 389mV$$

Page 775

$$R_{iC} = r_o \left[1 + \frac{\beta_o R_{th}}{R_{th} + r_\pi} \right] = 219k\Omega \left[1 + \frac{100(1.73k\Omega)}{1.73k\Omega + 10.2k\Omega} \right] = 3.40 M\Omega$$

Or more approximately, $R_{iC} = r_o [1 + g_m R_{th}] = 219k\Omega [1 + 9.8mS(1.73k\Omega)] = 3.93 M\Omega$

$$R_{iD} = r_o [1 + g_m R_{th}] = 223k\Omega [1 + 0.491(1.71k\Omega)] = 4.10 M\Omega$$

Page 778

$$(i) A_v^{CB} = g_m R_L \frac{\frac{R_6 \left(\frac{1}{g_m} \right)}{R_6 + \frac{1}{g_m}}}{R_I + \frac{R_6 \left(\frac{1}{g_m} \right)}{R_6 + \frac{1}{g_m}}} = g_m R_L \frac{\frac{R_6}{R_6 + \frac{1}{g_m}}}{g_m R_I + \frac{R_6}{R_6 + \frac{1}{g_m}}} = g_m R_L \frac{R_6}{R_6 (1 + g_m R_I) + R_I}$$

$$A_v^{CB} = g_m R_L \frac{R_6}{R_6 + R_I} \frac{1}{1 + \frac{g_m R_I R_6}{R_6 + R_I}} = \frac{g_m R_L}{1 + g_m R_{th}} \left(\frac{R_6}{R_6 + R_I} \right)$$

(ii) The voltage gains are proportional to the load resistance

$$A_v^{CE} = +8.48 \left(\frac{22k\Omega}{18k\Omega} \right) = +10.4 \quad A_v^{CG} = +4.12 \left(\frac{22k\Omega}{18k\Omega} \right) = +5.02$$

$$(iii) \text{CB: } A_v^{CB} \leq g_m R_L = 176 \quad A_v^{CB} \cong \frac{R_L}{R_{th}} = \frac{R_L}{R_I \parallel R_6} = \frac{18k\Omega}{1.73k\Omega} = 10.4 \quad 8.48 < 10.4 \ll 176$$

$$\text{CG: } A_v^{CG} \leq g_m R_L = 8.84 \quad A_v^{CB} \cong \frac{R_L}{R_{th}} = \frac{R_L}{R_I \parallel R_6} = \frac{18k\Omega}{1.71k\Omega} = 10.5 \quad 4.11 < 8.84 < 10.5$$

Page 786

(i) Since we need high gain, the emitter should be bypassed, and $R_{in}^{CE} = R_B \parallel r_\pi = 250k\Omega$.

If we choose $R_B \cong r_\pi$, $I_C = \frac{\beta_o}{40r_\pi} \cong \frac{100}{40(500k\Omega)} = 5 \mu A$

$$(ii) R_{in}^{CG} \cong \frac{1}{g_m} \quad I_C \cong \frac{1}{40(2k\Omega)} = 12.5 \mu A$$

Page 790

(i) Common – Emitter :

$$C_1 \gg \frac{1}{2\pi(250\text{Hz})(1\text{k}\Omega + 77.9\text{k}\Omega)} = 8.07\text{nF} \quad \text{Choose } C_1 = 82\text{ nF} = 0.082\ \mu\text{F}$$

$$C_2 \gg \frac{1}{2\pi(250\text{Hz})\left[10\text{k}\Omega \parallel \left(3\text{k}\Omega + \frac{1}{9.80\text{mS}}\right)\right]} = 0.269\mu\text{F} \quad \text{Choose } C_2 = 2.7\ \mu\text{F}$$

$$C_3 \gg \frac{1}{2\pi(250\text{Hz})(21.9\text{k}\Omega + 82\text{k}\Omega)} = 6.13\text{nF} \quad \text{Choose } C_{31} = 68\text{ nF} = 0.068\ \mu\text{F}$$

Common – Source :

$$C_1 \gg \frac{1}{2\pi(250\text{Hz})(1\text{k}\Omega + 892\text{k}\Omega)} = 713\text{pF} \quad \text{Choose } C_1 = 8200\text{ pF}$$

$$C_2 \gg \frac{1}{2\pi(250\text{Hz})\left[10\text{k}\Omega \parallel \left(2\text{k}\Omega + \frac{1}{0.491\text{mS}}\right)\right]} = 0.221\mu\text{F} \quad \text{Choose } C_2 = 2.2\ \mu\text{F}$$

$$C_3 \gg \frac{1}{2\pi(250\text{Hz})(21.5\text{k}\Omega + 82\text{k}\Omega)} = 6.15\text{nF} \quad \text{Choose } C_3 = 68\text{ nF} = 0.068\ \mu\text{F}$$

Page 793

Common – Collector :

$$C_1 \gg \frac{1}{2\pi(250\text{Hz})(1\text{k}\Omega + 95.5\text{k}\Omega)} = 6.60\text{nF} \quad \text{Choose } C_1 = 68\text{ nF} = 0.068\ \mu\text{F}$$

$$C_3 \gg \frac{1}{2\pi(250\text{Hz})(120\Omega + 82\text{k}\Omega)} = 7.75\text{nF} \quad \text{Choose } C_3 = 82\text{ nF} = 0.082\ \mu\text{F}$$

Common – Drain :

$$C_1 \gg \frac{1}{2\pi(250\text{Hz})(1\text{k}\Omega + 892\text{k}\Omega)} = 713\text{pF} \quad \text{Choose } C_1 = 8200\text{ pF}$$

$$C_3 \gg \frac{1}{2\pi(250\text{Hz})(1.74\text{k}\Omega + 82\text{k}\Omega)} = 7.60\text{nF} \quad \text{Choose } C_3 = 82\text{ nF} = 0.082\ \mu\text{F}$$

Page 796

Common – Base :

$$C_1 \gg \frac{1}{2\pi(250\text{Hz})(1\text{k}\Omega + 0.1\text{k}\Omega)} = 0.579\mu\text{F} \quad \text{Choose } C_1 = 6.8 \mu\text{F}$$

$$C_2 \gg \frac{1}{2\pi(250\text{Hz})\left(160\text{k}\Omega \parallel 300\text{k}\Omega \parallel \left[10.2\text{k}\Omega + 101(13\text{k}\Omega \parallel 1\text{k}\Omega)\right]\right)} = 12.2\text{nF} \quad \text{Choose } C_2 = 0.12 \mu\text{F}$$

$$C_3 \gg \frac{1}{2\pi(250\text{Hz})(21.9\text{k}\Omega + 82\text{k}\Omega)} = 6.13\text{nF} \quad \text{Choose } C_3 = 0.068 \mu\text{F}$$

Common – Gate :

$$C_1 \gg \frac{1}{2\pi(250\text{Hz})(1\text{k}\Omega + 1.74\text{k}\Omega)} = 0.232\mu\text{F} \quad \text{Choose } C_1 = 2.2 \mu\text{F}$$

$$C_2 \gg \frac{1}{2\pi(250\text{Hz})(1.5\text{M}\Omega \parallel 2.2\text{M}\Omega)} = 714\text{pF} \quad \text{Choose } C_2 = 8200\text{pF}$$

$$C_3 \gg \frac{1}{2\pi(250\text{Hz})(20.9\text{k}\Omega + 82\text{k}\Omega)} = 6.19\text{nF} \quad \text{Choose } C_3 = 0.068 \mu\text{F}$$

Page 797

(a) Common – Source :

$$C_2 = \frac{1}{2\pi(1000\text{Hz})\left[10\text{k}\Omega \parallel \left(2\text{k}\Omega + \frac{1}{0.491\text{mS}}\right)\right]} = 55.3\text{nF} \quad \text{Choose } C_2 = 0.056 \mu\text{F}$$

(b) Common – Collector :

$$C_3 \gg \frac{1}{2\pi(2000\text{Hz})(120\Omega + 100\text{k}\Omega)} = 795\text{pF} \quad \text{Choose } C_3 = 820\text{pF}$$

(c) Common – Gate :

$$C_1 \gg \frac{1}{2\pi(1000\text{Hz})(2\text{k}\Omega + 1.74\text{k}\Omega)} = 42.6\text{nF} \quad \text{Choose } C_1 = 0.042 \mu\text{F}$$

Page 801

$$(i) 20V = V_{GS} + 3600I_D \quad 20 = V_{GS} + 3600 \frac{0.020}{2} (V_{GS} - 1.5)^2 \rightarrow V_{GS} = 2.203V \quad I_D = 4.94 \text{ mA}$$

$$V_{DS} = 5 - (-V_{GS}) = 7.20 \text{ V} \quad \text{Q-point: } (4.94 \text{ mA}, 7.20 \text{ V}) \quad R_{in} = R_G = 22 \text{ M}\Omega$$

$$A_v^{CD} = \frac{g_m R_L}{1 + g_m R_L} \quad g_m = \frac{2(4.94 \text{ mA})}{(2.20 - 1.50)V} = 14.2 \text{ mS} \quad R_L = 3600\Omega \parallel 3000\Omega = 1630\Omega \quad A_v^{CD} = 0.959$$

$$(ii) R_{out}^{CD} = 3.6k\Omega \parallel \frac{1}{g_m} = 3.6k\Omega \parallel \frac{1}{0.0142} = 69.1 \Omega \quad v_{gs} \leq 0.2(2.20 - 1.50) \left[1 + 0.0142(1630) \right] = 3.38 \text{ V}$$

$$(iii) r_o = \frac{1}{\lambda} + V_{DS} = \frac{1}{0.015} + 5 + 2.21 = 14.8k\Omega \quad R_L = 3600\Omega \parallel 3000\Omega \parallel 14.8k\Omega = 1470\Omega \quad A_v^{CD} = 0.954$$

$$(iv) \frac{W}{L} = \frac{K_n}{K'_n} = \frac{2 \times 10^{-2}}{5 \times 10^{-5}} = \frac{400}{1}$$

Page 802

$$A = \frac{g_m R_S}{1 + g_m R_S} \quad g_m = \frac{2(4.94 \text{ mA})}{(2.20 - 1.50)V} = 14.2 \text{ mS} \quad R_S = 3600\Omega \quad A_v^{CD} = 0.981 \quad R_{in} = R_G = 22 \text{ M}\Omega$$

$$R_{out}^{CD} = 3.6k\Omega \parallel \frac{1}{g_m} = 3.6k\Omega \parallel \frac{1}{0.0142} = 69.1 \Omega \quad A_v^{CD} = A \frac{3000\Omega}{69.1\Omega + 3000\Omega} = 0.959$$

Page 805

(i) Reverse the direction of the arrow on the emitter of the transistor as well as the values of V_{EE} and V_{CC} .

$$(ii) R_{out}^{CD} = R_E \parallel \frac{1}{g_m} = 13k\Omega \parallel \frac{1}{40(331\mu A)} = 75.1 \Omega \quad A_v^{CB} = \frac{75.1\Omega}{75\Omega + 75.1\Omega} (13.2 \text{ mS})(7.58k\Omega) = 50.1$$

(iii) For $v_{CB} \geq 0$, we require $v_c \geq 0$. $V_C = 5 - I_C R_C = 2.29 \text{ V} \quad \therefore |v_c| \leq 2.29 \text{ V}$

$$v_o \leq 5mV(g_m R_L) = 5mV(13.2 \text{ mS})(7580\Omega) = 0.500 \text{ V}$$

$$(iv) R_E = 75\Omega \left[1 + 40(7.5 - 0.7) \right] = 20.5 \text{ k}\Omega \text{ (a standard 1% value)} \quad I_C \cong \frac{6.8V}{20.5k\Omega} = 332 \mu A$$

$$50 = 40(332\mu A)R_L \frac{75}{75 + 75} \rightarrow R_L = 7.53k\Omega \rightarrow R_C = 8.14 \text{ k}\Omega \rightarrow 8.06 \text{ k}\Omega \text{ (a standard 1% value)}$$

Page 806

$$(i) \text{ 5\% tolerances } I_C^{\max} \cong \frac{V_{EE}^{\max} - 0.7V}{R_E^{\min}} = \frac{5(1.05) - 0.7V}{13k\Omega(0.95)} = 368\mu A$$

$$V_C^{\min} = V_{CC}^{\min} - I_C^{\max} R_C^{\max} = 5V(0.95) - 368\mu A(8.2k\Omega)(1.05) = 1.58 V \quad 1.58 \geq 0, \text{ so active region is ok.}$$

$$10\% \text{ tolerances } I_C^{\max} \cong \frac{V_{EE}^{\max} - 0.7V}{R_E^{\min}} = \frac{5(1.1) - 0.7V}{13k\Omega(0.9)} = 410\mu A$$

$$V_C^{\min} = V_{CC}^{\min} - I_C^{\max} R_C^{\max} = 5V(0.90) - 410\mu A(8.2k\Omega)(1.1) = 0.802 V \quad 0.802 \geq 0, \text{ so active region is ok.}$$

$$(ii) A = g_m R_C = (13.2mS)(8200\Omega) = 108 \quad R_{out}^{CB} = 8.2k\Omega \quad R_{in}^{CB} = 75\Omega$$

$$A_v^{CG} = \frac{R_{in}^{CB}}{75\Omega + R_{in}^{CB}} A \frac{100k\Omega}{R_{out}^{CB} + 100k\Omega} = \frac{75\Omega}{75\Omega + 75\Omega} (108) \left(\frac{100k\Omega}{8200 + 100k\Omega} \right) = 49.9$$

Page 811

$$(ii) r_o \cong r_o = \frac{1}{\lambda I_D} = \frac{1}{0.015(2 \times 10^{-4})} = 333k\Omega$$

$$\text{or more exactly } V_{DS} = 25 - 10^5 I_D - 9.1 \times 10^3 I_D = 25 - 1.09 \times 10^5 (0.2mA) = 3.18 V$$

$$r_o = \frac{\frac{1}{\lambda} + V_{DS}}{I_D} = \frac{\frac{1}{0.015} + 3.18}{2 \times 10^{-4}} = 349k\Omega \quad R_L = 100k\Omega \parallel 100k\Omega \parallel 349k\Omega = 43.7k\Omega$$

$$A_v^{CS} = -(g_m R_L) \frac{R_{in}}{R_L + R_{in}} = -\frac{2(0.2mA)}{0.2V} (43.7k\Omega) \left(\frac{75\Omega}{75\Omega + 75\Omega} \right) = -43.7$$

$$(iii) I_D = \frac{0.01}{2} (0.25)^2 = 0.3125mA \quad V_{GS} - V_{TN} = 0.25V \quad V_{GS} = 0.25V - 2 = -1.75V$$

$$R_S = \frac{-V_{GS}}{I_D} = \frac{1.75V}{0.3125mA} = 5.60k\Omega \rightarrow 5.6k\Omega \quad R_L = 2 \frac{A_v}{g_m} = \frac{50(0.25V)}{0.3125mA} = 40k\Omega \quad R_D \parallel 100k\Omega = 40k\Omega$$

$$R_D = 66.7k\Omega \rightarrow 68k\Omega \quad C_1 \text{ remains unchanged.}$$

$$C_2 \gg \frac{1}{10^6 \pi \left(5.6k\Omega \parallel \frac{1}{2.5mS} \right)} = 0.853nF \rightarrow \text{Choose } C_2 = 8200pF$$

$$C_3 \gg \frac{1}{10^6 \pi (68k\Omega + 100k\Omega)} = 1.90pF \rightarrow \text{Choose } C_3 = 20pF$$

$$(iv) A = -g_m R_D = -(2mS)(100k\Omega) = -200 \quad R_{out} = 100k\Omega \quad R_{in} = 75\Omega$$

$$A_v^{CG} = \frac{R_{in}}{75\Omega + R_{in}} A \frac{100k\Omega}{R_{out} + 100k\Omega} = \frac{75\Omega}{75\Omega + 75\Omega} (-200) \left(\frac{100k\Omega}{100k\Omega + 100k\Omega} \right) = -50.0$$

Page 813

$$(i) M_1: I_D = \frac{K_n}{2}(V_{GS} - V_{TN})^2 \quad V_{GS} = -R_{S1}I_D \quad I_D = \frac{0.01}{2}(-200I_D + 2)^2 \rightarrow I_D = 5.00mA$$

$$V_{DS} = 15 - 5mA(820\Omega) = 10.9V$$

$$g_m = \sqrt{2K_n I_D} = \sqrt{2(0.01)(0.005)} = 10.0mS \quad r_o = \frac{1 + \lambda V_{DS}}{\lambda I_D} = \frac{1 + 0.02(10.9)}{0.02(5mA)} = 12.2k\Omega$$

$$Q_2: V_{EQ} = \frac{22k\Omega}{22k\Omega + 78k\Omega}(15V) = 3.30V \quad R_{EQ} = 22k\Omega \parallel 78k\Omega = 17.2k\Omega$$

$$I_C = 150 \frac{3.30 - 0.7}{17.2k\Omega + 151(1.6k\Omega)} = 1.52mA \quad V_{CE} = 15 - 1.52mA \left(4.7k\Omega + \frac{151}{150} 1.6k\Omega \right) = 5.41V$$

$$g_m = 40(1.52mA) = 60.8mS \quad r_\pi = \frac{150}{60.8mS} = 2.47k\Omega \quad r_o = \frac{80 + 5.41}{1.52mA} = 56.2k\Omega$$

$$Q_3: V_{EQ} = \frac{120k\Omega}{120k\Omega + 91k\Omega}(15V) = 8.53V \quad R_{EQ} = 120k\Omega \parallel 91k\Omega = 51.8k\Omega$$

$$I_C = 80 \frac{8.53 - 0.7}{51.8k\Omega + 81(3.3k\Omega)} = 1.96mA \quad V_{CE} = 15 - 1.96mA \left(\frac{81}{80} 3.3k\Omega \right) = 8.45V$$

$$g_m = 40(1.96mA) = 78.4mS \quad r_\pi = \frac{80}{78.4mS} = 1.02k\Omega \quad r_o = \frac{60 + 8.45}{1.96mA} = 34.9k\Omega$$

(ii) A typical op - amp gain is at least 10,000 which exceeds the amplification factor of a single transistor.

Page 815

$$(i) R_{L1} = 478\Omega \parallel 12.2k\Omega = 460\Omega \quad R_{L2} = 3.53k\Omega \parallel 54.2k\Omega = 3.31k\Omega \quad R_{L3} = 232\Omega \parallel 34.4k\Omega = 230\Omega$$

$$A_v = -10mS(460\Omega)(-62.8mS)(3.31k\Omega) \left[\frac{79.6mS(230\Omega)}{1 + 79.6mS(230\Omega)} \right] \left(\frac{1M\Omega}{10k\Omega + 1M\Omega} \right) = 898 \quad 20 \log(898) = 59.1dB$$

$$(ii) A_v \cong \left(-\frac{V_{DD}}{V_{GS} - V_{TN}} \right) (-10V_{CC})(1) = -\frac{15}{1}(-10)(15)(1) = 2250$$

$$(iii) A_v = -10mS(2.39k\Omega)(-62.8mS)(19.8k\Omega)(0.95)(0.99) = 28000$$

Page 820

$$(i) R_{out} = 3300 \left\| \left(\frac{1}{0.0796S} + \frac{3990}{90.1} \right) \right\| = 55.9\Omega$$

(ii) Note that these are obtained from SPICE.

$$(iii) A_{v1} = -g_m R_{L1} = -\sqrt{2(0.01)(0.001)}(3k\Omega \parallel 17.2k\Omega \parallel 2.39k\Omega) = 5.52$$

$$A_v = -5.52(-222)(3.31k\Omega)(0.95)(0.99) = 1150$$

CHAPTER 15

Page 842

$$(i) I_C = \alpha_F I_E = \frac{60}{61} \left[\frac{15 - 0.7}{2(75k\Omega)} \right] = 93.8 \mu A \quad V_{CE} = 15 - 93.8\mu A(75k\Omega) - (-0.7V) = 8.67 V$$

$$(ii) I_C = \alpha_F I_E = \frac{60}{61} \left[\frac{15 - V_{BE}}{2(75k\Omega)} \right] \quad \text{and} \quad V_{BE} = 0.025V \ln \left(\frac{I_C}{0.5 \times 10^{-15} A} \right) \rightarrow I_C = 94.7 \mu A$$

Page 844

$$v_{id} = v_1 - v_2 = 1.01 - 0.990 = 0.020 V \quad v_{ic} = \frac{v_1 + v_2}{2} = \frac{1.01 + 0.99}{2} = 01.00 V$$

$$v_{id} = v_1 - v_2 = 4.995 - 5.005 = -0.010 V \quad v_{ic} = \frac{v_1 + v_2}{2} = \frac{4.995 + 5.005}{2} = 5.00 V$$

$$v_{od} = A_{dd}v_{id} + A_{cd}v_{ic} \quad v_{oc} = A_{dc}v_{id} + A_{cc}v_{ic}$$

$$\begin{bmatrix} 2.20 \\ 0 \end{bmatrix} = \begin{bmatrix} A_{dd} & A_{cd} \\ A_{dc} & A_{cc} \end{bmatrix} \begin{bmatrix} 0.02 & 1.00 \\ -0.01 & 5.00 \end{bmatrix} \rightarrow \begin{bmatrix} A_{dd} & A_{cd} \\ A_{dc} & A_{cc} \end{bmatrix} = \begin{bmatrix} 100 & 0.20 \\ 0.100 & 1.00 \end{bmatrix}$$

Page 848

Differential output : $A_{dm} = A_{dd} = -20V_{CC} = -300 \quad A_{cm} = 0 \quad CMRR = \infty$

Single - ended output : $A_{dm} = \frac{A_{dd}}{2} = +10V_{CC} = 150 \quad CMRR = 20V_{EE} = 300 \quad A_{cm} = -\frac{150}{300} = -0.5$

Page 851

$$V_{IC} = 15V \left[\frac{1 - \frac{100}{101} \left(\frac{R_C}{2R_C} \right) \frac{15 - 0.7}{15}}{1 + \frac{100}{101} \left(\frac{R_C}{2R_C} \right)} \right] = 5.30 V$$

Page 853

$$I_{DC} = I_{SS} - \frac{V_O}{R_{SS}} = 100\mu A - \frac{15V}{750k\Omega} = 80 \mu A$$

Page 855

$$I_D = \frac{I_{SS}}{2} = 100 \mu A \quad V_{DS} = 12 - I_D R_D + V_{GS} = 12 - 100 \mu A (62 k\Omega) + V_{GS} = 5.8 V + V_{GS}$$

$$V_{GS} = V_{TN} + \sqrt{\frac{2I_D}{K_n}} = V_{TN} + 0.2 V \quad V_{TN} = 1 + 0.75 \left(\sqrt{V_{SB} + 0.6} - \sqrt{0.6} \right) \quad V_{SB} = -V_{GS} - (-12 V)$$

$$V_{SB} = 11.8 - V_{TN} \quad V_{TN} = 1 + 0.75 \left(\sqrt{12.4 - V_{TN}} - \sqrt{0.6} \right) \rightarrow V_{TN} = 2.75 V \quad V_{DS} = 8.75 V$$

Page 858

$$R_{od} = 2r_o \cong 2 \frac{V_A}{I_C} = 2 \frac{60 V}{37.5 \mu A} = 3.20 M\Omega \quad R_{oc} \cong 2\mu_f R_{EE} = 2(40)(60)(1 M\Omega) = 4.80 G\Omega$$

$$i_{dm} = g_m v_{dm} = 40(37.5 \mu A) v_{dm} = 1.5 \times 10^{-3} v_{dm} \quad i_{cm} \cong \frac{v_{cm}}{2R_{EE}} = \frac{v_{cm}}{2 M\Omega} = 5.00 \times 10^{-7} v_{cm}$$

Page 863

$$I_{C1} = I_{C2} = \frac{100 \left(\frac{150 \mu A}{2} \right)}{101} = 74.3 \mu A \quad I_{C3} = \frac{15 V}{20 k\Omega} = 750 \mu A \quad V_{CE3} = 15 - 0 = 0 V$$

$$V_{CE1} = 15 - 74.3 \mu A (10 k\Omega) - (-0.7) = 15.0 V \quad V_{CE2} = 15 - (74.3 \mu A - 7.5 \mu A)(10 k\Omega) - (-0.7) = 15.0 V$$

$$V_{EB3} = (74.3 \mu A - 7.5 \mu A)(10 k\Omega) = 0.668 V \quad I_{S3} = \frac{750 \mu A}{\exp\left(\frac{0.668 V}{0.025}\right)} = 1.87 \times 10^{-15} A$$

Page 865

$$(i) A_{dm}^{\max} = 560 (15) = 8400$$

$$(ii) I_{C1} \leq 50(1 \mu A) = 50 \mu A \quad A_{dm} = \frac{8400}{1 + \frac{28 \left(\frac{500 \mu A}{50 \mu A} \right)}{100}} = 2210$$

$$(iii) I_{C1} \leq 50(1 \mu A) = 50 \mu A \quad A_{dm} = \frac{8400}{1 + \frac{28 \left(\frac{5 mA}{50 \mu A} \right)}{100}} = 290$$

$$(iv) A_{dm}^{\max} = 560 (1.5) = 840$$

$$(v) R_{in} = 2r_{\pi} = 2 \frac{50}{40(50 \mu A)} = 50 k\Omega \quad R_{out} \cong \frac{15 V}{0.5 mA} = 30 k\Omega$$

$$R_{in} = 2r_{\pi} = 2 \frac{50}{40(50 \mu A)} = 50 k\Omega \quad R_{out} \cong \frac{15 V}{5 mA} = 3.0 k\Omega$$

Page 866

$$CMRR \cong g_{m2} R_1 = 40 (50 \mu A)(750 k\Omega) = 1500 \quad CMRR_{dB} = 20 \log(1500) = 63.5 \text{ dB}$$

Page 868

$$(i) A_{dm} = \frac{g_{m2}}{2} \left(\frac{R_C r_{\pi 3}}{R_C + r_{\pi 3}} \right) (g_{m3} r_{o3}) = \frac{40}{2} \left(\frac{I_{C2} R_C r_{\pi 3}}{R_C + r_{\pi 3}} \right) (40 I_{C3} r_{o3}) \cong 800 \left(\frac{0.7 r_{\pi 3}}{R_C + r_{\pi 3}} \right) (V_{A3}) = \frac{560 V_{A3}}{1 + \frac{R_C}{r_{\pi 3}}}$$

$$A_{dm} = \frac{560 V_{A3}}{1 + \frac{40 I_{C3} R_C}{\beta_{o3}}} = \frac{560 V_{A3}}{1 + \frac{40 I_{C2} R_C}{\beta_{o3}} \left(\frac{I_{C3}}{I_{C2}} \right)} = \frac{560 V_{A3}}{1 + \frac{40(0.7)}{\beta_{o3}} \left(\frac{I_{C3}}{I_{C2}} \right)} = \frac{560 V_{A3}}{1 + \frac{28}{\beta_{o3}} \left(\frac{I_{C3}}{I_{C2}} \right)}$$

$$(ii) A_{dm}^{\max} = 560 (75) = 42000 \quad I_{C1} \leq 50(1 \mu A) = 50 \mu A$$

$$A_{dm} = \frac{42000}{1 + \frac{28}{100} \left(\frac{500 \mu A}{50 \mu A} \right)} = 11000 \quad A_{dm} = \frac{42000}{1 + \frac{28}{100} \left(\frac{5 mA}{50 \mu A} \right)} = 1450$$

$$(iii) R_{in} = 2r_{\pi} = 2 \frac{50}{40(50 \mu A)} = 50 \text{ k}\Omega \quad R_{out} \cong r_{o3} = \frac{75V + 15V}{0.5 mA} = 180 \text{ k}\Omega$$

$$R_{in} = 2r_{\pi} = 2 \frac{50}{40(50 \mu A)} = 50 \text{ k}\Omega \quad R_{out} \cong \frac{90V}{5 mA} = 18.0 \text{ k}\Omega$$

Page 871

$$A_{v1} = -3.50 \quad A_{v2} = -22 mS(150 k\Omega \parallel 162 k\Omega \parallel 203 k\Omega) = -1238$$

$$A_{v3} = \frac{0.198 S(2 k\Omega \parallel 18 k\Omega)}{1 + 0.198 S(2 k\Omega \parallel 18 k\Omega)} = 0.9971 \quad A_{dm} = -3.50(-1238)(0.9971) = 4320$$

$$R_{in} = 2r_{\pi} = 2 \frac{100}{40(49.5 \mu A)} = 101 \text{ k}\Omega \quad R_{out} \cong \frac{1}{g_{m4}} + \frac{r_{o3} \parallel R_2}{\beta_{o4} + 1} = \frac{1}{40(4.95 mA)} + \frac{162 k\Omega \parallel 150 k\Omega}{101} = 776 \Omega$$

$$P \cong (I_1 + I_2 + I_3)(V_{CC} + V_{EE}) = (100 + 500 + 5000) \mu A(30V) = 168 \text{ mW}$$

$$(i) I_C = 50\mu A \left(\frac{150}{151} \right) = 49.7\mu A \quad I_{C3} = 500\mu A + \frac{5mA}{151} = 533\mu A \quad R_C = \frac{0.7V}{\left(49.7 - \frac{533}{150} \right)\mu A} = 15.2k\Omega$$

$$r_{\pi 3} = \frac{150}{40(533\mu A)} = 7.04 k\Omega \quad A_{v2} = -20(49.7\mu A)(15.2k\Omega \parallel 7.04k\Omega) = -4.68$$

$$I_{C4} = \frac{150}{151} 5mA = 4.97mA \quad r_{\pi 4} = \frac{150}{40(4.97mA)} = 755 \Omega \quad r_{o3} = \frac{75 + 14.3}{533\mu A} = 168 k\Omega$$

$$A_{v2} = -40(533\mu A) \left[168k\Omega \parallel 755 + 151(2k\Omega) \right] = -2304$$

$$g_{m4} = 40(4.97mA) = 0.199S \quad A_{v3} = \frac{0.199S(2k\Omega)}{1 + 0.199S(2k\Omega)} = 0.998$$

$$A_{dm} = -4.78(-2304)(0.998) = 11000$$

$$R_{id} = 2r_{\pi 1} = 2 \frac{150}{40(49.7\mu A)} = 151 k\Omega \quad R_{out} \cong \frac{1}{g_{m4}} + \frac{r_{o3} \parallel R_2}{\beta_{o4} + 1} = \frac{1}{40(4.95mA)} + \frac{168k\Omega}{151} = 1.12 k\Omega$$

CMRR is set by the input stage and doesn't change since the bias current is the same.

$$(ii) A_{v2} = -22mS(117k\Omega \parallel 203k\Omega) = -1630 \quad r_{o3} = \frac{50 + 14.3}{550\mu A} = 117 k\Omega$$

$$A_{dm} = -3.50(-1630)(0.998) = 5700 \quad R_{out} \cong \frac{1}{g_{m4}} + \frac{r_{o3} \parallel R_2}{\beta_{o4} + 1} = \frac{1}{40(4.95mA)} + \frac{117k\Omega}{101} = 1.16 k\Omega$$

CMRR and input resistance are set by the input stage and don't change.

$$(iii) A_v = \frac{A_{dm}}{1 + A_{dm}} = \frac{6920}{6921} = 0.99986 \quad R_{out} = \frac{R_o}{1 + A_{dm}} = \frac{1.62k\Omega}{1 + 6920} = 0.234 \Omega$$

$$R_{in} = R_{id}(1 + A_{dm}) = 101k\Omega(6921) = 699 M\Omega$$

Page 873

$$(i) V_{GS3} = 1 + \sqrt{\frac{2(500\mu A)}{2.5mA}} = 1.63 V \quad R_D = \frac{1.63V}{100\mu A} = 16.3 k\Omega$$

$$A_{v1} = -\frac{1}{2} \sqrt{2(0.005)(100\mu A)(16.3k\Omega)} = -8.16$$

$$A_{v2} = -g_{m3}r_{o3} = -\sqrt{2(0.0025)(0.0005)} \left(\frac{1}{0.01(0.5mA)} \right) = -316$$

$$g_{m4} = \sqrt{2(0.005mA)(0.005mA)} = 7.07mS \quad A_{v3} = \frac{7.07mS(2k\Omega)}{1 + 7.07mS(2k\Omega)} = 0.934$$

$$A_{dm} = -8.16(-316)(0.934) = 2410 \quad R_{id} = \infty \quad R_o = \frac{1}{g_{m4}} = \frac{1}{7.07mS} = 141 \Omega$$

$$CMRR = g_m R_1 = 1.00mS(375k\Omega) = 375 \text{ or } 51.5 \text{ dB}$$

$$(ii) P \cong (I_1 + I_2 + I_3)(V_{DD} + V_{SS}) = (5.7mA)(24V) = 137 \text{ mW}$$

Page 879

$$(i) V_{GS1} + V_{SG2} = 0.5mA(4.4k\Omega) = 2.2 V \text{ Since the device parameters are the same,}$$

$$V_{GS1} = V_{SG2} = 1.1 V \quad I_D = \frac{0.025}{2}(1.1-1)^2 = 125 \mu A$$

$$(ii) \text{ Since the device parameters are the same, } V_{BE1} = V_{EB2} = \frac{0.5mA(2.4k\Omega)}{2} = 0.6 V$$

$$I_C = (10^{-14} A) \exp\left(\frac{0.6}{0.025}\right) = 265 \mu A$$

Page 883

$$A_{v1} = \frac{v_d}{v_g} = -g_m n^2 R_L = -(50mA/V^2)(2V-1V)(10)^2(8\Omega) = -40.0$$

$$A_{vo} = A_{v1} \frac{1}{n} = -\frac{40.0}{10} = -4.00 \quad |v_g| \leq 0.2(2-1)V = 0.200 V \quad |v_d| \leq 0.2V(40) = 8.00 V$$

$$|v_o| \leq \frac{8V}{10} = 0.800 V$$

Page 890

$$(i) R_{bb} \rightarrow 0 \quad R_{out} = 432k\Omega \left[1 + \frac{150(18.4k\Omega)}{18.8k\Omega + 18.4k\Omega} \right] = 32.5 M\Omega$$

$$(ii) V_{EQ} = -15V \frac{270k\Omega}{110k\Omega + 270k\Omega} = -10.66 V \quad R_{EQ} = 110k\Omega \parallel 270k\Omega = 78.2 k\Omega$$

$$I_C = 150 \frac{-10.66 - 0.7 - (-15)}{78.2k\Omega + 151(18k\Omega)} = 195 \mu A \quad r_o = \frac{(75 + 11.5)V}{195\mu A} = 446 k\Omega \quad r_\pi = \frac{150}{40(195\mu A)} = 19.3 k\Omega$$

$$R_{out} = 446k\Omega \left[1 + \frac{150(18k\Omega)}{78.2k\Omega + 19.3k\Omega + 18k\Omega} \right] = 10.9 M\Omega$$

$$(iii) R_1 + R_2 \cong \frac{15V}{20\mu A} = 750k\Omega \quad \text{Using a spreadsheet with } I_o = 200 \mu A \text{ yields } V_{BB} = 9V.$$

$$R_1 = 750k\Omega \left(\frac{9V}{15V} \right) = 450 k\Omega \quad R_1 = 300 k\Omega \quad R_E = \frac{150}{151} \left[\frac{9 - 0.7 - 1.33\mu A(180k\Omega)}{200\mu A} \right] = 40.0 k\Omega$$

$$R_{out} = \left(\frac{75 + 15 - 8.3}{2 \times 10^{-4}} \right) \left[1 + \frac{150(40.0k\Omega)}{180k\Omega + 18.75k\Omega + 40.0k\Omega} \right] = 10.7 M\Omega$$

Page 893

$$(i) V_{DS} \geq V_{GS} - V_{TN} = 1 + \sqrt{\frac{2(0.2mA)}{2.49mA/V^2}} = 1.40 V \quad V_D = V_S + 1.40 = -15 + 0.2mA(18.2k\Omega) + 1.40 = -9.96V$$

$$(ii) \frac{W}{L} = \frac{K_n}{K'_n} = \frac{2.49mA/V^2}{25\mu A/V^2} = \frac{99.6}{1}$$

$$(iii) P_{R_s} = (0.2mA)^2 18.2k\Omega = 0.728 mW \quad I_{BIAS} = \frac{15V}{499k\Omega + 249k\Omega} = 20.1 \mu A$$

$$P_{R_4} = (20.1\mu A)^2 499k\Omega = 0.202 mW \quad P_{R_3} = (20.1\mu A)^2 249k\Omega = 0.101 mW$$

$$V_{GG} = -15V \frac{510k\Omega}{510k\Omega + 240k\Omega} = -10.2V \quad -10.2 - V_{GS} - 18000I_D = -15V$$

$$4.8 - V_{GS} - 18000 \frac{2.49mA}{2} (V_{GS} - 1)^2 = 0 \quad V_{GS} = 1.390 V \quad I_D = 189 \mu A$$

$$R_{out} \cong \mu_f R_s \cong \frac{1}{0.01} \sqrt{\frac{2(2.49 \times 10^{-3})}{189 \times 10^{-6}}} [1 + 0.01(11.6)] (18k\Omega) = 10.3 M\Omega$$

Page 894

$$R_{avg} = 10k\Omega(1 + 0.2) = 12 k\Omega \quad 12k\Omega(1 - 0.01) \leq R \leq 12k\Omega(1 + 0.01) \quad 11.88 k\Omega \leq R \leq 12.12 k\Omega$$

Page 896

$$(i) V_{DS1} = V_{TN} + \sqrt{\frac{2I_{REF}}{K_n(1 + \lambda V_{DS1})}} \quad V_{DS1} = 1 + \sqrt{\frac{2(150\mu A)}{250\mu A/V^2[1 + 0.0133V_{DS1}]}} \rightarrow V_{DS1} = 2.08 \text{ V}$$

$$I_O = 150\mu A \frac{1 + 0.0133(10)}{1 + 0.0133(2.08)} = 165 \mu A$$

$$(ii) V_{DS} \geq V_{GS} - V_{TN} \quad V_D - (-10V) \geq \sqrt{\frac{2I_D}{K_n}} \quad V_D \geq -10V + \sqrt{\frac{2(150\mu A)}{250\mu A/V^2}} = -8.91 \text{ V}$$

Page 897

$$MR = \frac{25/1}{3/1} = 8.33 \quad V_{DS1} = 1V + \sqrt{\frac{2(50\mu A)}{3(25\mu A/V^2)}} = 2.16 \text{ V} \quad MR = 8.33 \frac{1 + 0.02(15)}{1 + 0.02(2.16)} = 10.4$$

$$MR = \frac{2/1}{5/1} = 0.400 \quad V_{DS1} = 1V + \sqrt{\frac{2(50\mu A)}{5(25\mu A/V^2)}} = 1.89 \text{ V} \quad MR = 8.33 \frac{1 + 0.02(10)}{1 + 0.02(1.89)} = 0.463$$

Page 899

$$I_{REF} = I_S \exp\left(\frac{V_{BE1}}{V_T}\right) \left(1 + \frac{V_{BE1}}{V_{A1}} + \frac{2}{\beta_{FO}}\right) \quad 100\mu A = (0.1 fA) \exp(40V_{BE1}) \left(1 + \frac{V_{BE1}}{50V} + \frac{2}{100}\right) \rightarrow V_{BE1} = 0.690$$

$$V_{CE} \geq V_{BE} \rightarrow V_C \geq -V_{EE} + 0.690 \text{ V}$$

Page 900

$$MR = \frac{0.5A}{A} = 0.5 \quad MR = \frac{0.5}{1 + \frac{1.5}{75}} = 0.490 \quad MR = 0.5 \frac{1 + \frac{15}{60}}{1 + \frac{0.7}{60} + \frac{1.5}{75}} = 0.606$$

$$MR = \frac{5A}{2A} = 2.50 \quad MR = \frac{2.50}{1 + \frac{3.5}{75}} = 2.39 \quad MR = 2.5 \frac{1 + \frac{15}{60}}{1 + \frac{0.7}{60} + \frac{3.5}{75}} = 2.95$$

Page 901

$$(i) I_{O2} = 100\mu A \left(\frac{10/1}{5/1} \right) = 200 \mu A \quad I_{O3} = 100\mu A \left(\frac{20/1}{5/1} \right) = 400 \mu A$$

$$I_{O4} = 100\mu A \left(\frac{40/1}{5/1} \right) = 800 \mu A \quad I_{O5} = 100\mu A \left(\frac{2.5/1}{5/1} \right) = 50 \mu A$$

$$(ii) I_{O2} = 200\mu A \frac{1+0.02(10)}{1+0.02(2)} = 231 \mu A \quad I_{O3} = 400\mu A \frac{1+0.02(5)}{1+0.02(2)} = 423 \mu A$$

$$I_{O4} = 800\mu A \frac{1+0.02(12)}{1+0.02(2)} = 954 \mu A \quad I_{O5} = 50\mu A \frac{1+0.02(8)}{1+0.02(2)} = 55.8 \mu A$$

Page 902

$$(i) I_{O2} = 10\mu A \frac{1}{1+\frac{17}{50}} = 7.46 \mu A \quad I_{O3} = 5(7.46\mu A) = 37.3 \mu A \quad I_{O4} = 10(7.46\mu A) = 74.6 \mu A$$

$$I_{O2} = 10\mu A \frac{1+\frac{10}{50}}{1+\frac{0.7}{50}+\frac{17}{50}} = 8.86 \mu A \quad I_{O3} = 50\mu A \frac{1+\frac{10}{50}}{1+\frac{0.7}{50}+\frac{17}{50}} = 44.3 \mu A$$

$$I_{O4} = 100\mu A \frac{1+\frac{10}{50}}{1+\frac{0.7}{50}+\frac{17}{50}} = 88.6 \mu A$$

$$(ii) MR = \frac{10}{1+\frac{11}{50(51)}} = 9.957 \quad FE = \frac{10-9.957}{10} = 4.3 \times 10^{-3} \quad V_{CE2} = V_{BE1} + V_{BE3} = 1.4 V$$

Page 903

$$\text{MOS: } I_{O2} = 200\mu A \frac{1+0.02(10)}{1+0.02(2)} = 231 \mu A \quad R_{out2} = \frac{50V+10V}{231\mu A} = 260 k\Omega$$

$$I_{O3} = 400\mu A \frac{1+0.02(5)}{1+0.02(2)} = 423 \mu A \quad R_{out3} = \frac{50V+5V}{423\mu A} = 130 k\Omega$$

$$\text{BJT: } I_{O2} = 10\mu A \frac{1+\frac{10}{50}}{1+\frac{0.7}{50}+\frac{17}{100}} = 10.1 \mu A \quad R_{out2} = \frac{50V+10V}{10.1\mu A} = 5.94 M\Omega$$

$$I_{O3} = 50\mu A \frac{1+\frac{10}{50}}{1+\frac{0.7}{50}+\frac{17}{100}} = 50.7 \mu A \quad R_{out3} = \frac{50V+10V}{50.7\mu A} = 1.19 M\Omega$$

Page 904

$$I_{C1} = 100\mu A \frac{1 + \frac{0.7V}{50V}}{1 + \frac{0.7V}{50V} + \frac{6}{50V}} = 89.4\mu A \quad I_{C2} = 500\mu A \frac{1 + \frac{10V}{50V}}{1 + \frac{0.7V}{50V} + \frac{6}{50V}} = 529\mu A$$

$$R_{in} \cong \frac{1}{g_{m1}} = \frac{1}{40(89.4\mu A)} = 280 \Omega \quad \beta = \frac{529\mu A}{89.4\mu A} = 5.92 \quad R_{out} = \frac{50V + 10V}{529\mu A} = 113 \text{ k}\Omega$$

Page 906

$$V_{DS1} = V_{GS1} = 0.75V + \sqrt{\frac{2(100\mu A)}{1\text{mA}/V^2}} = 1.20 \text{ V} \quad I_{D2} = 100\mu A \frac{1 + \frac{10V}{50V}}{1 + \frac{1.2}{50V}} = 117 \mu A$$

$$R_{in} \cong \frac{1}{g_{m1}} = \frac{1}{\sqrt{2(10^{-3})(10^{-4})}} = 2.24 \text{ k}\Omega \quad \beta = \frac{117\mu A}{100\mu A} = 1.17 \quad R_{out} = \frac{50V + 10V}{117\mu A} = 513 \text{ k}\Omega$$

Page 907

$$(i) \quad R = \frac{V_T}{I_O} \ln\left(\frac{I_{REF}}{I_O} \frac{A_{E2}}{A_{E1}}\right) = \frac{0.025V}{25\mu A} \ln\left(\frac{100\mu A}{25\mu A} 5\right) = 3000 \Omega$$

$$K = 1 + \ln\left(\frac{100\mu A}{25\mu A} 5\right) = 4.00 \quad R_{out} = 4\left(\frac{75V}{25\mu A}\right) = 12.0 \text{ M}\Omega$$

$$(ii) \quad I_O = \frac{V_T}{R} \ln\left(\frac{I_{REF}}{I_O} \frac{A_{E2}}{A_{E1}}\right) \quad I_O = \frac{0.025V}{100\Omega} \ln\left(\frac{1000\mu A}{I_O}\right) \rightarrow I_O = 300.54 \mu A$$

$$K = 1 + \ln\left(\frac{100\mu A}{300.54\mu A} 10\right) = 2.202 \quad R_{out} = 2.202\left(\frac{75V}{300.54\mu A}\right) = 550 \text{ k}\Omega$$

Page 909

$$I_O = \frac{1}{R} \sqrt{\frac{2I_{REF}}{K_{n1}} \left(1 - \sqrt{\frac{I_O}{I_{REF}} \frac{(W/L)_1}{(W/L)_2}}\right)} \quad I_O = \frac{1}{2\text{k}\Omega} \sqrt{\frac{2(200\mu A)}{25\mu A/V^2} \left(1 - \sqrt{\frac{I_O}{200\mu A} 10}\right)}$$

$$I_O = 2.00\text{mA} \left(1 - \sqrt{\frac{I_O}{2.00\text{mA}}}\right) \rightarrow I_O = 764 \mu A$$

$$R_{out} = \frac{50V + 10V}{764\mu A} \left(1 + 2000 \sqrt{2(2.5 \times 10^{-4})(7.64 \times 10^{-4})}\right) = 176 \text{ k}\Omega$$

Page 912

$$R_{out} \cong \frac{\beta_o r_o}{2} = \frac{150}{2} \left(\frac{50V + 15V}{50\mu A}\right) = 97.5 \text{ M}\Omega \quad R_{out} = r_o = \frac{50V + 15V}{50\mu A} = 1.30 \text{ M}\Omega$$

Page 913

$$V_{DS2} = V_{GS2} = 0.8V + \sqrt{\frac{2(5 \times 10^{-5})}{2.5 \times 10^{-4}}} = 1.43V \quad V_{DS4} = 15 - 1.43 = 13.6V$$

$$R_{out} \cong \mu_{f4} r_{o2} = \sqrt{2(2.5 \times 10^{-4})(5 \times 10^{-5})} [1 + 0.015(13.6)] \left(\frac{1}{0.015} \frac{V + 13.6V}{50 \mu A} \right) \left(\frac{1}{0.015} \frac{V + 1.43V}{50 \mu A} \right) = 379 M\Omega$$

$$R_{out} = r_o = \frac{66.7V + 15V}{50 \mu A} = 1.63 M\Omega$$

Page 914

$$R_{out} \cong \frac{\beta_o r_o}{2} = \frac{100}{2} \left(\frac{67V + 14.3V}{50 \mu A} \right) = 81.3 M\Omega \quad R_{out} = r_o = \frac{67V + 15V}{50 \mu A} = 164 k\Omega$$

Page 916

$$(i) I_O = 25.015 \mu A + \frac{10V - 20V}{1.66 G\Omega} = 25.009 \mu A$$

$$(ii) V_{DS4} \geq V_{GS4} - V_{TN} = 0.2V \quad V_{D4} \geq V_{S4} + 0.2 \quad V_{D4} \geq 0.95 + 0.2 = 1.15V$$

$$(iii) I_O = 50 \mu A \pm 0.1\% \quad \Delta I_O \leq 50 nA \quad R_{out} \geq \frac{20V}{50 nA} = 400 M\Omega \quad \text{Choose } R_{out} = 1 G\Omega$$

$$r_o \cong \frac{50V}{50 \mu A} = 1 M\Omega \rightarrow \mu_f = 1000 \quad \mu_f \cong \frac{1}{\lambda} \sqrt{\frac{2K_n}{I_D}} \quad K_n = \left[\frac{0.01}{V} (1000) \right]^2 \frac{50 \mu A}{2} = 2.5 \frac{mA}{V^2}$$

$$(W/L)_2 = (W/L)_4 = \frac{2.5 \times 10^{-3}}{5 \times 10^{-5}} = \frac{50}{1} \quad (W/L)_3 = (W/L)_1 = \frac{1}{2} \left(\frac{50}{1} \right) = \frac{25}{1}$$

Page 917

$$(i) I_{REF} = \frac{5V - 0.7V}{43 k\Omega} = 100 \mu A \quad I_{REF} = \frac{7.5V - 0.7V}{43 k\Omega} = 158 \mu A$$

$$(ii) \text{ Since the transistors have the same parameters, } V_{GS1} = \frac{V_{DD} - (-V_{SS})}{3}$$

$$I_{D2} = I_{D1} = \frac{4 \times 10^{-4}}{2} (1.667 - 1)^2 = 89.0 \mu A \quad I_{D2} = I_{D1} = \frac{4 \times 10^{-4}}{2} (2.5 - 1)^2 = 450 \mu A$$

Page 918

$$I_O \cong \frac{0.025V}{6.8 k\Omega} \ln \frac{5 - 1.4}{10^{-16} (39 k\Omega)} = 101 \mu A \quad I_O \cong \frac{0.025V}{6.8 k\Omega} \ln \frac{7.5 - 1.4}{10^{-16} (39 k\Omega)} = 103 \mu A$$

Page 919

$$(i) I_O = \frac{V_T}{R} \ln\left(\frac{I_{C1} A_{E2}}{I_{C2} A_{E1}}\right) \quad I_O = \frac{0.025V}{1000\Omega} \ln[10(10)] = 115 \mu A$$

$$(ii) V_{CC} + V_{EE} \geq V_{BE1} + V_{BE4} \approx 1.4 V$$

Page 921

$$R = \sqrt{\frac{2}{5(25 \times 10^{-6})(10^{-4})}} \left(1 - \sqrt{\frac{5}{50}}\right) = 8.65 k\Omega$$

Page 923

$$(ii) R = \frac{V_T}{I_O} \ln\left(\frac{I_{C1} A_{E2}}{I_{C2} A_{E1}}\right) = \frac{0.02588V}{45\mu A} \ln\left(\frac{25}{5}\right) = 926 \Omega$$

$$A_{E1} = A \quad A_{E2} = 25 A_{E1} = 25 A \quad A_{E3} = A \quad A_{E4} = 5.58 A_{E3} = 5.58 A$$

Page 927

$$I_{D3} = I_{D4} = I_{D1} = I_{D2} = \frac{250\mu A}{2} = 125 \mu A \quad V_{GS1} = 0.75V + \sqrt{\frac{2(125\mu A)}{250\mu A/V^2}} = 1.75 V$$

$$V_{GS3} = -0.75V - \sqrt{\frac{2(125\mu A)}{200\mu A/V^2}} = -1.87 V$$

$$V_{DS1} = V_{D1} - V_{S1} = (5 - 1.87) - (-1.75) = 4.88 V \quad V_{SD3} = V_{SG3} = 1.87 V$$

$$M_1 \text{ and } M_2 : (125\mu A, 4.88V) \quad M_3 \text{ and } M_4 : (125\mu A, 1.87V)$$

$$G_m = g_{m1} = \sqrt{2(2.5 \times 10^{-4})(1.25 \times 10^{-4})} = 250 \mu S$$

$$R_o = r_{o2} \parallel r_{o4} = \frac{75.2V + 4.88V}{125\mu A} \parallel \frac{75.2V + 1.87V}{125\mu A} = 314 k\Omega$$

$$A_v = G_m R_o = 78.5$$

Page 928

$$CMRR \approx \mu_{f3} g_{m2} R_{SS} = \left(\frac{1}{\lambda} \sqrt{\frac{2K_{n3}}{I_{D3}}}\right) \left(\sqrt{2K_{n2} I_{D2}}\right) R_{SS} = \left(\frac{1}{\lambda} \sqrt{\frac{2K_{n3}}{I_{D3}}}\right) \left(\sqrt{2K_{n2} I_{D2}}\right) R_{SS}$$

$$K_{n3} = K_{n2} \quad I_{D2} = I_{D3} \quad CMRR = \frac{1}{0.0167} 2(0.005)10^7 = 5.99 \times 10^6 \quad \text{or } 136 dB$$

Page 932

For the buffered current mirror, $V_{EC4} = V_{EB3} + V_{EB11} + \frac{2V_A}{\beta_{FO4}(\beta_{FO11} + 1)}$

$$I_{C11} \cong \frac{2I_{C4}}{\beta_{FO4}} = \frac{2I_{C4}}{50} = \frac{I_{C4}}{25} \quad \Delta V_{EB} = 0.025 \ln\left(\frac{I_{C4}}{I_{C4}/25}\right) = 80.5 \text{ mV}$$

$$V_{EC4} = 0.7 + (0.7 - 0.081) + \frac{2(60)}{50(51)} = 1.37 \text{ V} \quad \Delta V_{EC} = \frac{2(60V)}{50(51)} = 47.1 \text{ mV} \quad V_{OS} = \frac{47 \text{ mV}}{100} = 0.47 \text{ mV}$$

Page 933

$$A_{dm} \cong A_{v1}A_{v2}A_{v3} \quad A_{v1} \cong \left(\beta_{o5} \frac{I_{C2}}{I_{C5}}\right) = \frac{150}{3} = 50 \quad A_{v2} \cong \mu_{f5} \cong 40(75) = 3000 \quad A_{v3} \cong 1$$

$$A_{dm} \cong 50(3000)(1) = 150000 \quad \text{Note that this assumes } R_L = \infty.$$

Page 934

$$CMRR = \frac{2}{100} \left[\frac{1}{100(40)(75)} - \frac{1}{2(40)(10^{-4})(10^7)} \right]^{-1} = 5.45 \times 10^6 \rightarrow 135 \text{ dB}$$

Page 941

$$(i) I_{REF} = \frac{22 + 22 - 1.4}{39 \text{ k}\Omega} = 1.09 \text{ mA} \quad I_1 = \frac{0.025V}{5 \text{ k}\Omega} \ln\left(\frac{1.09 \text{ mA}}{I_1}\right) \rightarrow I_1 = 20.0 \text{ }\mu\text{A}$$

$$I_2 = 0.75(1.09 \text{ mA}) \frac{1 + \frac{23.4V}{60V}}{1 + \frac{0.7V}{60V} + \frac{2}{50}} = 1.08 \text{ mA} \quad I_2 = 0.25(1.09 \text{ mA}) \frac{1 + \frac{21.3V}{60V}}{1 + \frac{0.7V}{60V} + \frac{2}{50}} = 351 \text{ }\mu\text{A}$$

$$(ii) R_o = r_{o21} \left[1 + \ln \frac{I_{C20} A_{E20}}{I_{C21} A_{E21}} \right] = \frac{60V + 13.5V}{18.4 \mu\text{A}} \left[1 + \ln \left(\frac{733 \mu\text{A}}{18.4 \mu\text{A}} \right) \right] = 18.7 \text{ M}\Omega$$

Page 945

$$(ii) V_{CE6} = V_{CE5} + \frac{2V_{A6}}{\beta_{FO6}} = 0.7 + \frac{2(60V)}{100} = 1.90 \text{ V}$$

Page 948

$$R_{th} = 2r_{o4} \parallel 1.3r_{o6} = 2 \left(\frac{60 + 13}{7.25 \mu\text{A}} \right) \parallel 1.3 \left(\frac{60 + 1.3}{7.16 \mu\text{A}} \right) = 20.1 \text{ M}\Omega \parallel 11.1 \text{ M}\Omega = 7.15 \text{ M}\Omega$$

Page 950

$$A_{v1} = -1.46 \times 10^{-4} (6.54 \text{ M}\Omega \parallel R_{in1}) = -1.46 \times 10^{-4} (6.54 \text{ M}\Omega \parallel 20.7 \text{ k}\Omega) = -3.01$$

$$(i) R_{eq2} = r_{\pi16} + (\beta_{o16} + 1)R_L = \frac{50(0.025)}{2mA} + 51(2k\Omega) = 103 k\Omega$$

$$R_{eq1} = r_{d14} + (r_{d13} + R_3) \parallel R_{eq2} = \frac{0.025V}{0.216mA} + \left[\frac{0.025V}{0.216mA} + 344k\Omega \right] \parallel 103k\Omega = 79.4 k\Omega$$

$$R_{in12} = \frac{50(0.025V)}{0.216mA} + 51(79.4k\Omega) = 4.06 M\Omega$$

$$R_{eq3} = (r_{d13} + R_3) \parallel \left(r_{d14} + \frac{r_{\pi12} + y_{22}^{-1}}{\beta_{o12} + 1} \right) = \left(\frac{0.025V}{0.216mA} + 344k\Omega \right) \parallel \left(\frac{0.025V}{0.216mA} + \frac{5.79k\Omega + 89.1k\Omega}{51} \right) = 1.97 k\Omega$$

$$r_{\pi16} = 50 \frac{0.025}{2mA} = 625\Omega \quad R_{out} = \frac{625 + 1970}{51} + 22 = 75.9 \Omega$$

$$(ii) I_{SC+} \cong \frac{0.7V}{27\Omega} = 25.9 mA \quad I_{SC-} \cong -\frac{0.7V}{22\Omega} = -31.8 mA$$

CHAPTER 16

Page 988

$$f_L \cong \frac{1}{2\pi} \sqrt{10^2 + 1000^2 - 2(50)^2 - 2(0)^2} = 159 \text{ Hz} \quad f_L \cong \frac{1}{2\pi} \sqrt{100^2 + 1000^2 - 2(500)^2 - 2(0)^2} = 114 \text{ Hz}$$

Page 989

$$\left| \frac{200s}{(s+1000)} \right| \geq 0.9 \left| \frac{200s(s+100)}{(s+10)(s+1000)} \right| \quad 1 \geq 0.9 \frac{\sqrt{\omega^2 + 100^2}}{\sqrt{\omega^2 + 10^2}} \rightarrow 0.81 \leq \frac{\omega^2 + 10^2}{\omega^2 + 100^2} \rightarrow \omega \geq 205 \text{ rad/s}$$

Page 996

(i) The value of C_2 does not change A_{mid} , ω_{P1} , ω_{P3} , ω_{z1} , or ω_{z3} .

$$\omega_{P2} = -\frac{1}{2\mu F \left(1.3k\Omega \parallel \frac{1}{1.23mS} \right)} = -1000 \text{ rad/s} \quad \omega_{Z3} = -\frac{1}{2\mu F (1.3k\Omega)} = -385 \text{ rad/s}$$

$$f_L = \frac{1}{2\pi} \sqrt{41.0^2 + 95.9^2 + 1000^2 - 2(0^2 + 0^2 + 385^2)} = 135 \text{ Hz}$$

$$(ii) A_{mid} = 10^{\frac{13.5}{20}} = 4.732 \quad 4.3k\Omega \parallel 100k\Omega \parallel r_o = \frac{4.732}{1.23mS} \rightarrow r_o = 57.5k\Omega$$

Note that the SPICE value of g_m probably differs from 1.23mS as well.

$$(iii) \omega_{P2} = -\frac{1}{10\mu F \left(1.3k\Omega \parallel \frac{1}{1.23mS} \parallel 57.5k\Omega \right)} = -202 \text{ rad/s}$$

$$f_L = \frac{1}{2\pi} \sqrt{41.0^2 + 95.9^2 + 202^2 - 2(0^2 + 0^2 + 76.9^2)} = 31.8 \text{ Hz}$$

Page 999

$$(ii) r_\pi = \frac{140(0.025V)}{175\mu A} = 20.0 \text{ k}\Omega \quad R_{1S}C_1 = (1k\Omega + 75k\Omega \parallel 20.0k\Omega)2\mu F = 33.6 \text{ ms} \quad R_{th} = 75k\Omega \parallel 1k\Omega = 987 \Omega$$

$$R_{2S}C_2 = \left(13k\Omega \parallel \frac{20.0k\Omega + 987\Omega}{141} \right) 10\mu F = 1.47 \text{ ms} \quad R_{3S}C_3 = (43k\Omega + 100k\Omega)0.1\mu F = 14.3 \text{ ms}$$

$$f_L \cong \frac{1}{2\pi} \left(\frac{1}{33.6ms} + \frac{1}{1.47ms} + \frac{1}{14.3ms} \right) = 124 \text{ Hz}$$

Page 1001

$$(i) A_v = -\frac{R_{in}}{R_I + R_{in}} \left(\frac{\beta_o}{r_\pi} R_L \right) \cong -\left(\frac{1260}{2260} \right) \left(\frac{100}{1.51k\Omega} \right) (4.3k\Omega \parallel 100k\Omega) = -157$$

$$A_v = -\frac{R_{in}}{R_I + R_{in}} \left(\frac{\beta_o}{r_\pi} R_L \right) \cong -\left(\frac{1260}{2260} \right) \left(\frac{100}{1.51k\Omega} \right) (4.3k\Omega \parallel 100k\Omega \parallel 46.8k\Omega) = -140$$

r_o is responsible for most of the discrepancy. r_π and β_o will also be differ from our hand calculations.

Note that 45% of the gain is lost because of the amplifier's low input resistance.

$$(ii) g_m = \frac{2(1.5mA)}{0.5V} = 6.00 \text{ mS} \quad R_{1S}C_1 = (1k\Omega + 243k\Omega)0.1\mu F = 24.4 \text{ ms}$$

$$R_{2S}C_2 = \left(1.3k\Omega \parallel \frac{1}{6.00mS} \right) 10\mu F = 1.48 \text{ ms} \quad R_{3S}C_3 = (4.3k\Omega + 100k\Omega)0.1\mu F = 10.4 \text{ ms}$$

$$f_L \cong \frac{1}{2\pi} \left(\frac{1}{24.4ms} + \frac{1}{1.48ms} + \frac{1}{10.4ms} \right) = 129 \text{ Hz}$$

Page 1003

$$(i) g_m = 40(0.1mA) = 4.00 \text{ mS} \quad R_{1S}C_1 = \left(100\Omega + 43k\Omega \parallel \frac{1}{4.00mS} \right) 4.7\mu F = 1.64 \text{ ms}$$

$$R_{2S}C_2 = (22k\Omega + 75k\Omega)1\mu F = 97.0 \text{ ms} \quad f_L \cong \frac{1}{2\pi} \left(\frac{1}{1.64ms} + \frac{1}{97.0ms} \right) = 98.7 \text{ Hz}$$

Page 1004

$$g_m = \frac{2(1.5mA)}{0.5V} = 6.00 \text{ mS} \quad R_{1S}C_1 = \left(100\Omega + 1.3k\Omega \parallel \frac{1}{6.00mS} \right) 1\mu F = 0.248 \text{ ms}$$

$$R_{2S}C_2 = (4.3k\Omega + 75k\Omega)0.1\mu F = 7.93 \text{ ms} \quad f_L \cong \frac{1}{2\pi} \left(\frac{1}{0.248ms} + \frac{1}{7.93ms} \right) = 662 \text{ Hz}$$

Page 1005

$$(i) \quad g_m = 40(1mA) = 40.0 \text{ mS} \quad r_\pi = \frac{100}{.04S} = 2.50 \text{ k}\Omega$$

$$R_{1S}C_1 = \left(1k\Omega + 100k\Omega \parallel \left[2.5k\Omega + 101(3k\Omega \parallel 47k\Omega)\right]\right)0.1\mu F = 7.52 \text{ ms}$$

$$R_{2S}C_2 = \left(47k\Omega + 3k\Omega \parallel \frac{2.5k\Omega + (100k\Omega \parallel 1k\Omega)}{101}\right)100\mu F = 4.70 \text{ s} \quad f_L \cong \frac{1}{2\pi} \left(\frac{1}{7.52ms} + \frac{1}{4.7s}\right) = 21.2 \text{ Hz}$$

$$A_{mid} \cong \frac{(\beta_o + 1)R_L}{R_{th} + r_\pi + (\beta_o + 1)R_L} \left(\frac{R_f}{R_f + R_B}\right) = \frac{101(3k\Omega \parallel 47k\Omega)}{990\Omega + 2.5k\Omega + 101(3k\Omega \parallel 47k\Omega)} \left(\frac{100k\Omega}{1k\Omega + 100k\Omega}\right) = +0.978$$

$$(ii) \quad R_{1S}C_1 = (1k\Omega + 243k\Omega)0.1\mu F = 24.4 \text{ ms}$$

$$R_{2S}C_2 = \left(24k\Omega + 1.3k\Omega \parallel \frac{1}{1mS}\right)47\mu F = 1.15 \text{ s} \quad f_L \cong \frac{1}{2\pi} \left(\frac{1}{24.4ms} + \frac{1}{1.15s}\right) = 6.66 \text{ Hz}$$

$$A_{mid} = + \left(\frac{R_G}{R_f + R_G}\right) \frac{g_m R_L}{1 + g_m R_L} = + \left(\frac{243k\Omega}{244k\Omega}\right) \frac{1mS(1.3k\Omega \parallel 24k\Omega)}{1 + (1.3k\Omega \parallel 24k\Omega)} = +0.550$$

Page 1009

$$C_\pi = \frac{g_m}{\omega_T} - C_\mu \quad C_\mu = \frac{C_{\mu o}}{\sqrt{1 + \frac{V_{CB}}{\varphi_{jc}}}}$$

$$(100\mu A, 8V): \quad C_\mu = \frac{2pF}{\sqrt{1 + \frac{7.3V}{0.6V}}} = 0.551 \text{ pF} \quad C_\pi = \frac{40(10^{-4})}{2\pi(500 \text{ MHz})} - 0.551 \times 10^{-12} = 0.722 \text{ pF}$$

$$(2mA, 5V): \quad C_\mu = \frac{2pF}{\sqrt{1 + \frac{4.3V}{0.6V}}} = 0.700 \text{ pF} \quad C_\pi = \frac{40(2 \times 10^{-3})}{2\pi(500 \text{ MHz})} - 0.700 \times 10^{-12} = 24.8 \text{ pF}$$

$$(50mA, 8V): \quad C_\mu = \frac{2pF}{\sqrt{1 + \frac{7.3V}{0.6V}}} = 0.551 \text{ pF} \quad C_\pi = \frac{40(5 \times 10^{-2})}{2\pi(500 \text{ MHz})} - 0.551 \times 10^{-12} = 636 \text{ pF}$$

Page 1012

$$(i) C_{GS} = C_{GD} = \frac{1}{2} C_{ISS} = 0.5 \text{ pF}$$

$$(ii) C_{GS} + C_{GD} = \frac{g_m}{\omega_T} \quad 5C_{GD} + C_{GD} = \frac{\sqrt{2(0.01)(0.01)}}{2\pi(200 \text{ MHz})} = 11.3 \text{ pF} \quad C_{GD} = 1.88 \text{ pF} \quad C_{GS} = 9.38 \text{ pF}$$

$$(iii) C_\mu = \frac{C_{\mu o}}{\sqrt{1 + \frac{V_{CB}}{\varphi_{jc}}}} = \frac{2 \text{ pF}}{\sqrt{1 + \frac{7.3 \text{ V}}{0.6 \text{ V}}}} = 0.551 \text{ pF} \quad C_\pi = \frac{g_m}{\omega_T} - C_\mu = \frac{40(20 \mu\text{A})}{2\pi(500 \text{ MHz})} - 0.551 \text{ pF} = -0.296 \text{ pF}$$

Page 1015

$$A_v = -\frac{R_{in}}{R_I + R_{in}} \left(\frac{\beta_o}{r_x + r_\pi} R_L \right) \quad R_{in} = 7.5 \text{ k}\Omega \parallel (1.51 \text{ k}\Omega + 250 \Omega) = 1.43 \text{ k}\Omega$$

$$\cong -\left(\frac{1430}{2430} \right) \left(\frac{100}{1.76 \text{ k}\Omega} \right) (4.3 \text{ k}\Omega \parallel 100 \text{ k}\Omega) = -139$$

$$A_v = -\frac{R_{in}}{R_I + R_{in}} \left(\frac{\beta_o}{r_\pi} R_L \right) \cong -\left(\frac{1260}{2260} \right) \left(\frac{100}{1.51 \text{ k}\Omega} \right) (4.3 \text{ k}\Omega \parallel 100 \text{ k}\Omega) = -157$$

Page 1023

(ii) The term $C_L \frac{R_L}{r_{\pi o}}$ is added to the value of C_T .

$$C_L \frac{R_L}{r_{\pi o}} = 3 \text{ pF} \left(\frac{4120}{656} \right) = 18.8 \text{ pF} \quad f_{p1} = \frac{1}{2\pi(656 \Omega)(156 + 18.8) \text{ pF}} = 1.39 \text{ MHz}$$

$$f_{p2} = \frac{g_m}{2\pi(C_\pi + C_L)} = \frac{0.064 \text{ S}}{2\pi(19.9 + 3) \text{ pF}} = 445 \text{ MHz}$$

$$(iii) C_\pi = \frac{0.064}{2\pi(500 \text{ MHz})} - 10^{-12} = 19.4 \text{ pF}$$

$$C_T = 19.4 + 1 \left[1 + 0.064(4120) + \frac{4120}{656} \right] = 290 \text{ pF} \quad f_{p1} = \frac{1}{2\pi(656 \Omega)290 \text{ pF}} = 837 \text{ kHz}$$

$$f_{p2} = \frac{g_m}{2\pi C_\pi} = \frac{0.064 \text{ S}}{2\pi(19.4 \text{ pF})} = 525 \text{ MHz} \quad f_z = \frac{g_m}{2\pi C_\mu} = \frac{0.064 \text{ S}}{2\pi(1 \text{ pF})} = 10.2 \text{ GHz}$$

$A_{mid} = -135$ is not affected by the value of f_T .

Page 1024

$$C_T = 10 + 2 \left[1 + 1.23mS(4.12k\Omega) + \frac{4120}{996} \right] = 30.4 pF \quad f_{P1} = \frac{1}{2\pi(996\Omega)30.4 pF} = 5.26 MHz$$

$$f_{P2} = \frac{g_m}{2\pi C_{GS}} = \frac{1.23mS}{2\pi(10 pF)} = 19.6 MHz \quad f_z = \frac{g_m}{2\pi C_{GD}} = \frac{1.23mS}{2\pi(2 pF)} = 97.9 MHz$$

$$f_T = \frac{g_m}{2\pi(C_{GS} + C_D)} = \frac{1.23mS}{2\pi(12 pF)} = 16.3 MHz$$

Page 1031

$$(ii) 1 + g_m R_E = 1 + 0.064(100) = 7.4 \quad R_{iB} = 250 + 1560 + 101(100) = 11.9 k\Omega$$

$$r_{\pi 0} = 11.9k\Omega \parallel (882 + 250) = 1030 \Omega$$

$$A_i = \frac{10k\Omega \parallel 30k\Omega \parallel 11.9k\Omega}{1k\Omega + 10k\Omega \parallel 30k\Omega \parallel 11.9k\Omega} = 0.821 \quad A_{mid} = -0.821 \left(\frac{264}{7.4} \right) = -29.3$$

$$f_H = \frac{1}{2\pi(1.03k\Omega) \left[\frac{19.9 pF}{7.4} + 0.5 pF \left(1 + \frac{264}{7.4} + \frac{4120}{1030} \right) \right]} = 6.70 MHz \quad GBW = 196 MHz$$

Page 1033

$$(i) A_{mid} \cong \frac{g'_m R_L}{1 + g'_m R_E} \quad g'_m = \frac{\beta_o}{r_x + r_\pi} = \frac{100}{250 + \frac{100}{40(0.1mA)}} = 3.96 mS \quad A_{mid} \cong \frac{3.96mS(17.0k\Omega)}{1 + 3.96mS(100\Omega)} = +48.2$$

$$f_H \cong \frac{1}{2\pi(17.0k\Omega)(0.5 pF)} = 18.7 MHz \quad GBW = 903 MHz$$

$$(ii) R_{iS} = R_4 \parallel \frac{1}{g_m} = 1.3k\Omega \parallel \frac{1}{3mS} = 265 \Omega \quad A_i = \frac{265}{100 + 265} = 0.726$$

$$A_{mid} = 0.726(g_m R_L) = 0.726(3mS)(4.12k\Omega) = 8.98 \quad f_H \cong \frac{1}{2\pi(4.12k\Omega)(4 pF)} = 9.66 MHz$$

$$f_T \cong \frac{3mS}{2\pi(11 pF)} = 43.4 MHz \quad GBW = 86.7 MHz$$

Page 1035

$$g_m = 40(1.5mA) = 60 \text{ mS} \quad r_\pi = \frac{100}{60\text{mS}} = 1.67 \text{ k}\Omega \quad R_L = 3\text{k}\Omega \parallel 47\text{k}\Omega = 2.82\text{k}\Omega$$

$$A_i = \frac{100\text{k}\Omega \parallel [150 + 1670 + 101(2820)]}{1\text{k}\Omega + 100\text{k}\Omega \parallel [150 + 1670 + 101(2820)]} = 0.987 \quad A_{mid} = 0.987 \frac{60\text{mS}(2.82\text{k}\Omega)}{1 + 60\text{mS}(2.82\text{k}\Omega)} = 0.980$$

$$C_\pi = \frac{60\text{mS}}{2\pi(500\text{MHz})} - 0.5\text{pF} = 18.6\text{pF} \quad f_H \cong \frac{1}{2\pi} \frac{1}{((990 + 150) \parallel 286\text{k}\Omega) \left(0.5\text{pF} + \frac{18.6\text{pF}}{1 + 169}\right)} = 230 \text{ MHz}$$

Page 1036

$$R_L = 1.3\text{k}\Omega \parallel 24\text{k}\Omega = 1.23\text{k}\Omega \quad A_i = \frac{430\text{k}\Omega}{1\text{k}\Omega + 430\text{k}\Omega} = 0.998$$

$$A_{mid} = 0.998 \frac{3\text{mS}(1.23\text{k}\Omega)}{1 + 3\text{mS}(1.23\text{k}\Omega)} = 0.785 \quad f_H \cong \frac{1}{2\pi} \frac{1}{(1\text{k}\Omega \parallel 430\text{k}\Omega) \left(1\text{pF} + \frac{10\text{pF}}{1 + 3.69}\right)} = 50.9 \text{ MHz}$$

Page 1039

$$f_z = \frac{1}{2\pi(25\text{M}\Omega)1\text{pF}} = 6.37 \text{ kHz} \quad f_p = \frac{1}{2\pi(50.25\text{k}\Omega)0.5\text{pF}} = 6.33 \text{ MHz}$$

Page 1041

$$\text{Differential Pair : } A_{dm} = -g_m R_C = -40(99.0\mu\text{A})(50\text{k}\Omega) = -198$$

$$C_\pi = \frac{40(99.0\mu\text{A})}{2\pi(500\text{MHz})} - 0.5\text{pF} = 0.761\text{pF} \quad r_\pi = \frac{100}{40(99.0\mu\text{A})} = 25.3 \text{ k}\Omega$$

$$f_H = \frac{1}{2\pi(250\Omega) \left[0.761\text{pf} + 0.5\text{pF} \left(1 + 198 + \frac{50\text{k}\Omega}{250\Omega}\right)\right]} = 3.18 \text{ MHz}$$

$$\text{CC - CB Cascade : } A_v = \frac{g_{m1} \left(\frac{1}{g_{m2}}\right)}{1 + g_{m1} \left(\frac{1}{g_{m2}}\right)} (g_m R_C) = +\frac{198}{2} = +99 \quad f_H \cong \frac{1}{2\pi(50\text{k}\Omega)(0.5\text{pF})} = 6.37 \text{ MHz}$$

Page 1042

$$g_m = 40(1.6mA) = 64.0 \text{ mS} \quad r_\pi = \frac{100}{64mS} = 1.56 \text{ k}\Omega \quad C_\pi = \frac{64.0mS}{2\pi(500 \text{ MHz})} - 0.5 \text{ pF} = 19.9 \text{ pF}$$

$$A_{mid} = \frac{r_\pi}{R_I + r_x + r_\pi} (-g_m R_L) = \frac{1.56 \text{ k}\Omega}{882\Omega + 250\Omega + 1.56 \text{ k}\Omega} (-64.0mS)(4.12k\Omega) = -153$$

$$f_{p1} \cong \frac{1}{2\pi r_{\pi 0}(C_\pi + 2C_\mu)} = \frac{1}{2\pi(656\Omega)(19.9 + 1)pF} = 11.6 \text{ MHz}$$

$$f_{p2} \cong \frac{1}{2\pi R_L(C_\mu + C_L)} = \frac{1}{2\pi(4120\Omega)(0.5 + 5)pF} = 7.02 \text{ MHz}$$

Page 1043

$$f_{p1} \cong \frac{1}{4\pi C_{GGB}r_{o2}} = \frac{0.02(100\mu A)}{4\pi(1pF)} = 159 \text{ kHz} \quad f_{p1} \cong \frac{1}{4\pi C_{GGB}r_{o2}} = \frac{0.02(25\mu A)}{4\pi(1pF)} = 39.8 \text{ kHz}$$

Page 1050

$$(i) X_C = \frac{1}{2\pi(530 \text{ Hz})39 \text{ pF}} = 7.69 \text{ M}\Omega \gg 2.39 \text{ k}\Omega$$

$$X_C = \frac{1}{2\pi(530 \text{ Hz})1 \text{ pF}} = 300 \text{ M}\Omega \gg 51.8 \text{ k}\Omega \parallel 19.8 \text{ k}\Omega = 14.3 \text{ k}\Omega$$

$$(ii) X_1 = \frac{1}{2\pi(667 \text{ kHz})0.01\mu F} = 23.9 \Omega \ll 1.01 \text{ M}\Omega$$

$$X_2 = \frac{1}{2\pi(667 \text{ kHz})47\mu F} = 5.07 \text{ m}\Omega \ll 66.7 \Omega$$

$$X_3 = \frac{1}{2\pi(667 \text{ kHz})1\mu F} = 239 \text{ m}\Omega \ll 2.69 \text{ k}\Omega$$

Page 1052

$$Z_C = \frac{1}{2\pi j(5 \text{ MHz})0.01\mu F} = -j3.18 \Omega$$

Page 1053

$$(i) f_o = \frac{1}{2\pi\sqrt{(10\mu H)(100 pF + 20 pF)}} = 4.59 \text{ MHz} \quad r_o = \frac{50V + 15V - 1.6V}{3.2mA} = 19.8k\Omega$$

$$Q = \frac{100k\Omega \parallel 100k\Omega \parallel r_o}{2\pi(4.59 \text{ MHz})(10\mu H)} = 49.2 \quad BW = \frac{4.59 \text{ MHz}}{49.2} = 93.3 \text{ kHz}$$

$$A_{mid} = -g_m(100k\Omega \parallel 100k\Omega \parallel r_o) = -\sqrt{2(0.005)(0.0032)}(100k\Omega \parallel 100k\Omega \parallel 19.8k\Omega) = -80.2$$

(ii) f_o is unchanged

CHAPTER 17

Page 1078

$$(i) A_v = \frac{A}{1 + A\beta} \quad \beta = \frac{10k\Omega}{10k\Omega + 91k\Omega} = 0.0990 \quad A_v = \frac{10^4}{1 + 10^4(0.0990)} = 10.1$$

$$R_{in} = R_{id}(1 + A\beta) = 25k\Omega[1 + 10^4(0.0990)] = 24.8 M\Omega \quad R_{out} = \frac{R_o}{1 + A\beta} = \frac{10^3}{1 + 10^4(0.0990)} = 1.01 \Omega$$

$$(ii) A = 4730 \frac{1k\Omega + 25k\Omega + 9.01k\Omega}{25k\Omega + 9.01k\Omega} = 4870 \quad A_v = \frac{4870}{1 + 4870(0.0990)} = 10.1$$

$$R_{in} = R_{id}(1 + A\beta) = 34.0k\Omega[1 + 4870(0.0990)] = 16.4 M\Omega \quad R_{out} = \frac{R_o}{1 + A\beta} = \frac{662\Omega}{1 + 4870(0.0990)} = 1.37 \Omega$$

(iii) $h_{12}^A = 0$ (No reverse gain through the amplifier.)

$$h_{21}^A = \left. \frac{i_2}{i_1} \right|_{v_2=0} = -\frac{25000(10^4)}{1000} = -2.5 \times 10^5 \quad h_{21}^F = \left. \frac{i_2}{i_1} \right|_{v_2=0} = -\frac{10k\Omega}{10k\Omega + 91k\Omega} = -0.0990$$

Page 1086


$$(i) y_{21}^A = \left. \frac{i_2}{v_1} \right|_{v_2=0} = +g_m = +39.1 mS \quad y_{21}^F = \left. \frac{i_2}{v_1} \right|_{v_2=0} = -\frac{1}{R_F} = -10^{-5} S$$

$y_{12}^A = 0$ (No reverse gain through the amplifier.)

$$(ii) A = -\frac{4.76k\Omega}{4.76k\Omega + 3.84k\Omega} (150) (10k\Omega \parallel 100k\Omega \parallel 5k\Omega \parallel 52.6k\Omega) = -252 k\Omega$$

$$\beta = -\frac{1}{R_F} = -10^{-5} S = -0.01 mS \quad A_r = \frac{-252k\Omega}{1 - 252k\Omega(-0.01mS)} = -71.6 k\Omega$$
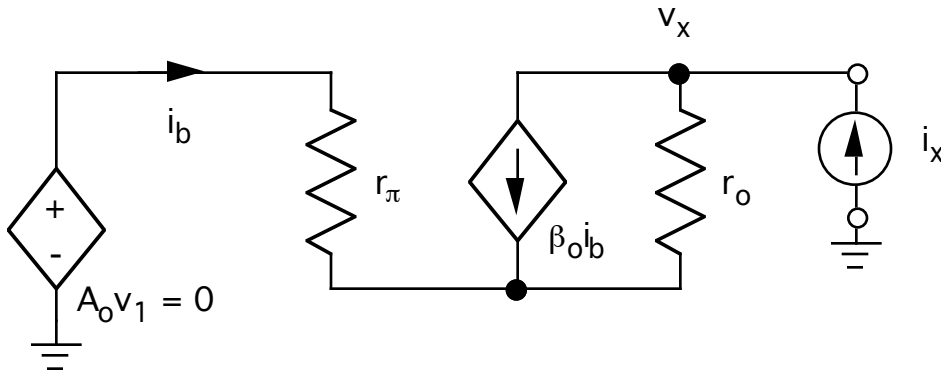
$$R_{in} = \frac{R_{in}^A}{1 + A\beta} = \frac{2.13k\Omega}{1 + 2.52} = 605 \Omega \quad R_{out} = \frac{R_o}{1 + A\beta} = \frac{10k\Omega \parallel 100k\Omega \parallel 5k\Omega \parallel 52.6k\Omega}{1 + 2.52} = 863 \Omega$$



$$v_x = (i_x - \beta_o i_b) r_o + i_x r_\pi \quad i_b = -i_x \quad v_x = (i_x - \beta_o i_x) r_o + i_x r_\pi = i_x r_o \left(\beta_o + 1 + \frac{\beta_o}{\mu_f} \right)$$

$$R_{out} = \frac{v_x}{i_x} = r_o \left(\beta_o + 1 + \frac{\beta_o}{\mu_f} \right) \cong \beta_o r_o \quad \text{for } \beta_o \gg 1 \quad \text{and} \quad \mu_f \gg \beta_o$$

Page 1100

R_E is now connected between the emitter and collector of Q_2 in the upper half of Fig. 17.36. However, when the A - circuit is constructed, y_{22}^F is connected in parallel with R_E , so the resistance at the output of the A - circuit is still 901Ω . The value of y_{11}^F is unchanged, so overall the A - circuit is unchanged. Likewise, β is unchanged, and so A_{tr} is the same.

Page 1102

(i) Using voltage division : $v_+ - v_- = -v_{p1} \frac{R_1 \parallel R_{id}}{R_2 + (R_1 \parallel R_{id})} \quad v_o = A(v_+ - v_-) \quad T = -\frac{v_o}{v_{p1}} = A \frac{R_1 \parallel R_{id}}{R_2 + (R_1 \parallel R_{id})}$

(ii) $T = A \frac{R_1}{R_1 + R_2} \frac{R_{id}}{R_{id} + R_3} = A \frac{R_1}{R_1 + R_2} \frac{R_{id}}{R_{id} + \frac{R_1 R_2}{R_1 + R_2}} = A \frac{R_1 R_{id}}{R_{id} (R_1 + R_2) + R_1 R_2}$

$$T = A \frac{R_1 R_{id}}{R_1 R_{id} + (R_1 + R_{id}) R_2} = A \frac{\frac{R_1 R_{id}}{R_1 + R_{id}}}{\frac{R_1 R_{id}}{R_1 + R_{id}} + R_2} = A \frac{R_1 \parallel R_{id}}{R_2 + R_1 \parallel R_{id}}$$

Page 1108

$$R_D = 50k\Omega \left[1 + \frac{100(5k\Omega \parallel 25k\Omega)}{5k\Omega + 2.5k\Omega + (5k\Omega \parallel 25k\Omega)} \right] = 1.84 M\Omega$$

$$|T_{SC}| = 10^4 \frac{101(3.85k\Omega)}{5k\Omega + 2.5k\Omega + 101(3.85k\Omega)} = 9810 \quad |T_{OC}| = 10^4 \frac{(5k\Omega \parallel 25k\Omega)}{5k\Omega + 2.5k\Omega + (5k\Omega \parallel 25k\Omega)} = 3570$$

$$R_{out} = 1.84 M\Omega \left(\frac{1 + 9810}{1 + 3570} \right) = 5.06 M\Omega$$

Page 1114

The analysis is the same with r_π and $\beta_o \rightarrow \infty$.

$$R_D = r_{o3} \left(1 + \frac{\beta_{o3}}{\mu_{f2} + \beta_{o3} + 1} \right) \rightarrow 2r_{o3} \quad |T_{OC}| = \frac{1}{1 + \frac{\beta_o + 1}{\mu_f}} \rightarrow 0 \quad |T_{SC}| = \frac{\beta_o + 1}{1 + \frac{2\beta_o + 1}{\mu_f}} \rightarrow \frac{\mu_f}{2}$$

$$R_{out} = 2r_{o3} \frac{1 + \frac{\mu_f}{2}}{1 + 0} \equiv \mu_f r_{o3}$$

Page 1116

$$f_B = \frac{f_T}{A_o} = \frac{10^7 \text{ Hz}}{10^5} = 100 \text{ Hz} \quad f_H = \beta f_T = \frac{10^7 \text{ Hz}}{10^3} = 10 \text{ kHz}$$

Page 1120

$$\angle T(j\omega) = -3 \tan^{-1}(\omega) = -\pi \rightarrow \omega = 1.732 \quad |T(j\omega)| = \frac{5}{(\sqrt{\omega^2 + 1})^3} = 0.625$$

$$GM = 20 \log \left(\frac{1}{0.625} \right) = 4.08 \text{ dB}$$

Page 1122

From the Bode plot, the phase shift at the unity gain frequency (10 MHz) is -130° .
The phase margin is $180^\circ - 130^\circ = 50^\circ$.

Page 1124

$$G_m = g_{m2} = \sqrt{2(10^{-3})(5 \times 10^{-5})} = 0.316 \text{ mS} \quad R_O = r_{o4} \parallel r_{o2} \cong \frac{1}{2\lambda I_D} = \frac{1}{2(0.02)5 \times 10^{-5}} = 500 \text{ k}\Omega$$

$$f_T = \frac{1}{2\pi} \left(\frac{G_m}{C_C} \right) = \frac{1}{2\pi} \left(\frac{0.316 \text{ mS}}{20 \text{ pF}} \right) = 2.51 \text{ MHz}$$

$$f_B = \frac{1}{2\pi} \left[\frac{1}{R_O C_C (1 + A_{v2})} \right] = \frac{1}{2\pi} \left[\frac{1}{R_O C_C (1 + \mu_{f2})} \right] \cong \frac{1}{2\pi} \left[\frac{1}{500 \text{ k}\Omega (20 \text{ pF}) \left[1 + \frac{1}{0.02} \sqrt{\frac{2(0.001)}{5 \times 10^{-4}}} \right]} \right] = 158 \text{ Hz}$$

Page 1126

$$f_z \cong \frac{1}{2\pi} \frac{g_{m5}}{C_C} = \frac{1}{2\pi} \frac{\sqrt{2(0.001)5 \times 10^{-4}}}{20 \times 10^{-12}} = 7.96 \text{ MHz} \quad R = \frac{1}{g_{m5}} = \frac{1}{\sqrt{2(0.001)5 \times 10^{-4}}} = 1.00 \text{ k}\Omega$$

Page 1127

$$G_m = g_{m2} = 40(5 \times 10^{-5}) = 2.00 \text{ mS} \quad R_O = r_{\pi5} \cong \frac{100 \text{ V}}{40(5.5 \times 10^{-4} \text{ A})} = 4.54 \text{ k}\Omega$$

$$f_T = \frac{1}{2\pi} \left(\frac{G_m}{C_C} \right) = \frac{1}{2\pi} \left(\frac{2.00 \text{ mS}}{30 \text{ pF}} \right) = 10.6 \text{ MHz} \quad f_z = \frac{1}{2\pi} \left(\frac{g_{m5}}{C_C} \right) = \frac{1}{2\pi} \left[\frac{40(5 \times 10^{-4})}{3 \times 10^{-11}} \right] = 106 \text{ MHz}$$

$$f_B = \frac{1}{2\pi} \left[\frac{1}{r_{\pi5} C_C (1 + \mu_{f2})} \right] \cong \frac{1}{2\pi} \left[\frac{1}{4.54 \text{ k}\Omega (30 \text{ pF}) [1 + 40(50)]} \right] = 584 \text{ Hz}$$

Page 1128

$$(ii) \quad SR = \frac{100 \mu\text{A}}{20 \text{ pF}} = 5.00 \times 10^6 \frac{\text{V}}{\text{s}} = 5.00 \frac{\text{V}}{\mu\text{s}}$$

Page 1129

$$SR = \frac{100 \mu\text{A}}{20 \text{ pF}} = 5.00 \times 10^6 \frac{\text{V}}{\text{s}} = 5.00 \frac{\text{V}}{\mu\text{s}}$$

Page 1132

$$G_m = g_{m2} = 40(2.5 \times 10^{-4}) = 10.0 \text{ mS} \quad f_T = \frac{1}{2\pi} \left(\frac{G_m/2}{C_C + C_{\mu3}} \right) = \frac{1}{4\pi} \left(\frac{10.0 \text{ mS}}{50.8 \text{ pF}} \right) = 15.7 \text{ MHz}$$

$$\phi_M = 90 - \tan^{-1} \left(\frac{15.7 \text{ MHz}}{142 \text{ MHz}} \right) + \tan^{-1} \left(\frac{15.7 \text{ MHz}}{173 \text{ MHz}} \right) + \tan^{-1} \left(\frac{15.7 \text{ MHz}}{192 \text{ MHz}} \right) + \tan^{-1} \left(\frac{15.7 \text{ MHz}}{206 \text{ MHz}} \right) = 69.5^\circ$$

Page 1137

$$(i) SR \cong \frac{I_1}{C_C + C_{GD5}} = \frac{1mA}{65pF} = 15.4 \times 10^6 \frac{V}{s} = 15.4 \frac{V}{\mu s}$$

$$(ii) 30^\circ = \tan^{-1}\left(\frac{f_T}{49.2MHz}\right) + \tan^{-1}\left(\frac{f_T}{82.1MHz}\right) + \tan^{-1}\left(\frac{f_T}{100MHz}\right) \rightarrow f_T = 16.6 MHz$$

$$C_C = 65pF \left(\frac{8.5MHz}{16.6MHz}\right) - 2pF = 31.3 pF$$

Page 1144

$$f_o = \frac{1}{2\pi(10k\Omega)(1nF)} = 15.9kHz \quad |v_o| = \frac{3(0.6V)}{\left(2 - \frac{10k\Omega}{10k\Omega}\right)\left(1 + \frac{24k\Omega}{12k\Omega}\right) - \frac{24k\Omega}{10k\Omega}} = 3.00 V$$

Page 1149

$$f_p = \frac{1}{2\pi \sqrt{31.8mH \left[\frac{31.8fF(7pF)}{7.0318pF} \right]}} = 5.016 MHz \quad f_p = \frac{1}{2\pi \sqrt{31.8mH \left[\frac{31.8fF(25pF)}{25.0318pF} \right]}} = 5.008 MHz$$
