

*Week 8: MOSFET I-V Characteristics,
DC Analysis and Small Signal Model*



Topics to cover ...

- MOSFET Non-ideal I-V Characteristics
- P-channel Devices and Other types
- DC Analysis of MOSFET circuits
- MOSFET Small Signal Model
- Reading Assignment:
Chap 4.1 - 4.4, 4.9 and 13.8 of Jaeger and Blalock or
Chap 4.1 - 4.6 of Sedra & Smith



Summary of NMOS I-V Characteristics

Region	Cutoff	Triode	Saturation
Conditions	$v_{GS} < V_t$	$v_{GS} \geq V_t$	
		$v_{DS} < v_{GS} - V_t$	$v_{DS} \geq v_{GS} - V_t$
I-V relation	$i_D = 0$	$i_D = K'_n \frac{W}{L} \left[(v_{GS} - V_t)v_{DS} - \frac{1}{2}v_{DS}^2 \right]$	$i_D = \frac{1}{2} K'_n \frac{W}{L} (v_{GS} - V_t)^2$

➔ Cutoff region $v_{GS} < V_t$

➔ Triode region

$$v_{GS} \geq V_t \quad \text{and}$$

$$v_{DS} < v_{GS} - V_t$$


➔ Saturation region

$$v_{GS} \geq V_t \quad \text{and}$$



$$v_{DS} \geq v_{GS} - V_t$$

$$K'_n = \mu_n C_{ox}$$

Voltage ↑

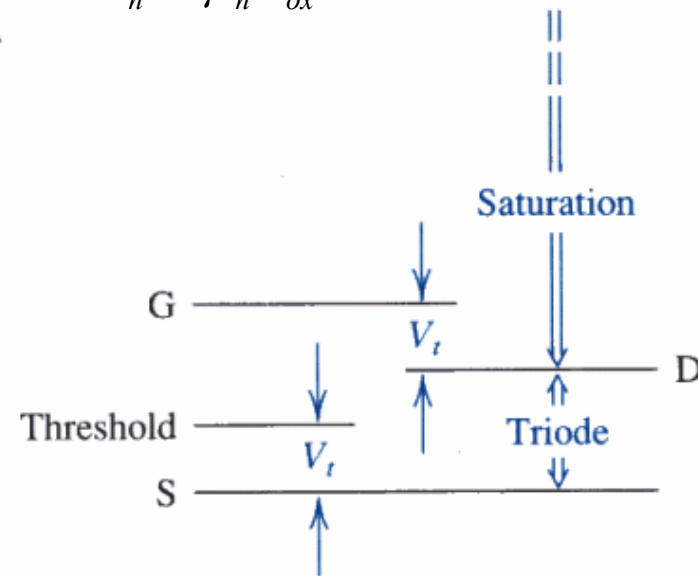

Ideal Characteristics of I_D vs V_{DS}

  

NMOS




Non-ideal I-V Characteristics


- Finite Output Resistance in Saturation
- The role of the Body
- Temperature Effects
- Breakdown and Input Protection



Channel-Length Modulation

 

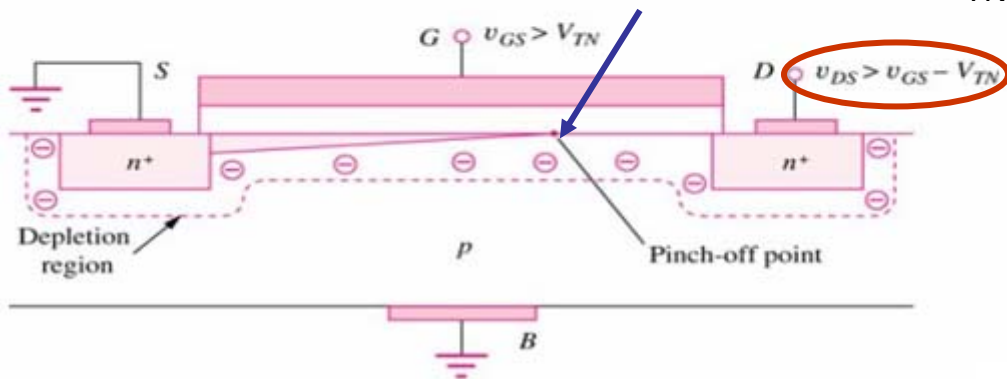(b) where gate-to-channel voltage = V_{TN}



At $v_{DS} = v_{GS} - V_{TN} = V_{DSsat}$,

- Channel pinch-off


- As v_{DS} increases beyond v_{DSsat} , the pinch-off point moves away from D towards S

- Effective channel length L is reduced, or that channel length is modulated by V_{DS} .

- I_D increases with V_{DS} .

- Output resistance is finite in saturation mode.

 
- Output resistance is finite in saturation mode.



$$i_D = \frac{K'_n W}{2} \underbrace{L}_{\text{effective}} (v_{GS} - V_{TN})^2$$



Channel-Length Modulation

 


- This effect is modeled by adding a term $(1+\lambda v_{DS})$ to the I-V equation:

$$i_D = \frac{K'_n W}{2 L} (v_{GS} - V_{TN})^2 (1 + \lambda v_{DS})$$

λ = channel length modulation parameter




The Role of Body - Body Effect

 

- Channel-body can be regarded as a pn junction
- If channel-body junction is reverse-biased,
 - Depletion layer beneath the gate oxide becomes wider
 - Since the amount of negative charges in the (channel + depletion) layer = amount of positive charges in the gate (Constant for a fixed gate-source voltage)
 - Channel depth is reduced
 - This is equivalent to an increase in the threshold voltage

Body Effect

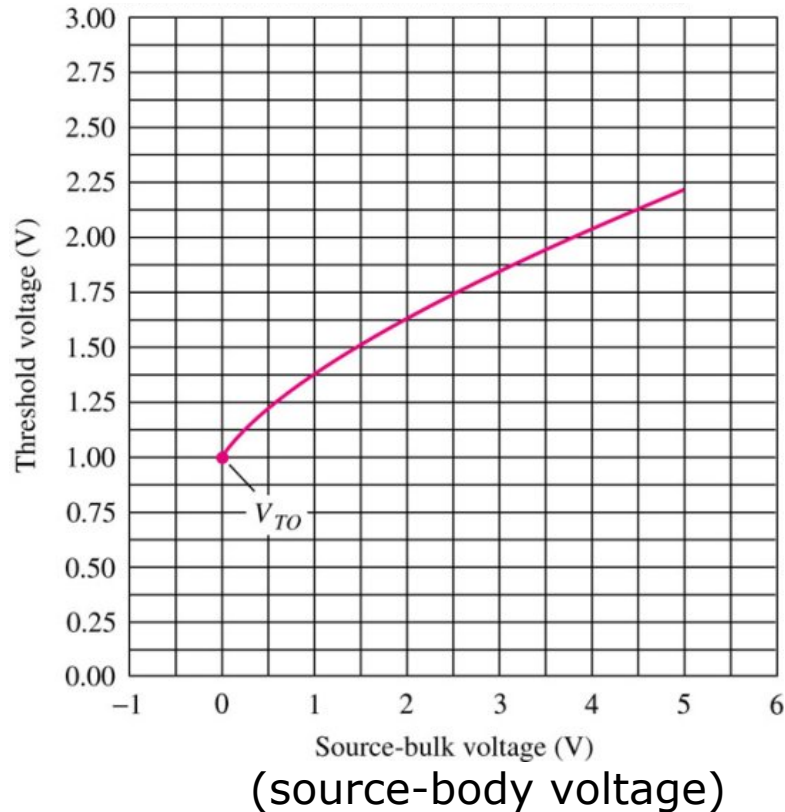

- Non-zero v_{SB} changes threshold voltage:

$$V_{TN} = V_{TO} + \gamma \left(\sqrt{v_{SB} + 2\phi_F} - \sqrt{2\phi_F} \right)$$

where

V_{TO} = zero substrate bias for V_{TN} (V)

γ = body-effect parameter (\sqrt{V})

$2\Phi_F$ = surface potential parameter (V)

It follows that the body voltage controls i_D .

This phenomenon is known as the **body effect**.




Temperature Effects

- V_t and mobility μ are sensitive to temperature:
 - V_t decreases by 2mV for every 1°C rise in temperature
 - mobility μ decreases with temperature
- Overall, increase in temperature results in lower drain currents




Avalanche Breakdown

 

- As V_D is increased, the drain-body junction becomes reversed biased
→ Breakdown occurs at voltages of 20 to 150V
→ Rapid increase in the drain current
- Normally, no permanent damage to the device




Punch-through Breakdown

 

- When V_D is increased to a point, \rightarrow the depletion region surrounding D extends to the S \rightarrow Punch-through breakdown (about 20 V)
- Occurs in devices with short channels
- Normally, no permanent damage to the device




Gate-Oxide Breakdown

 

- When V_{GS} exceeds about 30 V (or lower in modern IC technology) → Gate oxide breaks down like in the case of a capacitor
- Results in permanent damage to the device



Input Protection

 

- Since the MOSFET has a very small input capacitance and a very high input resistance, a small amount of static charges accumulating on the gate can cause the gate voltage to exceed the breakdown level
 - e.g., Electrostatic Discharge (ESD) from human body
- Clamping diodes can be used in the I/O pins to protect the circuit from gate-oxide breakdown






Topics to cover ...

- MOSFET Non-ideal I-V Characteristics
- P-channel Devices and Other types
- DC Analysis of MOSFET circuits
- MOSFET Small Signal Model



P-channel MOSFET (PMOS)

   
- Similar to NMOS, but doping and voltages reversed
 - Body tied to highest voltage (V_{dd}) to prevent forward-biasing pn junctions
 - Source typically tied to V_{dd} too
 - Gate voltage high: transistor is OFF
 - Gate voltage low: transistor is ON when $V_{GS} < V_t$ (threshold voltage)
 - Inverted channel of positively charged holes
 - v_{GS} and v_{DS} are negative and V_t is also negative



Symbols



PMOS I-V Characteristics

 

V_t , v_{GS} and v_{DS} are negative.

→ Cutoff region $|v_{GS}| < |V_t|$

→ Triode region

$$|v_{GS}| \geq |V_t| \quad \text{and}$$

$$|v_{DS}| < |v_{GS} - V_t|$$

→ Saturation region

$$|v_{GS}| \geq |V_t| \quad \text{and}$$

$$|v_{DS}| \geq |v_{GS} - V_t|$$


Cutoff	Triode/Linear	Saturation
$i_D = 0$	$i_D = K_p \left[(v_{GS} - V_t)v_{DS} - \frac{1}{2}v_{DS}^2 \right]$	$i_D = \frac{1}{2}K_p (v_{GS} - V_t)^2$

where $K_p = K_p' \frac{W}{L}$, $K_p' = \mu_p C_{ox}$

μ_p is typically 2 to 3 times lower than μ_n



Complementary MOS (CMOS) Technology

 




PMOS transistor is fabricated in the **n well**

Complementary MOS or CMOS integrated-circuit technologies provide both NMOS and PMOS on a same IC




Depletion-mode MOSFET

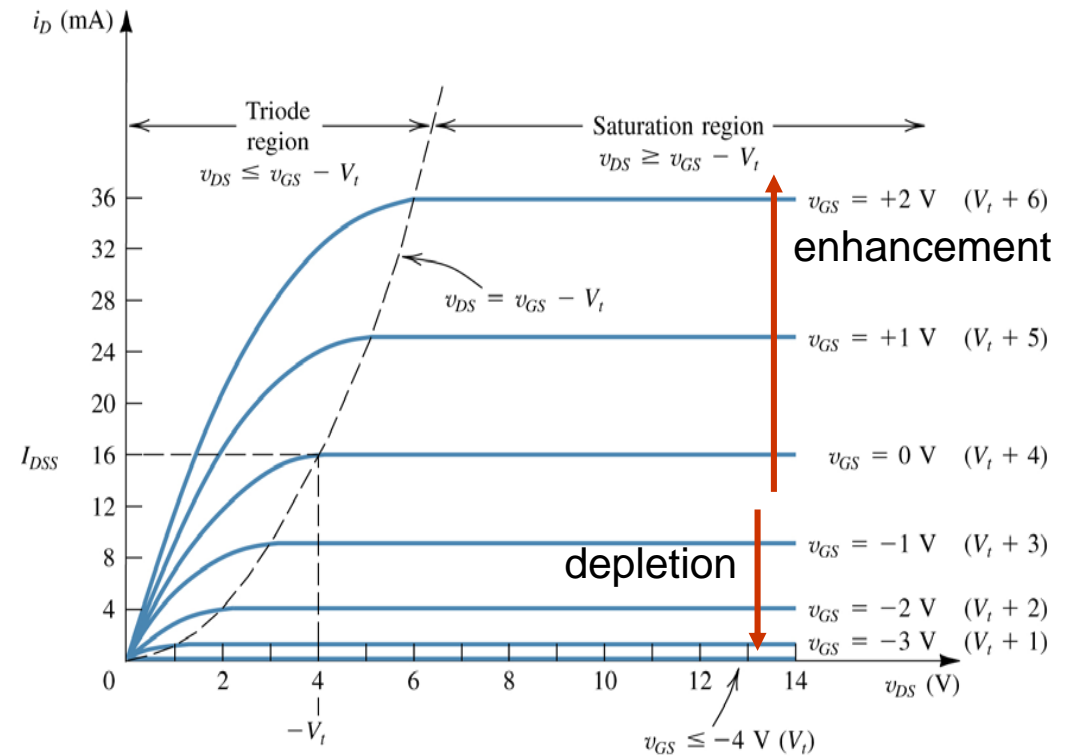  
- A depletion-type MOSFET has a built-in channel by fabrication
 - It is ON when no gate-source voltage is applied
 - Must apply a negative v_{GS} to turn off device
- V_t is negative for NMOS




MOSFET Circuit Symbols

 


(a) NMOS enhancement-mode device

 


(b) PMOS enhancement-mode device

 


(c) NMOS depletion-mode device

 


(d) PMOS depletion-mode device

 


(e) Three-terminal NMOS transistors

 


(f) Three-terminal PMOS transistors

 

 
(g) Shorthand notation—NMOS enhancement-mode device



 (h) Shorthand notation—NMOS depletion-mode device



 (i) Shorthand notation—PMOS enhancement-mode device



(j) Shorthand notation—PMOS depletion-mode device

- (g) and (i) are the most commonly used symbols in VLSI logic design.
- MOS devices are symmetric.
- In NMOS, n^+ region at higher voltage is the drain.
- In PMOS p^+ region at lower voltage is the drain



Topics to cover ...

- MOSFET Non-ideal I-V Characteristics
- P-channel Devices and Other types
- DC Analysis of MOSFET circuits
- MOSFET Small Signal Model




DC Analysis Approach

- Assume an operation mode (usually the saturation mode)
- Use circuit analysis to find V_{GS}
- Use V_{GS} to calculate I_D , and I_D to find V_{DS}
- Check validity of operation region assumptions
- Change assumptions and analyze again if required.



Example 1

 

(a)

Problem: Find Q-pt (I_D , V_{DS})


Assumption: Transistor is saturated.

Analysis: Simplify the circuit,


$$V_{TN} = 1 \text{ V}$$

$$K_n = 25 \mu\text{A/V}^2$$


Thevenin Equivalent

 

Example 1

 

Example 2

 


Problem: Find Q-pt (I_D , V_{DS})

Assumption: Transistor is saturated
(since $V_{DS} = V_{GS}$)



Example 3

 


Problem: Find Q-pt (I_D , V_{DS})

Assumption: transistor is saturated



Example 4 (PMOS)

 


Problem: Find Q-pt (I_D , V_{DS})

Assumption: transistor is saturated (since $V_{DS} = V_{GS}$)



Current Mirror

 Current Mirror is an important building block in IC amplifiers.



As Q_1 must be in saturation mode,

$$I_{D1} = \frac{1}{2} k'_n \left(\frac{W}{L} \right)_1 (V_{GS} - V_t)^2$$

$$I_{D1} = I_{REF} = \frac{V_{DD} - V_{GS}}{R}$$

If Q_2 operates in saturation,

$$I_O = I_{D2} = \frac{1}{2} k'_n \left(\frac{W}{L} \right)_2 (V_{GS} - V_t)^2$$

$$\frac{I_O}{I_{REF}} = \frac{(W/L)_2}{(W/L)_1}$$

If $(W/L)_2 = (W/L)_1$, $I_O = I_{REF}$, output mirrors the input.

Note that channel modulation effect is neglected.



Current Steering Circuit

Once a constant current is generated, it can be replicated to provide dc bias currents for the various amplifier stages in an IC.

Assume Q_2 , Q_3 and Q_5 are in active mode.

$$I_2 = I_{REF} \frac{(W/L)_2}{(W/L)_1}$$

$$I_3 = I_{REF} \frac{(W/L)_3}{(W/L)_1}$$

$$I_5 = I_4 \frac{(W/L)_5}{(W/L)_4} \quad \text{where} \quad I_4 = I_3$$

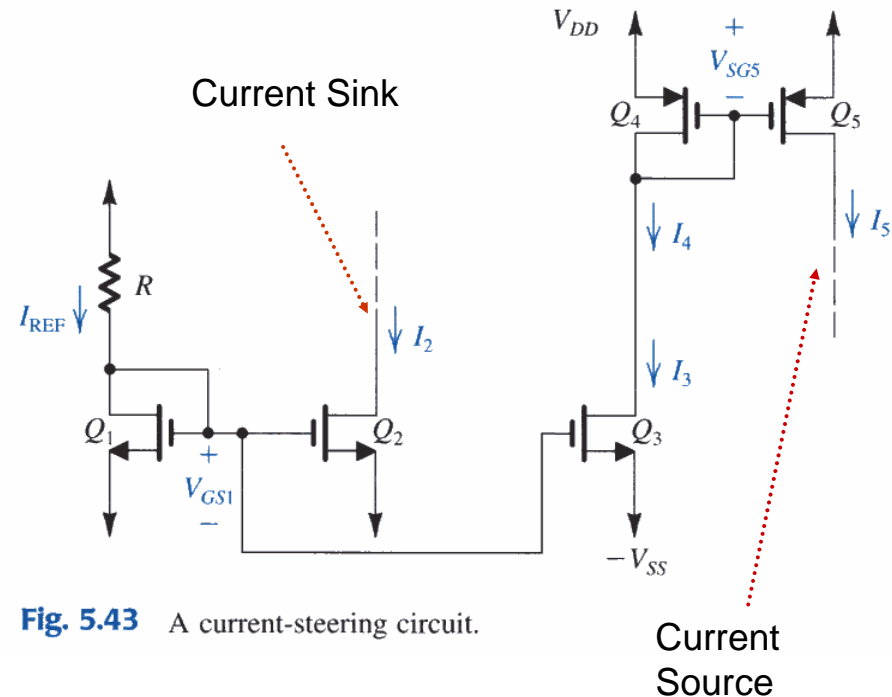


Fig. 5.43 A current-steering circuit.

Current Source



Topics to cover ...

- MOSFET Non-ideal I-V Characteristics
- P-channel Devices and Other types
- DC Analysis of MOSFET circuits
- MOSFET Small Signal Model




Big Picture: Large Signal Analysis

For the conceptual MOSFET amplifier shown right,

$$v_{GS} = V_{GS} + v_{gs}$$
 
$$\begin{aligned} i_D &= \frac{1}{2} k'_n \frac{W}{L} (V_{GS} + v_{gs} - V_t)^2 \\ &= \frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_t)^2 + k'_n \frac{W}{L} (V_{GS} - V_t) v_{gs} + \frac{1}{2} k'_n \frac{W}{L} v_{gs}^2 \end{aligned}$$



For small input signal that $\frac{1}{2} k'_n \frac{W}{L} v_{gs}^2 \ll k'_n \frac{W}{L} (V_{GS} - V_t) v_{gs}$

which results in $v_{gs} \ll 2(V_{GS} - V_t)$ $V_{gs} < 0.2(V_{GS} - V_t)$ is commonly required.

we obtain,
$$i_D = \underbrace{\frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_t)^2}_{I_D} + \underbrace{k'_n \frac{W}{L} (V_{GS} - V_t) v_{gs}}_{i_d}$$




Small Signal Transconductance g_m


$$i_D = \underbrace{\frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_t)^2}_{I_D} + \underbrace{k'_n \frac{W}{L} (V_{GS} - V_t) v_{gs}}_{i_d}$$

→ $g_m = \frac{i_d}{v_{gs}} = k'_n \frac{W}{L} (V_{GS} - V_t)$

Graphic interpretation:

 

Small Signal Model

 

MOSFET small signal model

$$g_m \equiv \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{v_{GS}=V_{GS}} = \frac{i_d}{v_{gs}} = k'_n \frac{W}{L} (V_{GS} - V_t)$$

$$r_o \equiv \left[\left. \frac{\partial i_D}{\partial v_{DS}} \right]_{v_{GS}=V_{GS}} \right]^{-1} = \frac{1 + \lambda V_{DS}}{\lambda I_D} \cong \frac{1}{\lambda I_D}$$

r_o is output resistance due to channel length modulation effect.



Observations on Transconductance

→ Formula 1:
$$g_m = k'_n \frac{W}{L} (V_{GS} - V_t)$$

It shows:

$$g_m \propto k', W/L, \text{ and } (V_{GS} - V_t)$$

→ Formula 2:
$$g_m = \sqrt{2k'_n} \sqrt{\frac{W}{L}} \sqrt{I_D}$$

It shows:

(1) For a given MOSFET,

$$g_m \propto \sqrt{I_D}$$

(2) At a given bias current,

$$g_m \propto \sqrt{W/L}$$

In contrast, the g_m of BJT $\propto I_C$ and is independent of the geometry.

Reference equations:

$$I_D = \frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_t)^2$$

$$(V_{GS} - V_t) = \sqrt{\frac{2I_D}{k'_n \frac{W}{L}}}$$

For BJT:

$$g_m = \frac{I_C}{V_T}$$

→ Formula 3:
$$g_m = \frac{I_D}{(V_{GS} - V_t) / 2}$$

The g_m of MOSFET is much smaller than that of BJT for that the values of $(V_{GS} - V_t)/2$ are at least 0.1V or so.

In spite of their low g_m , MOSFETs have many other advantages, such as high R_{in} , small size, low power dissipation and ease of fabrication.





Modeling the Body Effect

- S-to-B voltage affects threshold voltage and in turn the drain current
- This effect can be modeled by adding a **back-gate transconductance**:

$$g_{mb} = \left. \frac{\partial i_D}{\partial v_{BS}} \right|_{Q\text{-point}} = - \left. \frac{\partial i_D}{\partial v_{SB}} \right|_{Q\text{-point}}$$

$$= - \left(\frac{\partial i_D}{\partial V_{TN}} \right) \left(\frac{\partial V_{TN}}{\partial v_{SB}} \right)_{Q\text{-point}} = \eta g_m$$

  $0 < \eta < 1$ is called back-gate transconductance parameter.



- Body terminal is a reverse-biased diode. Hence, no current flows through it.

