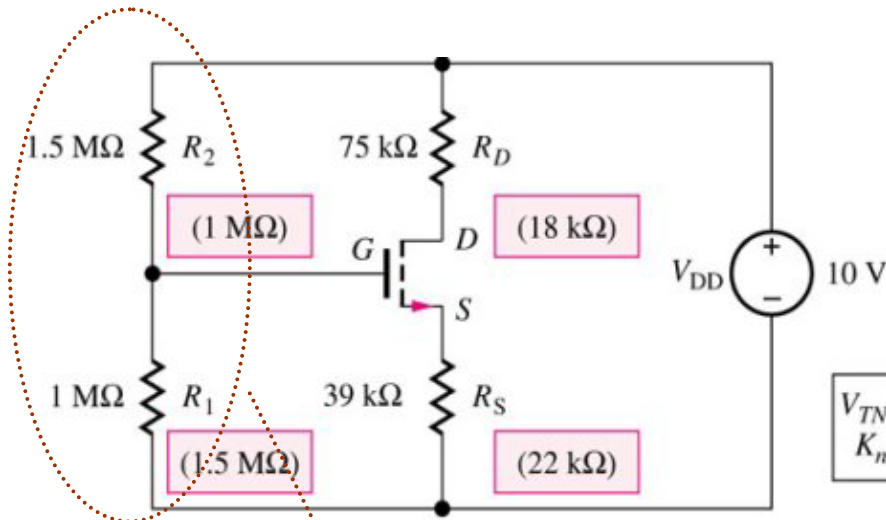


Example 1



(a)

Problem: Find Q-pt (I_D , V_{DS})


Assumption: Transistor is saturated.

Analysis: Simplify the circuit,


$$V_{TN} = 1 \text{ V}$$

$$K_n = 25 \mu\text{A/V}^2$$

Thevenin Equivalent

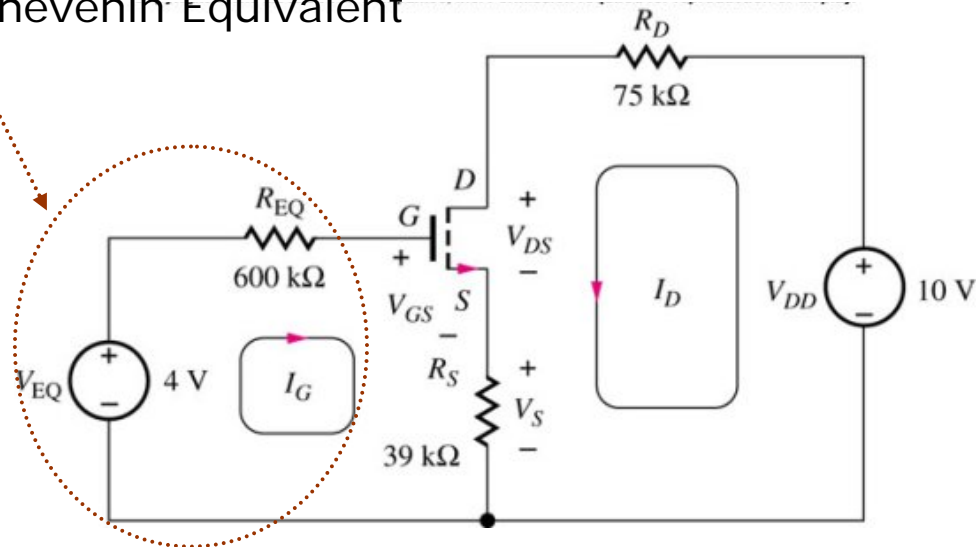

Example 1

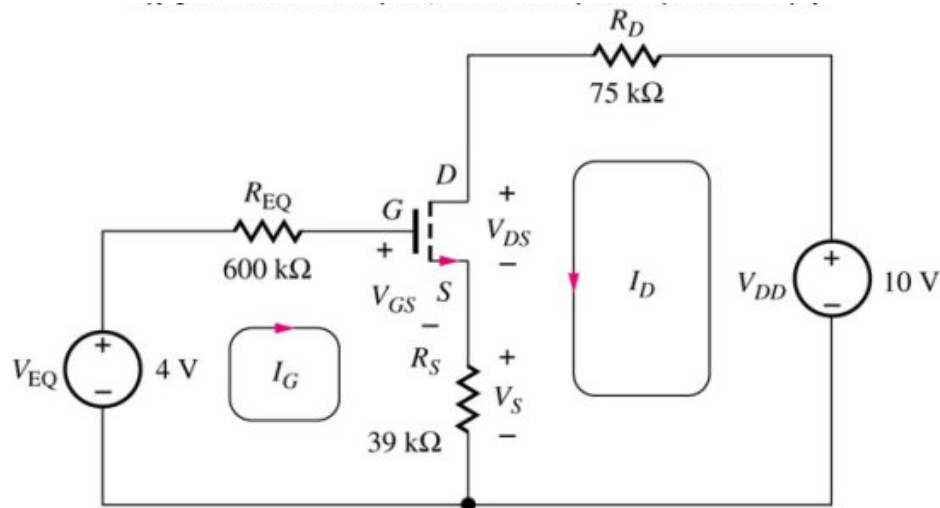

$$\therefore V_{GS} = -2.71\text{V}, +2.66\text{V}$$

Since $V_{GS} < V_{TN}$ for $V_{GS} = -2.71\text{ V}$ and MOSFET will be cut-off,
 $\therefore V_{GS} = +2.66\text{V}$ and $I_D = 34.4\ \mu\text{A}$

Also, $V_{DD} = I_D(R_D + R_S) + V_{DS}$
 $\therefore V_{DS} = 6.08\text{V}$

$V_{DS} > V_{GS} - V_{TN}$. Hence saturation region assumption is correct.

Q-pt: (34.4 μA , 6.08 V) with $V_{GS} = 2.66\text{ V}$

Note: body effect and channel length modulation effect have been neglected.

Since $I_G = 0$, $V_{EQ} = V_{GS} + I_D R_S$


$$V_{EQ} = V_{GS} + \frac{K_n R_S}{2} (V_{GS} - V_{TN})^2$$

$$4 = V_{GS} + \frac{(25 \times 10^{-6})(3.9 \times 10^4)}{2} (V_{GS} - 1)^2$$

$$V_{GS}^2 + 0.05V_{GS} - 7.21 = 0$$



Example 2

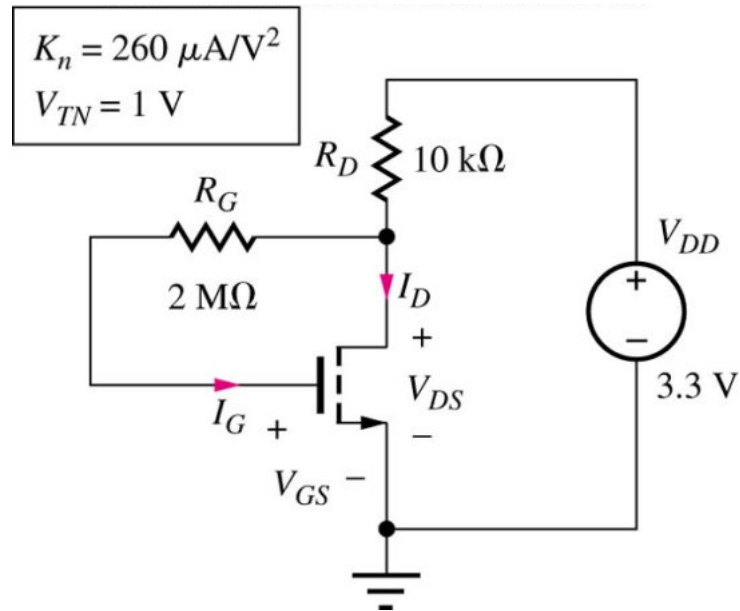

Problem: Find Q-pt (I_D , V_{DS})

Assumption: Transistor is saturated
(since $V_{DS} = V_{GS}$)

Analysis:

$$V_{DS} = V_{DD} - I_D R_D$$

$$V_{GS} = V_{DD} - \frac{K_n R_D}{2} (V_{GS} - V_{TN})^2$$

$$\therefore V_{GS} = 3.3 - \frac{(2.6 \times 10^{-4})(10^4)}{2} (V_{GS} - 1)^2$$

$$\therefore V_{GS} = -0.769 \text{ V}, +2.00 \text{ V}$$

Since $V_{GS} < V_{TN}$ for $V_{GS} = -0.769 \text{ V}$
and MOSFET will be cut-off,


$$V_{GS} = +2.00 \text{ V} \text{ and } I_D = 130 \mu\text{A}$$

$V_{DS} > V_{GS} - V_{TN}$. Hence saturation
region assumption is correct.

Q-pt: (130 μA , 2.00 V)



Example 3

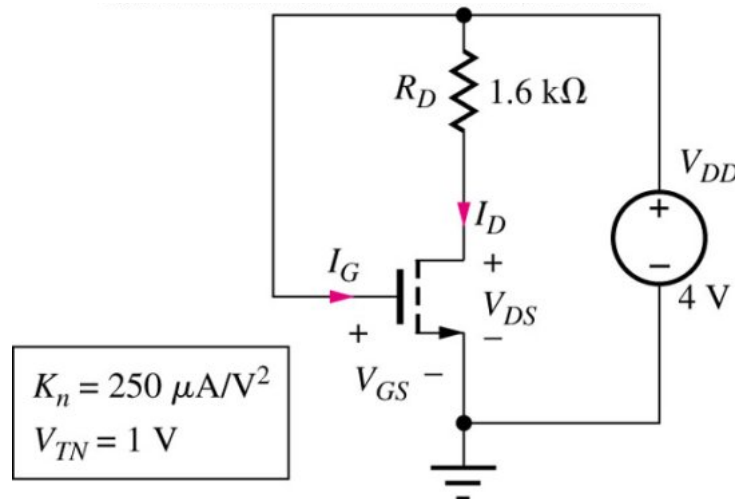

Problem: Find Q-pt (I_D , V_{DS})

Assumption: transistor is saturated

Analysis:

$$V_{GS} = V_{DD} = 4 \text{ V}$$

$$I_D = \frac{250 \mu\text{A}}{2} \frac{(4-1)^2}{\text{V}^2} = 1.13 \text{ mA}$$

Also $V_{DD} = I_D R_D + V_{DS}$

$$\therefore 4 = 1600 I_D + V_{DS}$$

$$\therefore V_{DS} = 2.19 \text{ V}$$

But $V_{DS} < V_{GS} - V_{TN}$. Hence, saturation region assumption is incorrect

Using triode region equation,

$$4 - V_{DS} = 1600 (250) \frac{\mu\text{A}}{\text{V}^2} \left(4 - 1 - \frac{V_{DS}}{2}\right) V_{DS}$$


$$\therefore V_{DS} = 2.3 \text{ V} \text{ and } I_D = 1.06 \text{ mA}$$

$V_{DS} < V_{GS} - V_{TN}$, transistor is in triode region

Q-pt: (1.06 mA, 2.3 V)



Example 4 (PMOS)

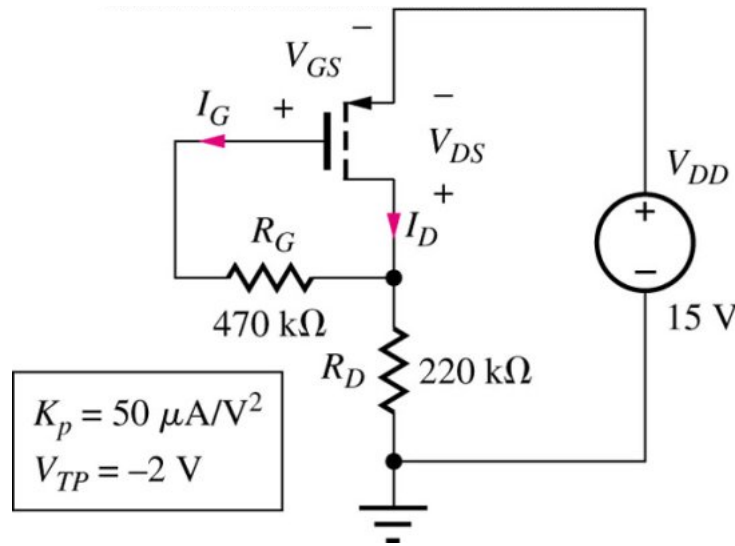

Problem: Find Q-pt (I_D , V_{DS})

Assumption: transistor is saturated (since $V_{DS} = V_{GS}$)

Analysis:

Since $I_G = 0$, $V_{GS} = V_{DS}$

$$\text{Also } 15\text{V} - (220\text{k}\Omega)I_D + V_{DS} = 0$$

$$\therefore 15\text{V} - (220\text{k}\Omega)\frac{50\mu\text{A}}{2\sqrt{2}}(V_{GS} + 2)^2 + V_{GS} = 0$$

$$\therefore V_{GS} = -0.369\text{V}, -3.45\text{V}$$

Since $V_{GS} = -0.369 \text{ V}$ is less than $V_{TP} = -2 \text{ V}$, $V_{GS} = -3.45 \text{ V}$

$$I_D = 52.5 \mu\text{A} \text{ and } V_{GS} = -3.45 \text{ V}$$

$$|V_{DS}| > |V_{GS} - V_{TP}|$$

Hence saturation assumption is correct.

Q-pt: (52.5 μA , -3.45 V)

