Prevention of Voltage Instability

- Excitation Control of Synchronous
 Generators
- Static Reactive Power Compensation
- Need for Reactive Power Reserve

Synchronous Generator Reactive Power Supply Capability

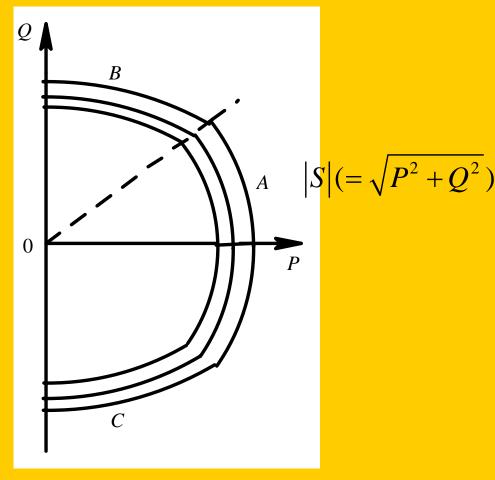


Fig. 10-5 Reactive power supply capability of synchronous generators.

Effect of Current Power Factor on Bus Voltage

$$\overline{V}_{bus} = \overline{V}_{Th} - jX_{Th}\overline{I}$$

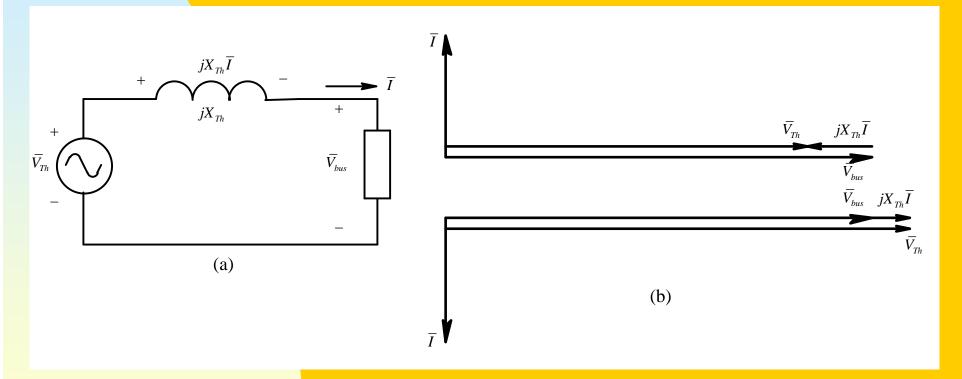


Fig. 10-6 Effect of leading and lagging currents due to the shunt compensating device.

Static Var Compensators (SVC)

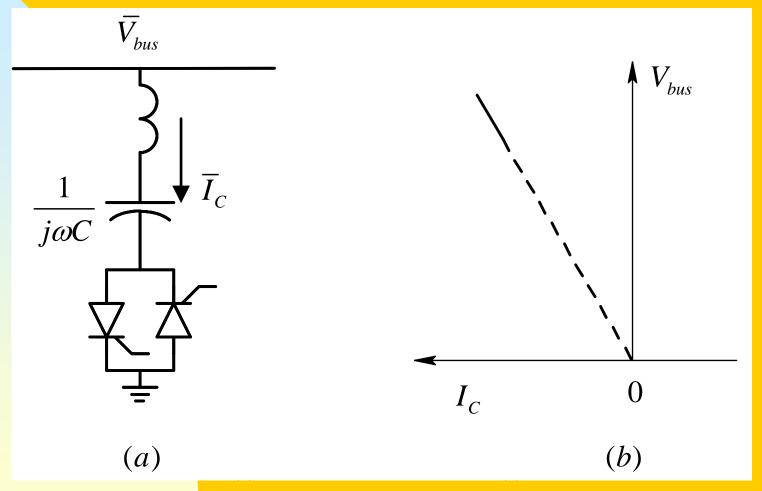


Fig. 10-7 V-I characteristic of SVC.

Thyristor Controlled Reactors (TCR)

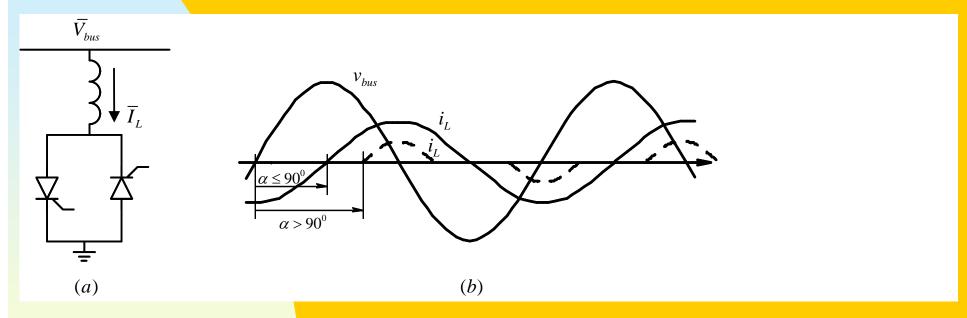


Fig. 10-8 Thyristor-Controlled Reactor (TCR).

Voltage Control by SVC and TCR Combination

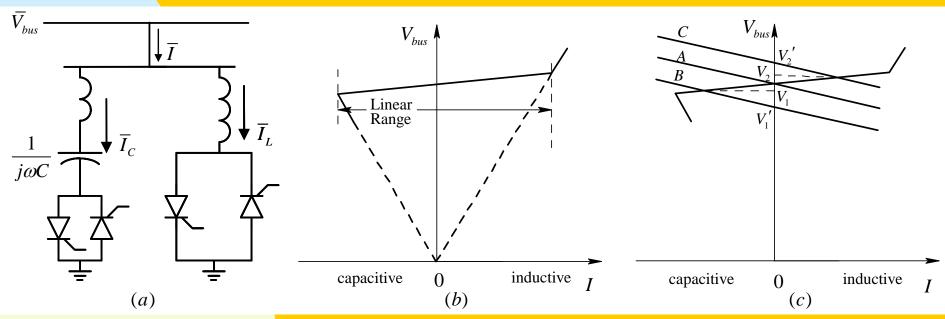


Fig. 10-9 Parallel combination of SVC and TCR.

STATCOM

$$\overline{V}_{conv} = \overline{V}_{bus} - jX\overline{I}_{conv}$$

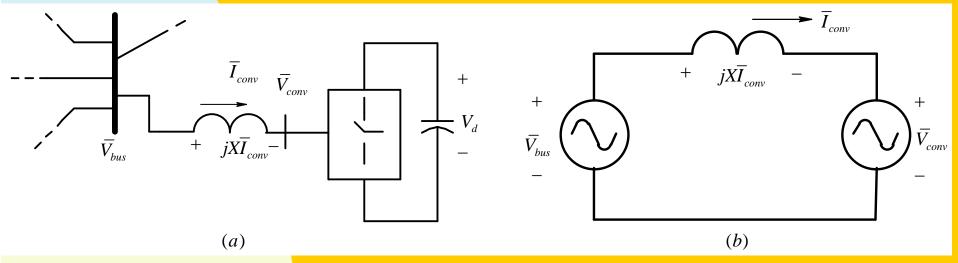


Fig. 10-10 STATCOM.

STATCOM V-I Characteristic

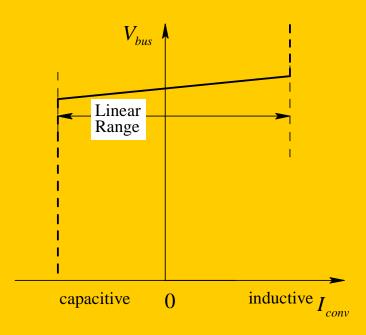


Fig. 10-11 STATCOM VI characteristic.

Thyristor-Controlled Series Capacitor (TCSC)

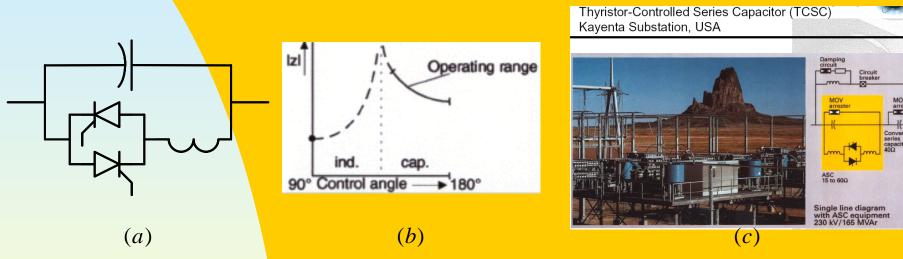


Fig. 10-12 Thyristor-Controlled Series Capacitors (TCSC) [source: Siemens Corp.].

Summary

- Importance
- Radial System Example
- Voltage Collapse
- Prevention of Voltage Stability
- Synchronous Generators
- Static Reactive Power Compensators