

# *ELE 2110A Electronic Circuits*

## *Week 12: Output Stages, Frequency Response*

(2 hours only)



# Topics to cover ...

- Output Stages
- Amplifier Frequency Response

Reading Assignment:

Chap 15.3, 16.1 of Jaeger and Blalock or  
Chap 14.1 – 14.4 of Sedra & Smith




# Multistage Amplifiers

Practical amplifiers usually consist of a number of stages connected in cascade.

- The first (input) stage is usually required to provide
  - a high input resistance
  - a high common-mode rejection for a differential amplifier
- Middle stages are to provide
  - majority of voltage gain
  - conversion of the signal from differential mode to single-end mode
  - shifting of the dc level of the signal
- The last (output) stage is to provide
  - a low output resistance in order to
    - avoid loss of gain and
    - provide the current required by the load (power amplifiers)



# Example

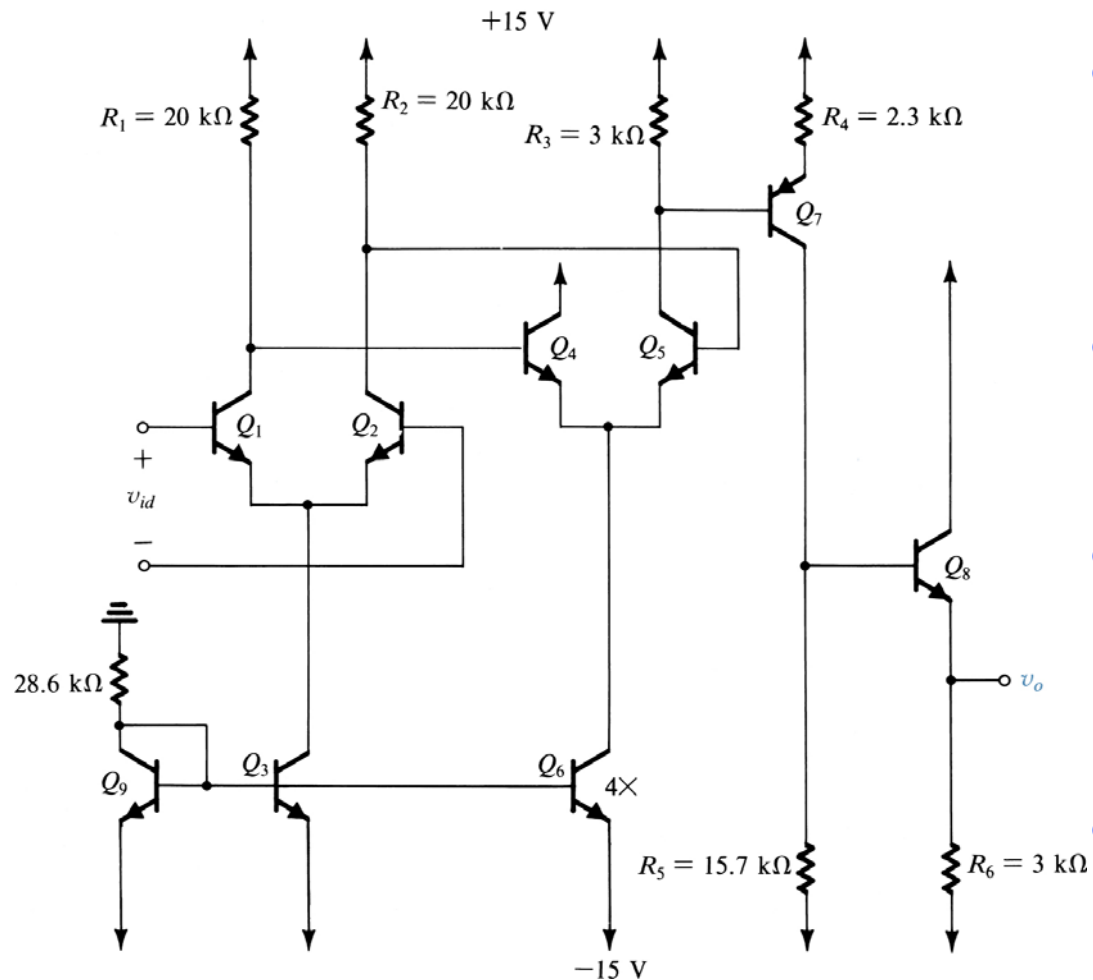

- The input stage ( $Q_1, Q_2$ ) is differential-in and differential-out
  - biased by current source  $Q_3$
- ( $Q_4, Q_5$ ) is a differential-in and single-ended-out stage
  - biased by current source  $Q_6$
- $Q_7$  provides
  - additional gain
  - shifting the dc level of the signal
- The output stage  $Q_8$  is an emitter follower




# Output Stages

- Function of an output stage is
  - To provide a low output resistance so that it can deliver the output signal to the load without loss of gain
- Requirements of an output stage:
  - Large input signal range
    - b/c it is the final stage of the amplifier, and usually deals with relatively large signals.
    - Small-signal approximations and models either are not applicable or must be used with care.
  - Low distortion
  - High power efficiency



# Classification of Output Stages

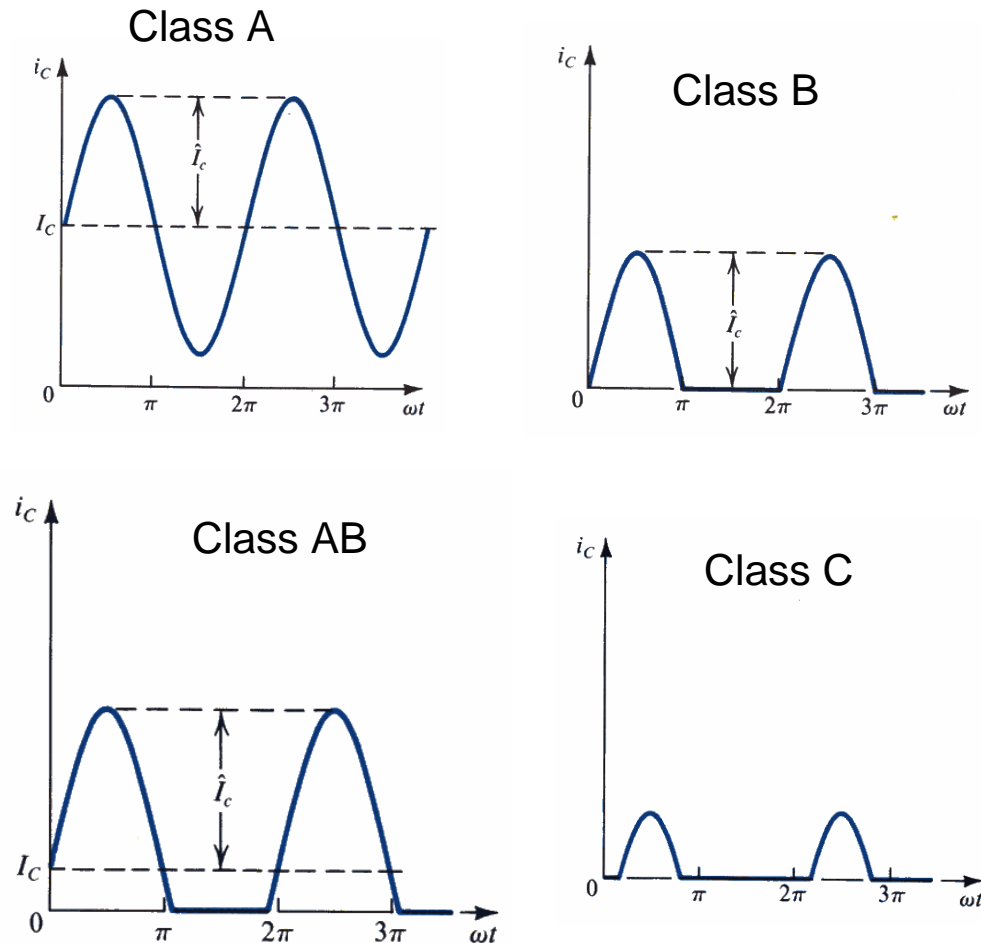


Collector or Drain current waveforms of different output stages

- Class A: the transistor conducts for the entire cycle of the input signal
- Class B: the transistor conducts for only half the cycle
- Class AB: conduction cycle is greater than  $180^\circ$  and less than  $360^\circ$ 
  - Used for opamp output stage and audio power amplifiers
- Class C: conduction cycle is less than  $180^\circ$ 
  - Used for radio-frequency (RF) power amplifications (mobile phones, radio and TV)


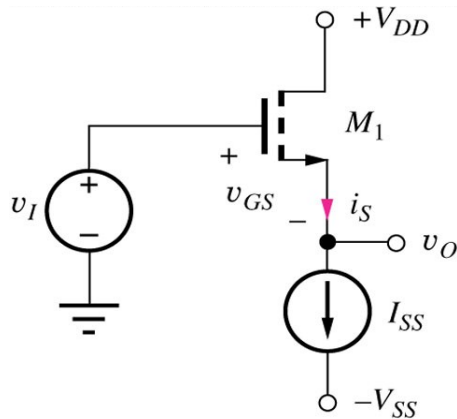
# Class-A Amplifier: Source/Emitter Follower



For a source follower biased by an ideal current source,  $v_{GS}$  is fixed and

$$v_O = v_I - V_{GS1} = v_I - \left( V_{TN} + \sqrt{\frac{2I_{SS}}{K_n}} \right)$$

Input range:


$$-V_{SS} + V_{GS} \leq v_I \leq V_{DD} + V_{TN}$$

Output range:


$$-V_{SS} \leq v_O \leq V_{DD}$$

The largest output voltage is
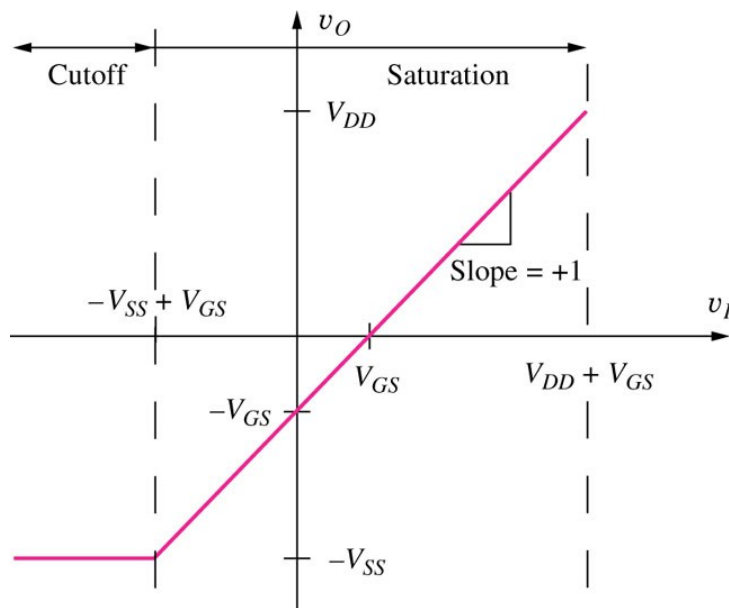
$$v_O \cong V_{DD} \sin \omega t \quad (\text{if } V_{SS} = V_{DD})$$



# Source Emitter with Load

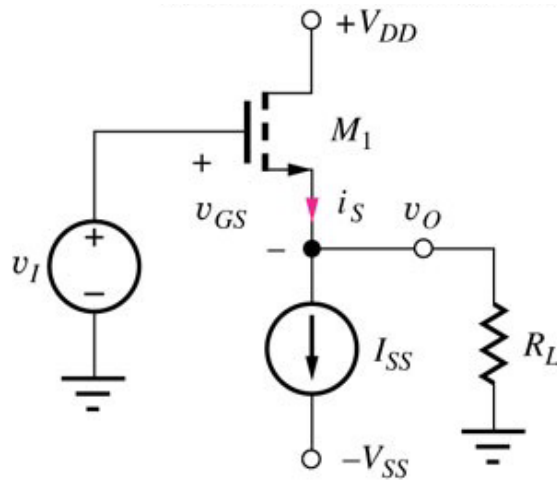

To maintain class A operation,  
 $i_s > 0$  at all times:

$$\therefore i_S = I_{SS} + \frac{v_o}{R_L} \geq 0$$

$$v_o \geq -I_{SS} R_L$$

For largest output amplitude:  $v_o \cong V_{DD} \sin \omega t$

We have:  $V_{DD} \sin \omega t \geq -I_{SS} R_L$  for all  $t$

The lowest value for the LHS occurs when  $\sin \omega t = -1$ ,


$$\therefore V_{DD} \leq I_{SS} R_L$$

$$\therefore I_{SS} \geq \frac{V_{DD}}{R_L}$$





# Power Efficiency

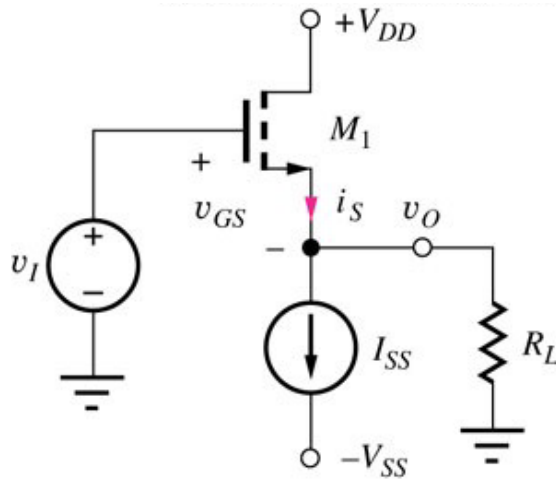

The largest output voltage is

$$v_O \cong V_{DD} \sin \omega t$$

Average power supplied to the source follower:

$$P_{av} = \frac{1}{T} \int_0^T \left[ I_{SS} (V_{DD} + V_{SS}) + \left( \frac{V_{DD} \sin \omega t}{R_L} \right) V_{DD} \right] dt$$

$$= I_{SS} (V_{DD} + V_{SS}) = 2I_{SS} V_{DD} \quad (\text{if } V_{SS} = -V_{DD})$$

Average power delivered to the load:

$$P_{ac} = \frac{\left( \frac{V_{DD}}{\sqrt{2}} \right)^2}{R_L} = \frac{V_{DD}^2}{2R_L}$$

Efficiency of amplifier is:

$$\zeta = \frac{P_{ac}}{P_{av}} = \frac{V_{DD}^2 / (2R_L)}{2I_{SS} V_{DD}}$$



$$\leq \frac{V_{DD}^2 / (2R_L)}{2 \left( \frac{V_{DD}}{R_L} \right) V_{DD}} = 25\%$$

$$I_{SS} \geq \frac{V_{DD}}{R_L}$$

- Low efficiency



# Push-Pull Operation: Class B

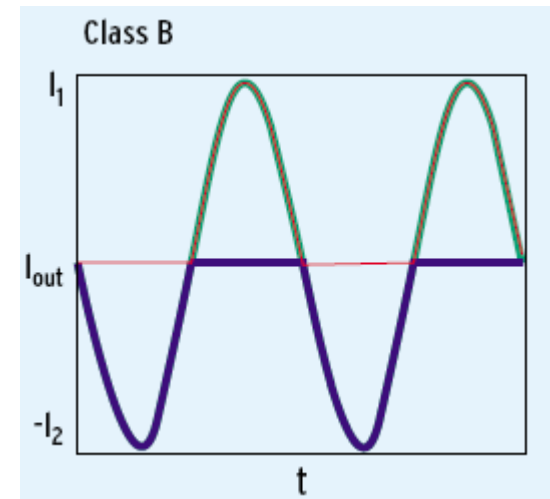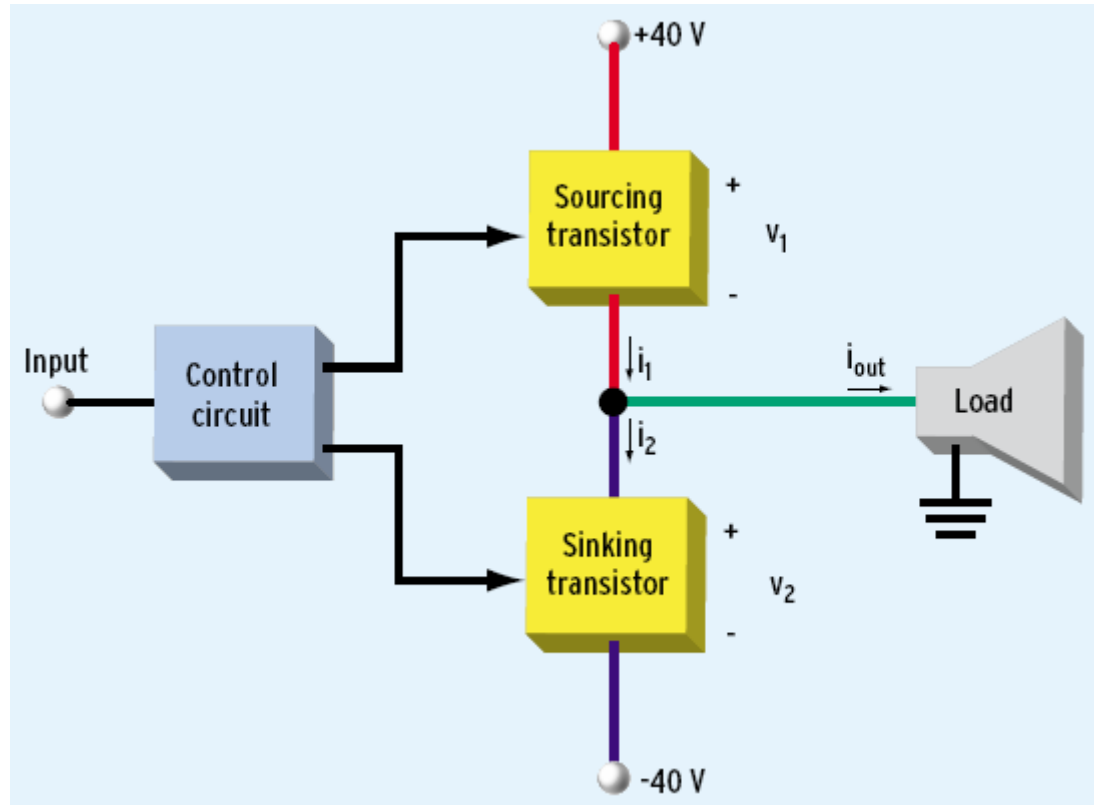


When a push-pull amplifier is operated in Class B, all of the output current comes either from the current-sourcing transistor or from the current-sinking device but never from both at the same time.

Source: B. Putzeys, "Digital Audio's final frontier", IEEE Spectrum, Mar 2003.



# Class-B Amplifier

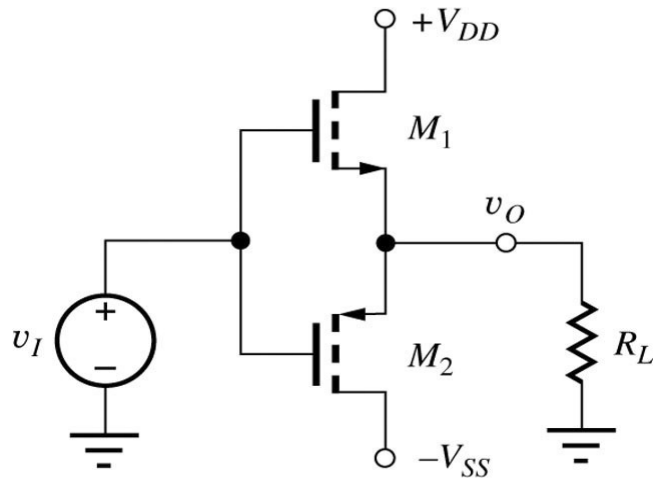

- A complementary pair of source followers biased at zero source current

- When




$$V_{TP} \leq v_I \leq V_{TN}$$

neither transistor conducts

- No quiescent (DC) current consumption!





# Class-B Amplifier

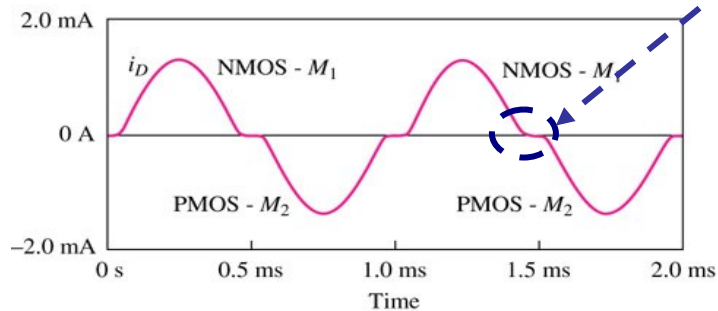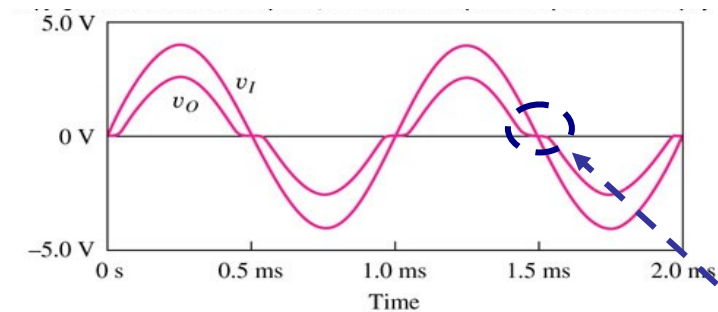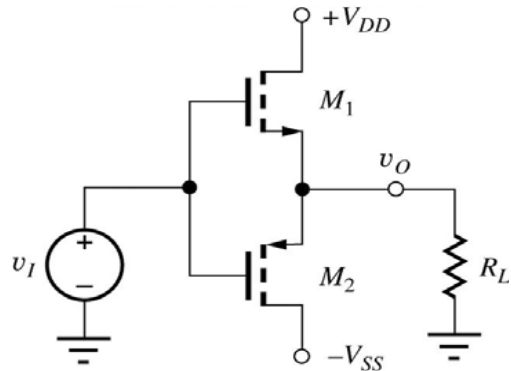

- When  $V_I > V_{TN}$ ,
  - $M_1$  turns on and acts as an source follower,  $v_o \approx v_i - V_{TN}$
  - $M_2$  off
- When  $V_I < V_{TP}$ ,
  - $M_2$  turns on and acts as an source follower,  $v_o \approx v_i - V_{TP}$
  - $M_1$  off
- Power efficiency is high, can be up to about 80%
- Disadv.: Output waveform suffers from a dead-zone → Large distortion



# Class AB

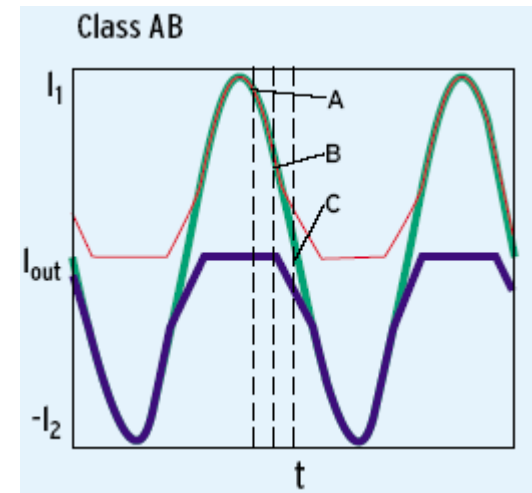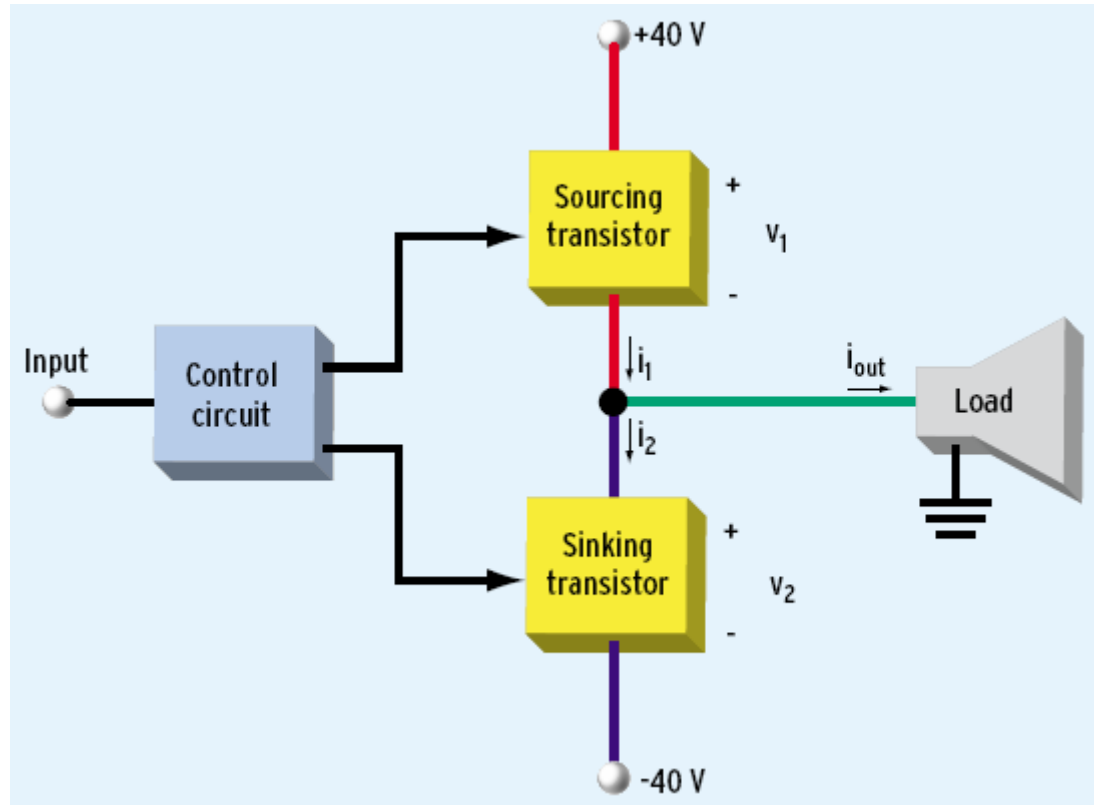


Class AB exhibits less distortion by allowing the transistors to work together when the output signal is near zero, in what is called the crossover region.

Source: B. Putzeys, "Digital Audio's final frontier", IEEE Spectrum, Mar 2003.



# Class-AB Amplifiers


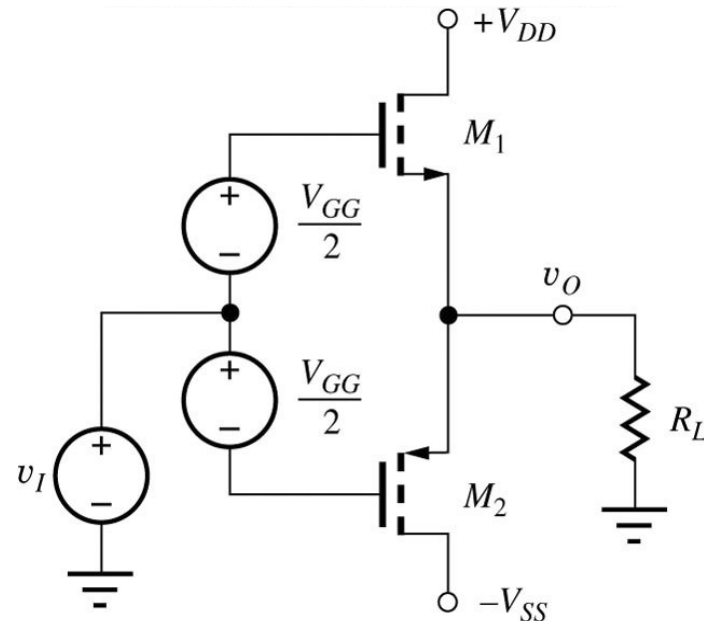


- Remove dead zone by biasing transistors into conduction but at a low quiescent current level
  - Distortion less than Class-B but worse than Class-A amplifier
- For each transistor,  $180^\circ < \text{conduction angle} < 360^\circ \rightarrow$  Class AB amplifier
- Power efficiency lower than Class-B but higher than Class-A amplifier



# Class-AB Amplifiers

Biasing examples:

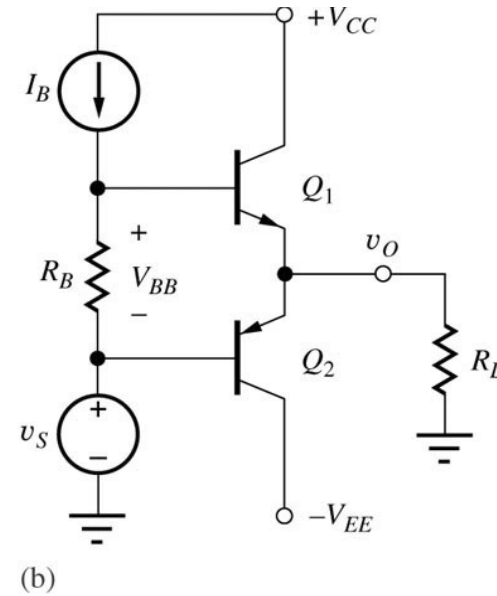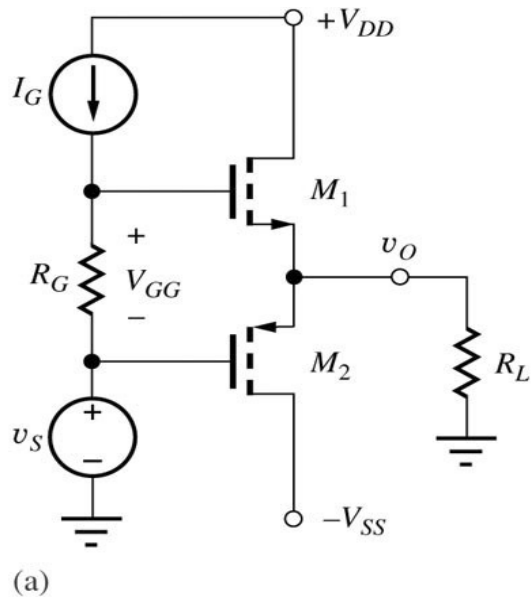

DC currents:

$$I_D = \frac{K_n}{2} \left( \frac{V_{GG}}{2} - V_{TN} \right)^2$$

$$I_C = I_S \exp \left( \frac{I_B R_B}{2V_T} \right)$$



# Topics to cover ...

- Output Stages


- Amplifier Frequency Response





# Frequency Response of Amplifiers

A typical amplifier:

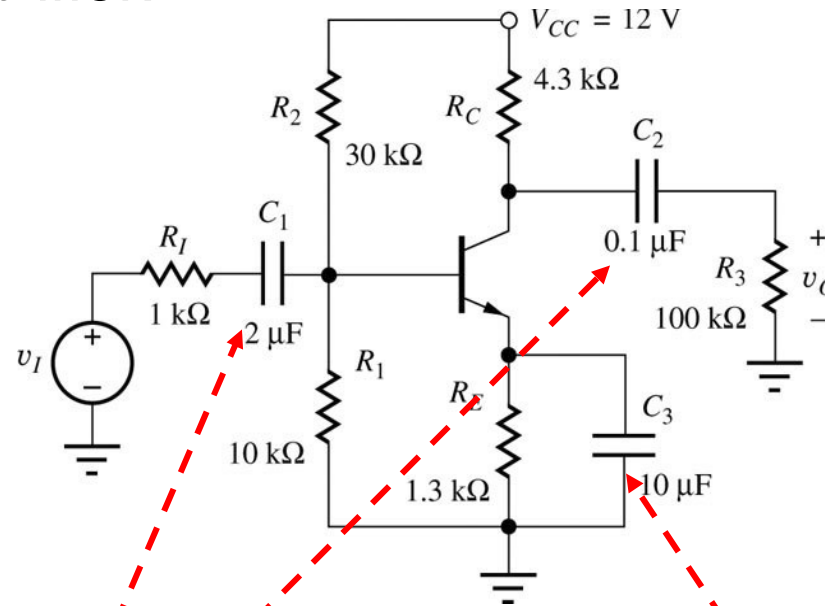


Block DC and low frequency signals

By-pass high frequency currents

Amplifier's gain is frequency dependent!




# Typical Amplifier Transfer Function

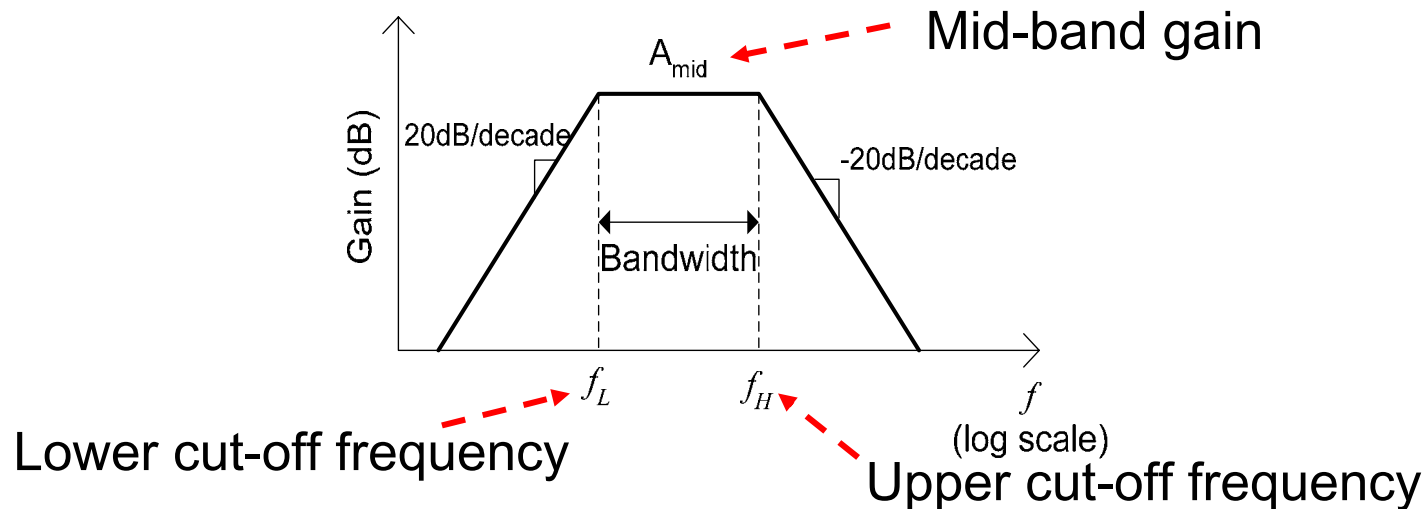

- In low frequency side, drop in gain is caused by coupling and bypass capacitors
- In high frequency side, drop in gain is caused by transistor's parasitic capacitors
  - More on this topic later
- In the mid-band range, no capacitors are in effect:
  - Coupling and bypass capacitors are short circuits
  - Transistor parasitic capacitors are open circuits


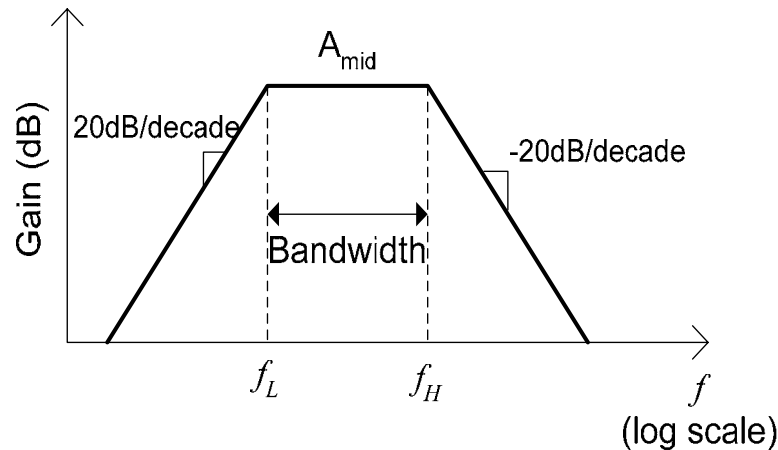
# Estimate $f_L$ : Short-Circuit Time Constant Method



- Lower cutoff frequency for a network with  $n$  coupling and bypass capacitors can be estimated by:



$$\omega_L \cong \sum_{i=1}^n \frac{1}{R_{iS} C_i}$$
$$f_L = \omega_L / 2\pi$$

$R_{iS}$  = resistance at terminals of  $i^{\text{th}}$  capacitor  $C_i$  with all other capacitors replaced by short circuits.

Product  $R_{iS} C_i$  is “short-circuit time constant” associated with  $C_i$ .



# SCTC: Example

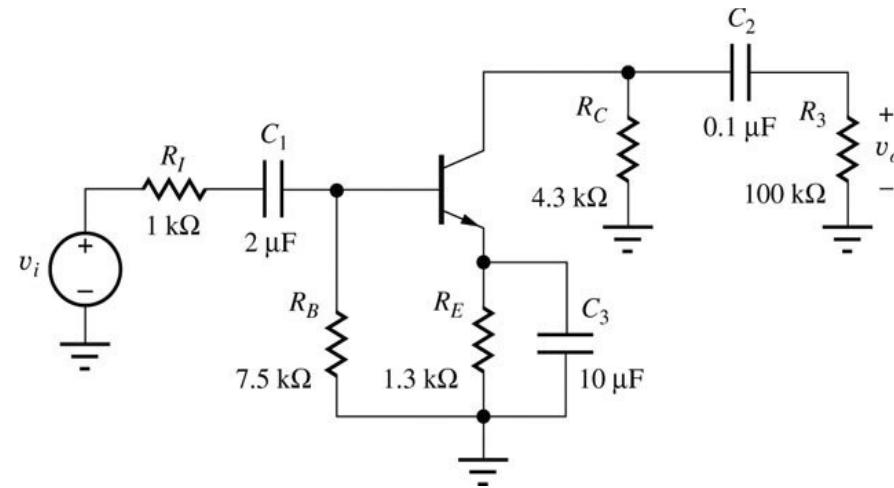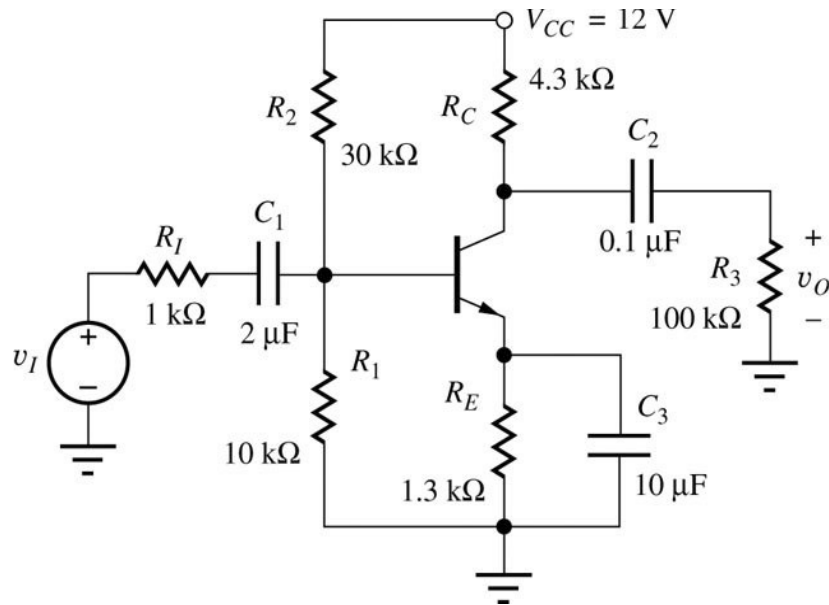

$\beta = 100$  and  $V_A = 75V$   
 Q-point: (1.73mA, 2.32V)

AC equivalent with **finite**  
 coupling capacitances


BJT small signal parameters:

$$r_\pi = \frac{V_T}{I_B} = \frac{25mV}{1.73mA/100} = 1.45k\Omega$$


$$r_o = \frac{V_A + V_{CE}}{I_C} = \frac{75V + 2.32V}{1.73mA} = 44.7k\Omega$$



# Time Constant Associated with $C_1$

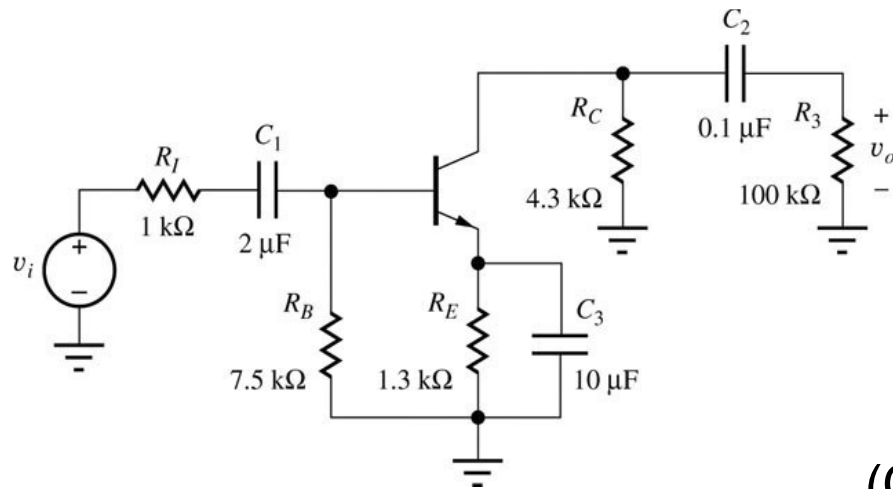

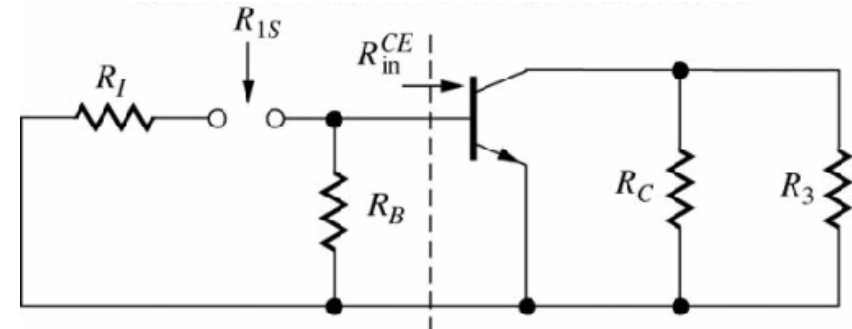To find the time constant associated with  $C_1$ :



( $C_2$  and  $C_3$  are short-circuited and set  $v_i = 0$ )


$$R_{1s} = R_I + (R_B \parallel R_{in}^{CE}) = R_I + (R_B \parallel r_{\pi})$$

$$R_{1s} = 1000\Omega + (7500\Omega \parallel 1450\Omega) = 2220\Omega$$


$$\frac{1}{R_{1s} C_1} = \frac{1}{2.22k\Omega \cdot 2\mu F} = 225 \text{ rad/s}$$



# Time Constant Associated with $C_2$

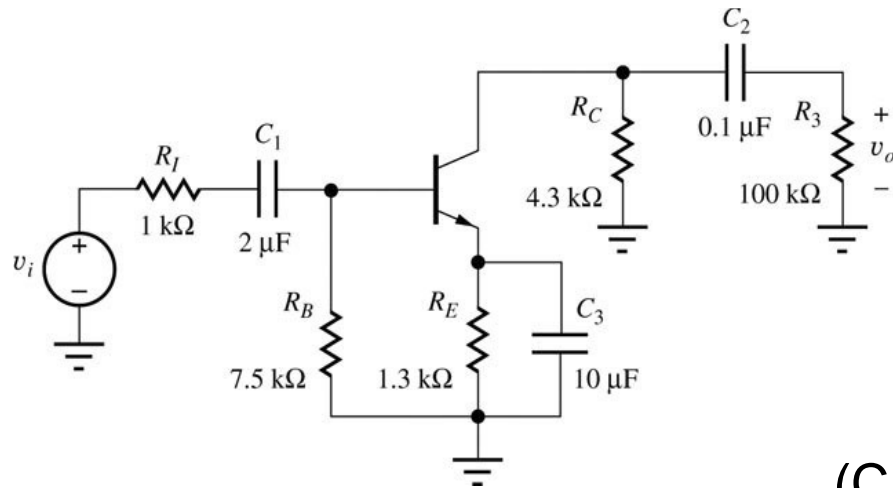

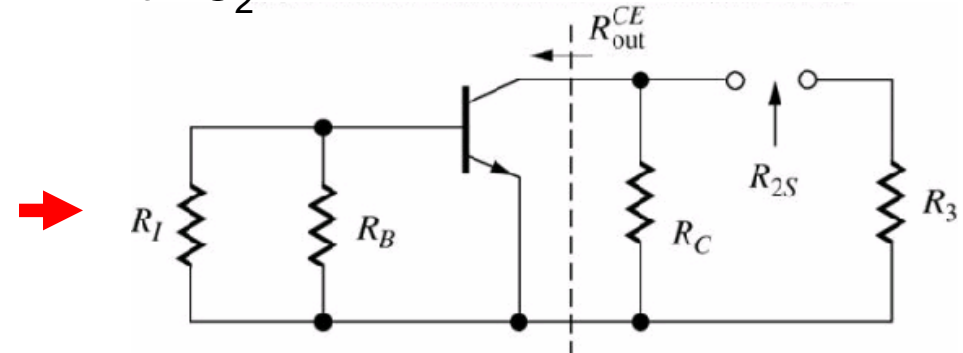To find the time constant associated with  $C_2$ :



( $C_1$  and  $C_3$  are short-circuited and set  $v_i = 0$ )


$$R_{2S} = R_3 + (R_C \parallel R_{out}^{CE}) = R_3 + (R_C \parallel r_o) \cong R_3 + R_C$$

$$R_{2S} = 100k\Omega + (4.3k\Omega \parallel 44.7k\Omega) = 104k\Omega$$

$$\frac{1}{R_{2S}C_2} = \frac{1}{104k\Omega \cdot 0.1\mu F} = 96.1 \text{ rad/s}$$



# Time Constant Associated with $C_3$

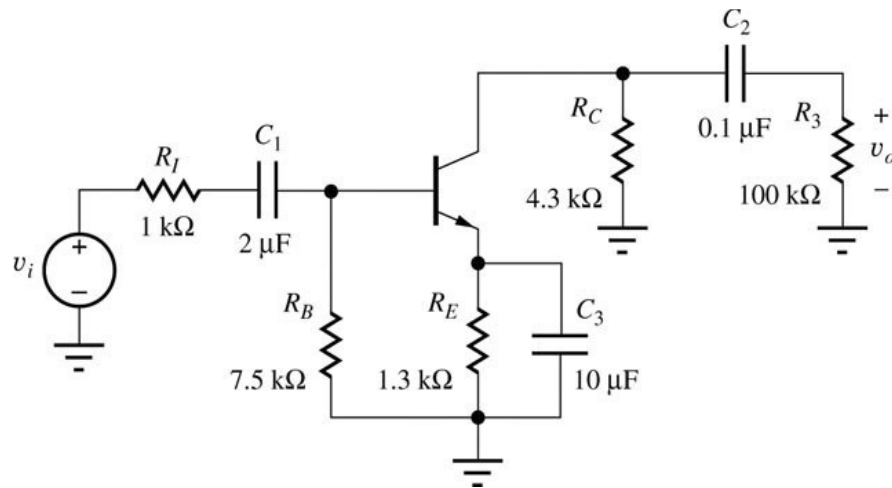

$$R_{3S} = R_E \parallel R_{out}^{CC} = R_E \parallel \frac{r_{\pi} + R_{th}}{\beta + 1}$$


$$= R_E \parallel \frac{r_{\pi} + (R_I \parallel R_B)}{\beta + 1}$$

To find the time constant associated with  $C_3$ :



$$R_{3s} = 1300k\Omega \parallel \frac{1450V + 1000\Omega \parallel 7500\Omega}{101}$$

$$= 22.7\Omega$$

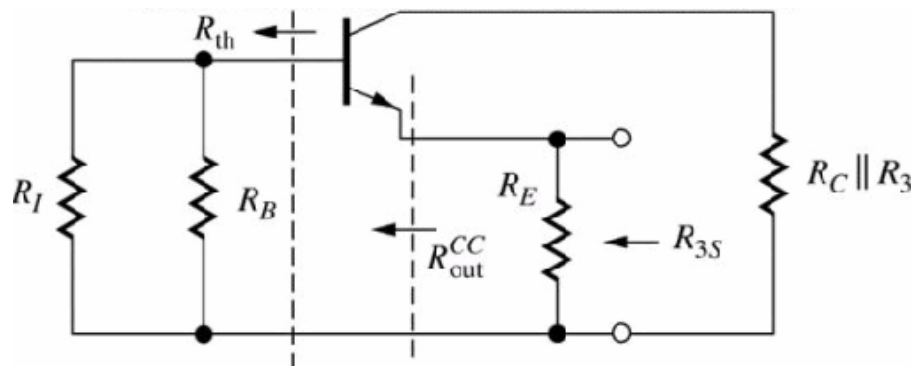

$$\frac{1}{R_{3s} C_2} = \frac{1}{22.7k\Omega \cdot 10\mu F} = 4410 \text{ rad/s}$$

( $C_1$  and  $C_2$  are short-circuited and set  $v_i = 0$ )



# Lower Cutoff Frequency

The lower cutoff frequency is:

$$\omega_L \cong \sum_{i=1}^3 \frac{1}{R_{iS} C_i} = 225 + 96.1 + 4410 = 4730 \text{ rad/s}$$

and


$$f_L = \frac{\omega_L}{2\pi} = 753 \text{ Hz}$$

In this example the time constant associated with the bypass capacitor  $C_3$  is dominant.






# High Frequency Response

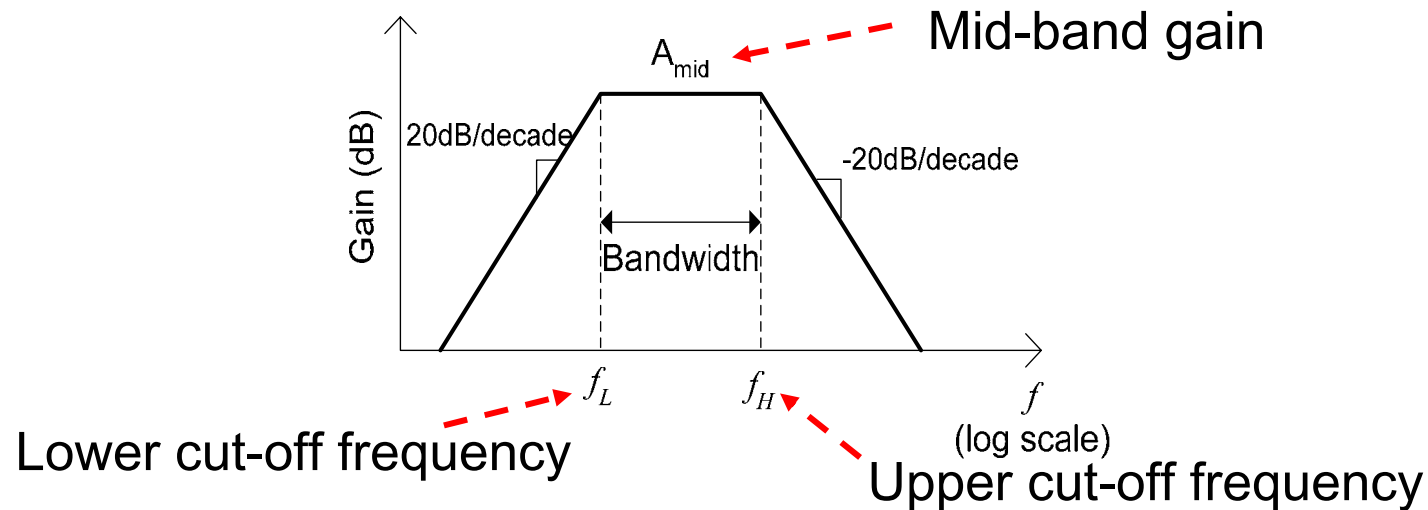

- At high frequency side, drop in gain is caused by transistor's parasitic capacitors


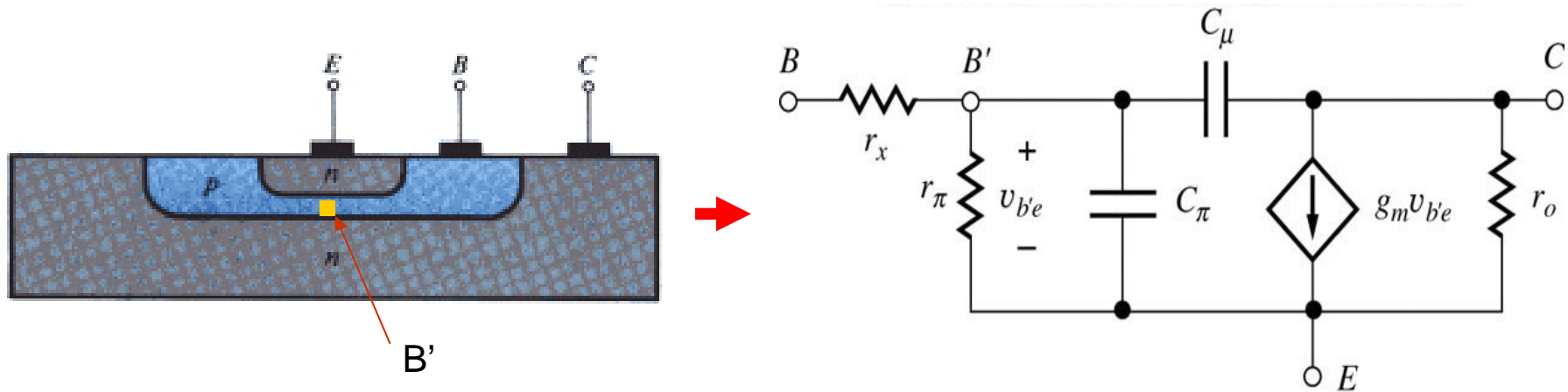
# High Frequency Small Signal Model for BJT



Model for active mode BJT



$C_\pi$ : diffusion capacitance of the forward-biased base-emitter junction.

$C_\mu$ : depletion capacitance of the reverse-biased base-collector junction.

$r_x$ : the resistance of the silicon material of the base region between the base terminal and the intrinsic base terminal B' that is right under the emitter region.


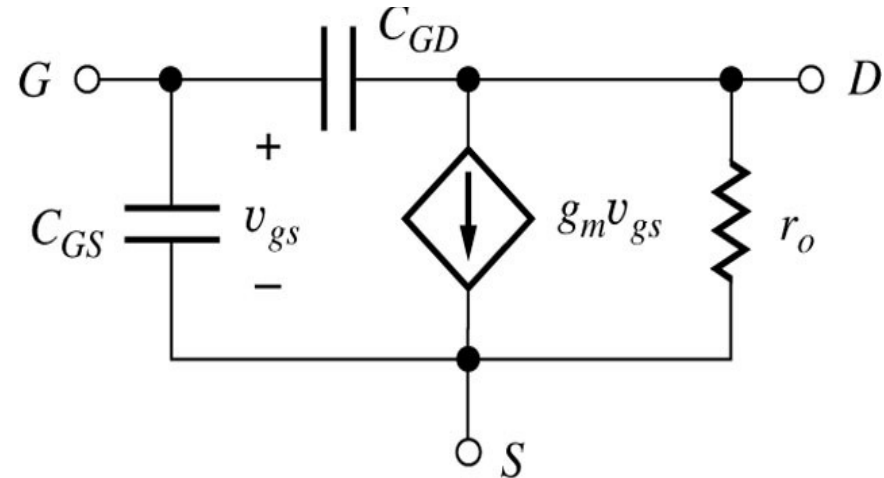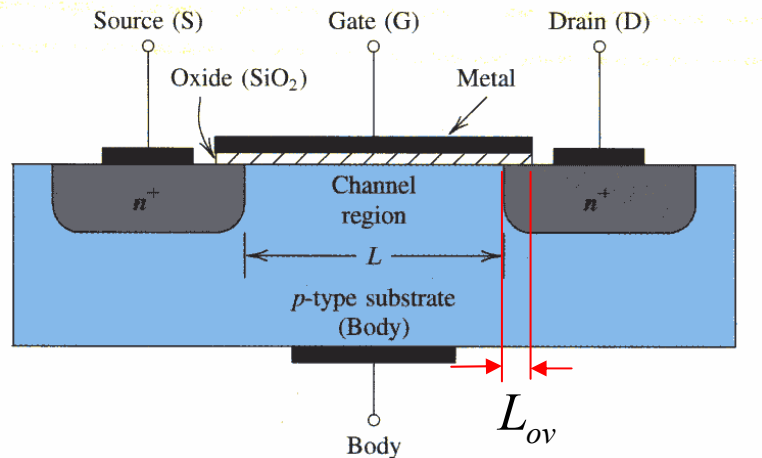
# High-frequency Small Signal Model for MOSFET




Model for saturation mode MOSFET

$C_{gs} = \frac{2}{3}WLC_{ox}$  = the capacitance between the Gate and the conducting channel.

$C_{gd} = C_{ov} = WL_{ov}C_{ox}$  = the overlap capacitance (very small).


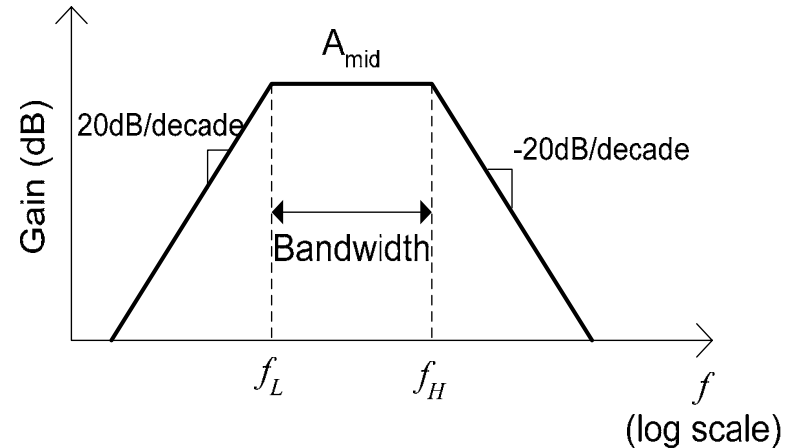
# Open-Circuit Time Constant Method to Determine $f_H$




$f_H$  can be estimated by open-circuit time constant method:

$$\omega_H \cong \frac{1}{\sum_{i=1}^m R_{io} C_i}, \quad f_H = \omega_H / 2\pi$$

where  $R_{io}$  is resistance at terminals of  $i^{\text{th}}$  capacitor  $C_i$  with all other capacitors open-circuited.


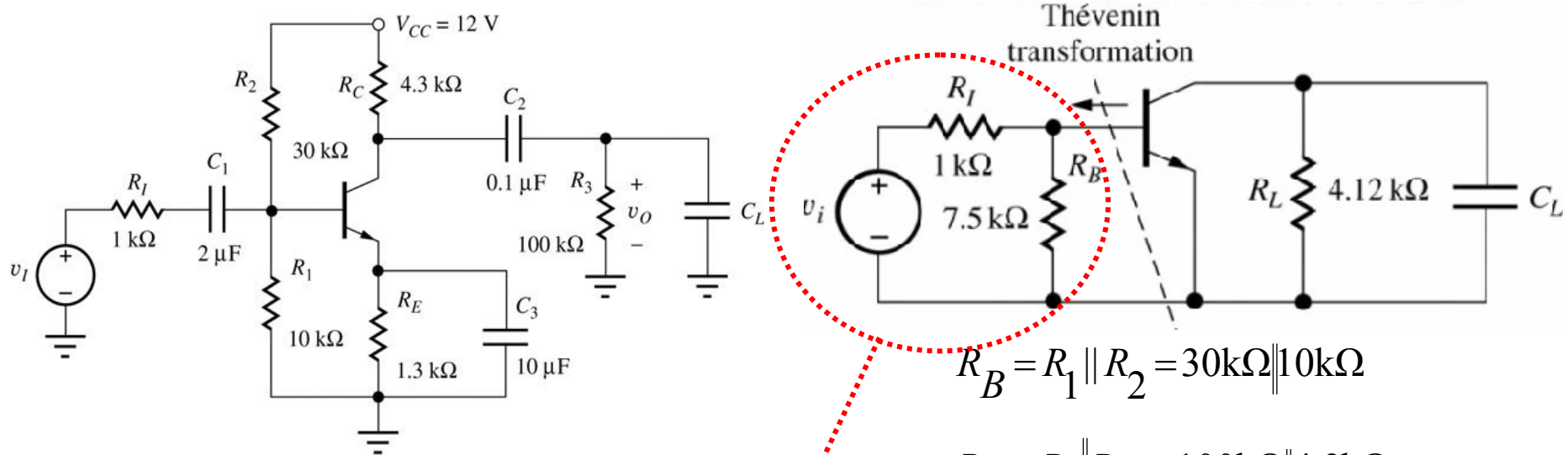
# High Frequency Analysis of C-E Amplifier



$$R_B = R_1 \parallel R_2 = 30\text{k}\Omega \parallel 10\text{k}\Omega$$


$$R_L = R_3 \parallel R_C = 100\text{k}\Omega \parallel 4.3\text{k}\Omega$$

$\beta = 100$  and  $V_A = 75\text{V}$   
 Let Q-point be (1.6mA, 3V)

$$C_\pi = 19.9\text{pF}$$

$$C_\mu = 0.5\text{pF}$$

$$r_x = 250\Omega$$

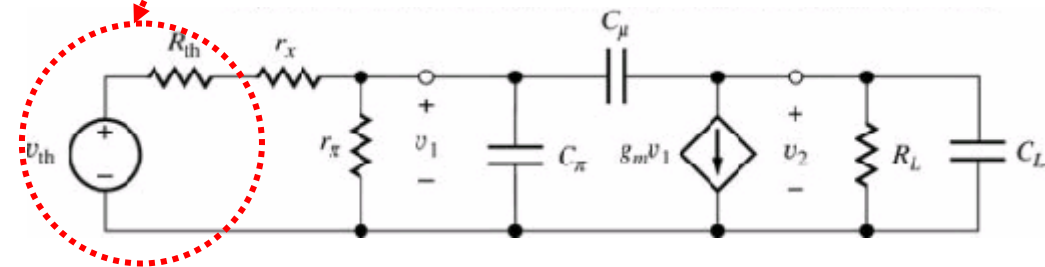


$$v_{th} = v_i \frac{R_B}{R_I + R_B}$$


$$R_{th} = \frac{R_I R_B}{R_I + R_B} = 882\Omega$$



# High Frequency Small Signal Equivalent

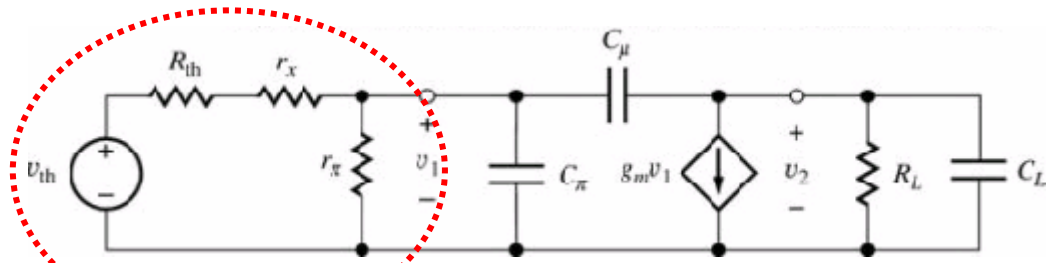

Norton source transformation

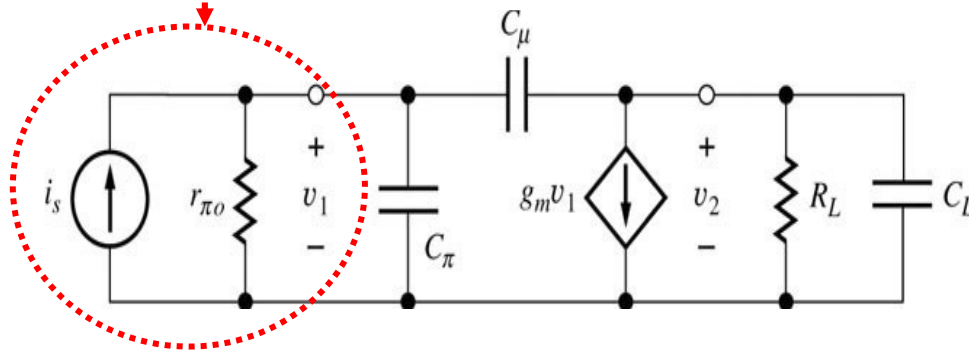


$$i_s = \frac{v_{th}}{R_{th} + r_x}$$

$$r_{\pi o} = r_{\pi} \parallel (R_{th} + r_x)$$



# Determine $A_{mid}$

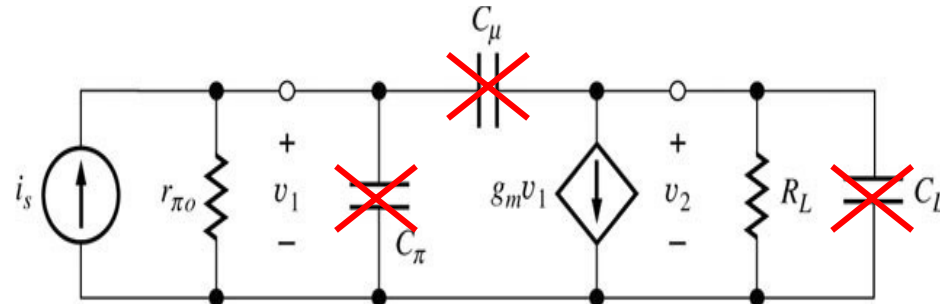

$$v_2 = -g_m (i_s r_{\pi 0}) R_L$$

$$i_s = \frac{v_{th}}{R_{th} + r_x} \quad r_{\pi 0} = r_{\pi} \parallel (R_{th} + r_x)$$


$$\frac{v_2}{v_{th}} = -g_m R_L \frac{r_{\pi 0}}{R_{th} + r_x} = -g_m R_L \frac{r_{\pi}}{R_{th} + r_x + r_{\pi}}$$

$$A_{mid} = -\frac{\beta_o R_L}{R_{th} + r_x + r_{\pi}} = -\frac{100(4120)}{882 + 250 + 1560} = -153$$


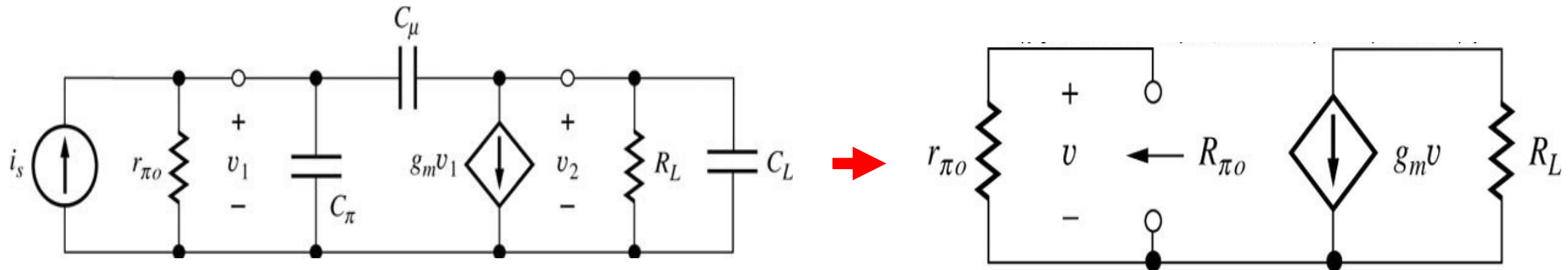
# OCTC: Time Constant Associated with $C_\pi$

To find the time constant associated with  $C_\pi$ :



( $C_\mu$  is open-circuited and set  $i_s = 0$ )

$$R_{\pi 0} = r_{\pi 0} = r_\pi \parallel (R_{th} + r_x) = 1.56 \text{ k}\Omega \parallel (882 \Omega + 250 \Omega) = 656 \Omega$$

$$C_\pi = 19.9 \text{ pF}$$


$$C_\pi R_{\pi 0} = 1.3 \times 10^{-8}$$





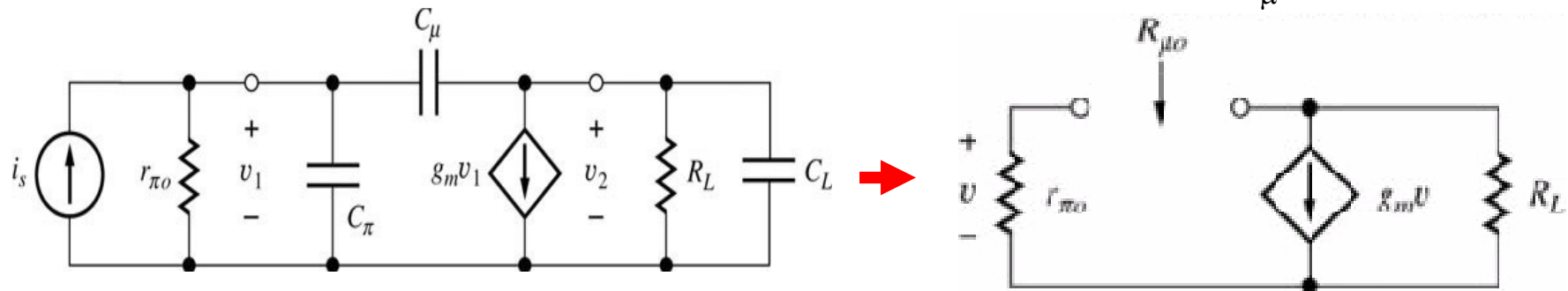
# OCTC: Time Constant Associated with $C_\mu$

To find the time constant associated with  $C_\mu$ :



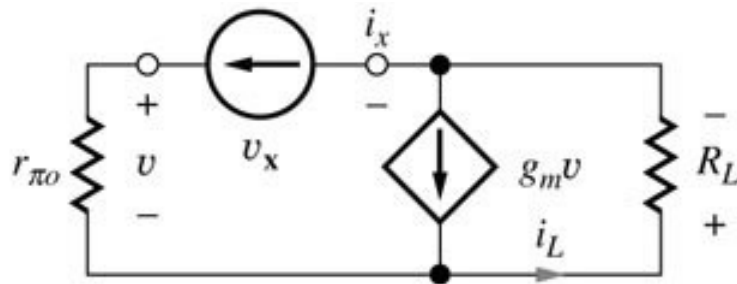( $C_\pi$  is open-circuited and set  $i_s = 0$ )



$$v_x = i_x r_{\pi 0} + i_L R_L = i_x r_{\pi 0} + (i_x + g_m v) R_L$$

$$R_{\mu 0} = \frac{v_x}{i_x} = r_{\pi 0} \left( 1 + g_m R_L + \frac{R_L}{r_{\pi 0}} \right) \quad \left| \quad v = i_x r_{\pi 0} \right.$$

$$\therefore R_{\mu 0} = 656 \Omega \left( 1 + 0.064(4120) + \frac{4120}{656} \right) = 178 k\Omega$$

$$C_\mu R_{\mu 0} = 89.0 \times 10^{-9}$$



# Upper Cutoff Frequency

Upper cutoff frequency:

$$\omega_H \cong \frac{1}{R_{\pi o} C_{\pi} + R_{\mu o} C_{\mu}} = \frac{1}{1.3 \times 10^{-8} + 89 \times 10^{-9}} = 9.8 \times 10^6 \text{ rad/s}$$

$$f_H = \frac{\omega_H}{2\pi} = 1.56 \text{ MHz}$$

