

*Week 7: Common-Collector Amplifier,
MOS Field Effect Transistor*





Topics to cover ...

- Common-Collector Amplifier
- MOS Field Effect Transistor
 - Physical Operation and I-V Characteristics of n-channel devices
 - Non-ideal effects
 - P-channel devices and other types
- Reading Assignment:
Chap 14.1 – 14.5 of Jaeger and Blalock , or
Chap 5.7 of Sedra & Smith
And
Chap 4.1 – 4.4 of Jaeger and Blalock or
Chap 5.1-5.2 of Sedra & Smith



Common-Collector Amplifier

 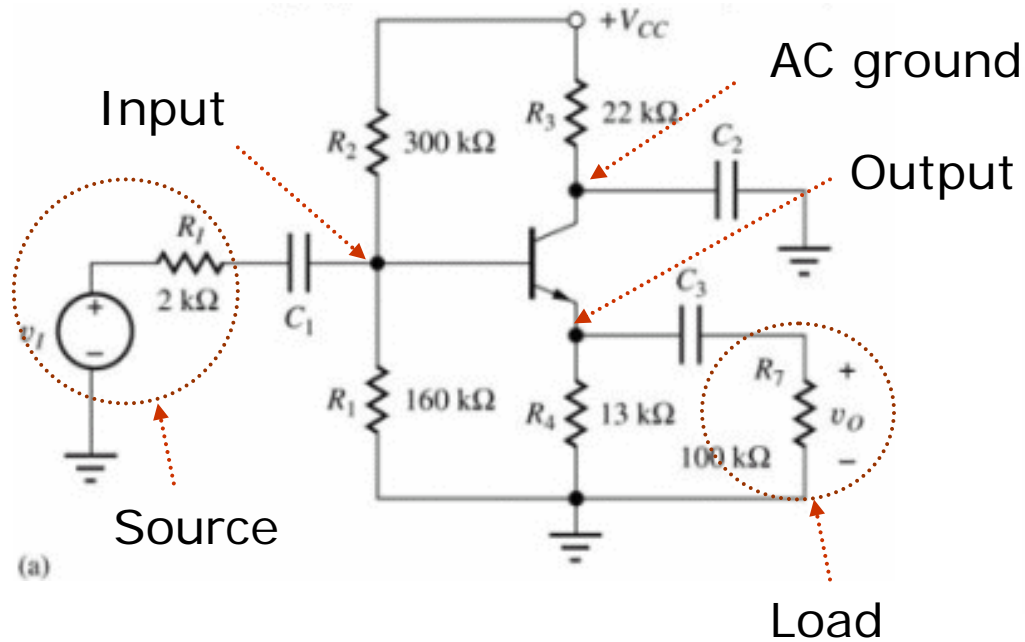

AC/Small signal equivalent



Also called “Emitter follower”

$$R_L = R_4 \parallel R_7$$

$$R_B = R_1 \parallel R_2$$



Terminal Voltage Gain

 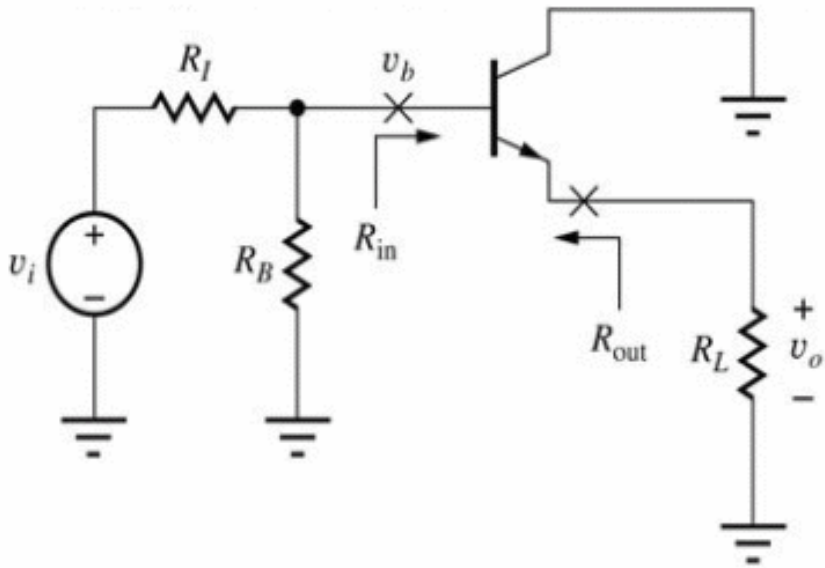

$$A_{vt}^{CC} = \frac{v_o}{v_b} = \frac{(\beta+1)R_L}{r_\pi + (\beta+1)R_L}$$

$$\therefore A_{vt}^{CC} \cong \frac{g_m R_L}{1 + g_m R_L} \quad \text{for } \beta \gg 1$$


In most C-C amplifiers, $g_m R_L \gg 1$

$$\therefore A_{vt}^{CC} \cong 1$$

Output voltage at emitter follows input voltage, hence the circuit is named ***Emitter Followers***.




 Input Resistance and Overall Voltage Gain



Input resistance looking into the base terminal is given by
 
$$R_{in}^{CC} = \frac{v_b}{i} = r_{\pi} + (\beta + 1)R_L$$



Overall voltage gain is


$$A_v^{CC} = \frac{v_o}{v_i} = \left(\frac{v_o}{v_b} \right) \left(\frac{v_b}{v_i} \right) = A_{vt} \left(\frac{v_b}{v_i} \right)$$

$$= A_{vt}^{CC} \left[\frac{R_B \parallel R_{in}^{CC}}{R_I + (R_B \parallel R_{in}^{CC})} \right]$$



Example 1

 - **Problem:** Find overall voltage gain.
- **Given data:** $\beta=100$, Q-point values: $I_C=245\mu\text{A}$, $V_{CE}=3.64\text{V}$, $g_m=9.8\text{m}\Omega^{-1}$, $r_\pi=10.2\text{k}\Omega$.
- **Assumptions:** Small-signal operating conditions.
- **Analysis:**



$$R_B = R_1 \parallel R_2 = 104\text{k}\Omega$$

$$R_L = R_4 \parallel R_7 = 11.5\text{k}\Omega$$

$$R_{in} = r_\pi + (\beta + 1)R_L = 10.2\text{k}\Omega + 101(10.2\text{k}\Omega) = 1.17\text{M}\Omega$$

$$A_{vt} = \frac{g_m R_L}{1 + g_m R_L} = 0.991$$

$$A_v = A_{vt} \left[\frac{R_B \parallel R_{in}^{CC}}{R_I + (R_B \parallel R_{in}^{CC})} \right] = 0.956$$



Input Signal Range

For small-signal operation, magnitude of $v_{be} < 5$ mV.


$$v_{be} = ir_{\pi} = \frac{v_b r_{\pi}}{r_{\pi} + (\beta + 1)R_L} = \frac{v_b}{1 + g_m R_L + \frac{R_L}{r_{\pi}}}$$

$$\left| v_b \right| \leq 0.005 \left(1 + g_m \left(R_L + \frac{R_L}{\beta} \right) \right)$$


$$\cong 0.005(1 + g_m R_L) V$$

If $g_m R_L \gg 1$, v_b can be increased beyond 5 mV limit.

 Emitter followers can be used with relatively large input signals!




Output Resistance

 

$$i_x = -i - \beta i = \frac{v_x}{R_{th} + r_\pi} - \beta \left(-\frac{v_x}{R_{th} + r_\pi} \right)$$
 
$$\therefore R_{out}^{CC} \cong \frac{R_{th} + r_\pi}{\beta + 1} = \frac{r_\pi}{\beta + 1} + \frac{R_{th}}{\beta + 1}$$



$$R_{out}^{CC} = \frac{\alpha}{g_m} + \frac{R_{th}}{\beta + 1} \cong \frac{1}{g_m} + \frac{R_{th}}{\beta + 1}$$

$$R_{out}^{CC} \cong \frac{1}{g_m} + \frac{R \text{ connected to base}}{\beta + 1}$$

$$R_{th} = R_I \parallel R_B$$


Small output resistance!




Example 2

 - **Problem:** Find output resistance.
- **Given data:** $\beta=100$, Q-point values: $I_C=245\mu\text{A}$, $V_{CE}=3.64\text{V}$, $g_m=9.8\text{mS}$, $r_\pi=10.2\text{k}\Omega$, $r_o=219\text{k}\Omega$.
- **Assumptions:** Small-signal operating conditions.
- **Analysis:**

$$R_{out}^{CC} = \frac{\alpha}{g_m} + \frac{R_{th}}{\beta+1} = \frac{0.990}{9.80\text{mS}} + \frac{1.96\text{k}\Omega}{101} = 120\Omega$$



Current Gain

 

- Terminal current gain $A_{it}^{CC} = \frac{i_l}{i} = \beta + 1$




Summary of Emitter Follower

- *Voltage gain*: Close to unity.
- *Input resistance*: Large
- *Output resistance*: Small
- *Input signal range*: relatively large
- *Terminal current gain*: Large ($\beta+1$)

- Excellent for use as a voltage buffer



Voltage Buffer

 


Without buffer:

$$v_o = \frac{R_L}{R_s + R_L} v_s \ll v_s \quad \text{if } R_L \ll R_s$$

With buffer:
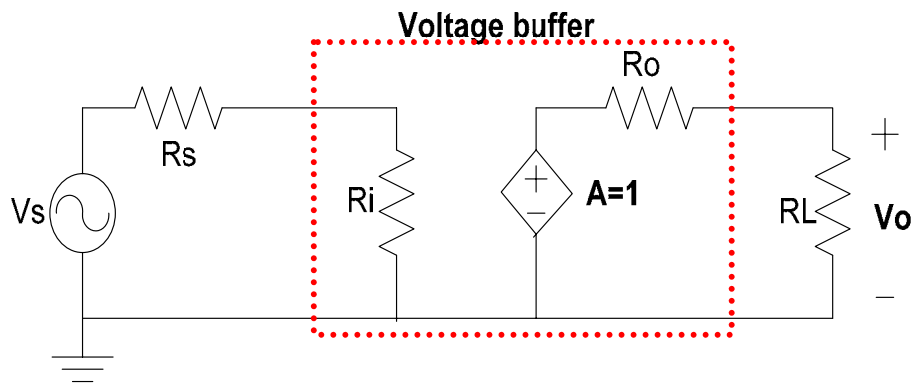
$$v_o = \left(\frac{R_i}{R_s + R_i} v_s \right) A \frac{R_L}{R_L + R_o}$$
$$\cong A v_s = v_s \quad \text{for } R_i \gg R_s \text{ and } R_o \ll R_L$$



Requirement of voltage buffer:

- High input resistance
- Low output resistance
- Unity voltage gain





Summary of Single Stage BJT Amplifiers

	C-E ($R_E=0$)	Emitter Degenerated C-E	C-C	C-B
Terminal Voltage Gain	Inverting & large	Inverting & moderate	1	Non-inverting & Large
Input Resistance	Moderate	Large	Large	Low
Output Resistance	Moderate	Large	Low	Large
Input Voltage Range	Small	Moderate	Large	Moderate
Terminal Current Gain	Inverting & Large	Inverting & Large	Non-inverting & Large	1



More Complicated Amplifier ...

 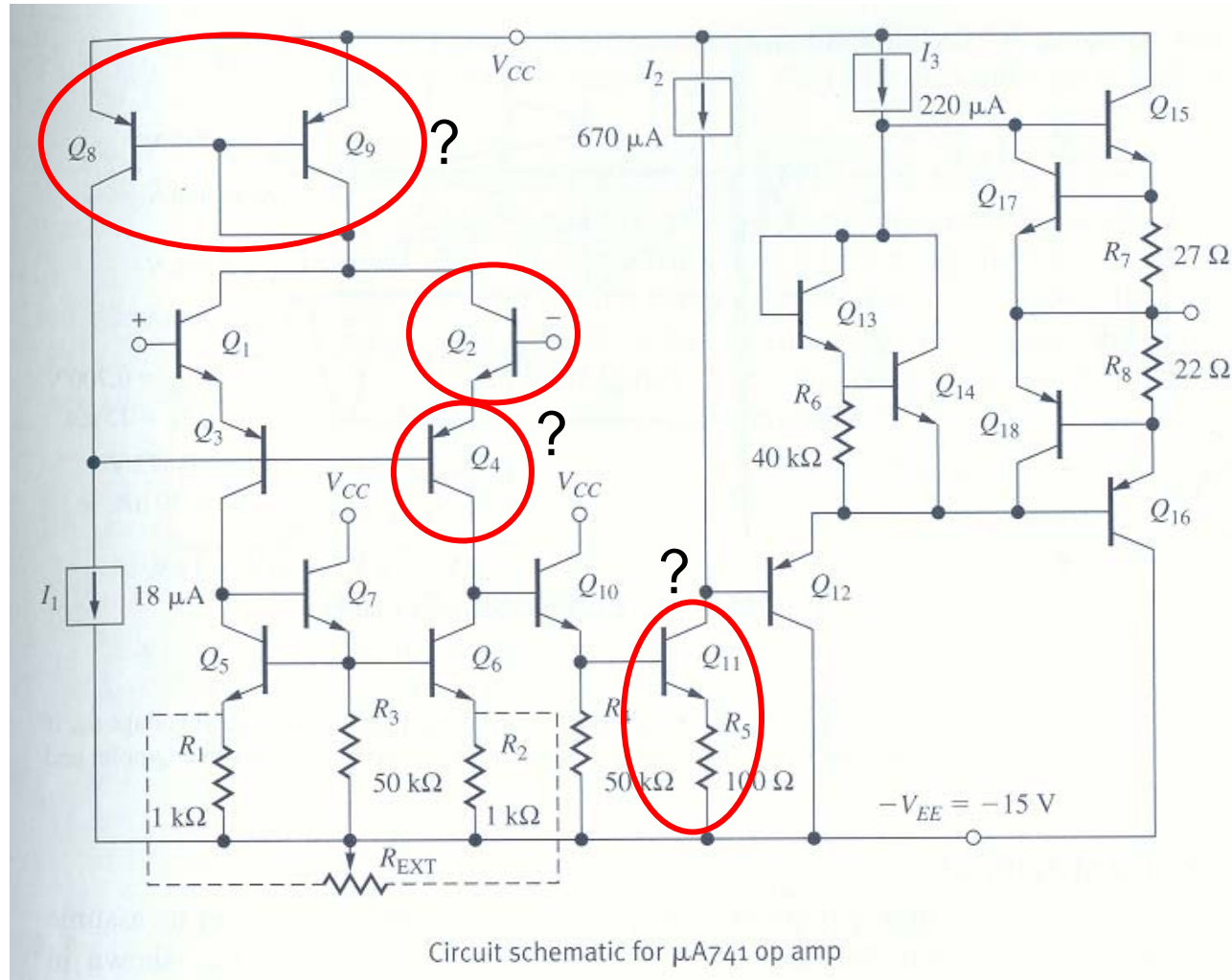

$\mu A741$ Die Photograph (Courtesy of Fairchild Semiconductor)

741 Op-amp - Built from single stage amplifiers



Topics to cover ...


- Common-Collector Amplifier
- MOS Field Effect Transistor
 - Physical Operation and I-V Characteristics of n-channel devices
 - Non-ideal effects
 - P-channel devices and other types



Introduction


- Metal-Oxide Semiconductor Field-Effect Transistor (MOSFET) is the primary component in high-density chips such as memories and microprocessors
- Compared with BJT, MOSFET has
 - Higher integration scale
 - Lower manufacturing cost
 - Simpler circuitry for digital logic and memory
 - Inferior analog circuit performance in general
- Recent trend: more and more analog circuits are implemented in MOS technology for
 - lower cost
 - integration with digital circuits in a same chip (mixed-signal IC)



 


Microphotograph of
a state-of-the-art CPU chip


Structure of MOSFET

 

(a)

 

(b)

 


(c) symbol

- Four terminals:
 - Gate, Source, Drain and body
- Two types
 - n-Channel (NMOS)
 - p-Channel (PMOS)
- The minimum value of L is referred as the **feature size** of the fabrication technology.
 - E.g., 45nm is used for Intel's Core 2 processors.




Low Gate Voltage

 

- Body is commonly tied to ground
- When the gate is at a low voltage ($V_{GS} \sim 0$):
 - P-type body is at low voltage
 - Source-body and drain-body diodes are OFF (reverse bias)
 - $i_G = 0$ (always), $i_{DS} = 0$
- Depletion region between n+ and p-type bulk
 - No current can flow, transistor is said in “**Cutoff**” mode




Increase Gate Voltage

 

- Vertical electric field established
- Under the gate-oxide:
 - Holes (positive charges) repelled
 - Depletion region under gate oxide formed



Further Increase Gate Voltage

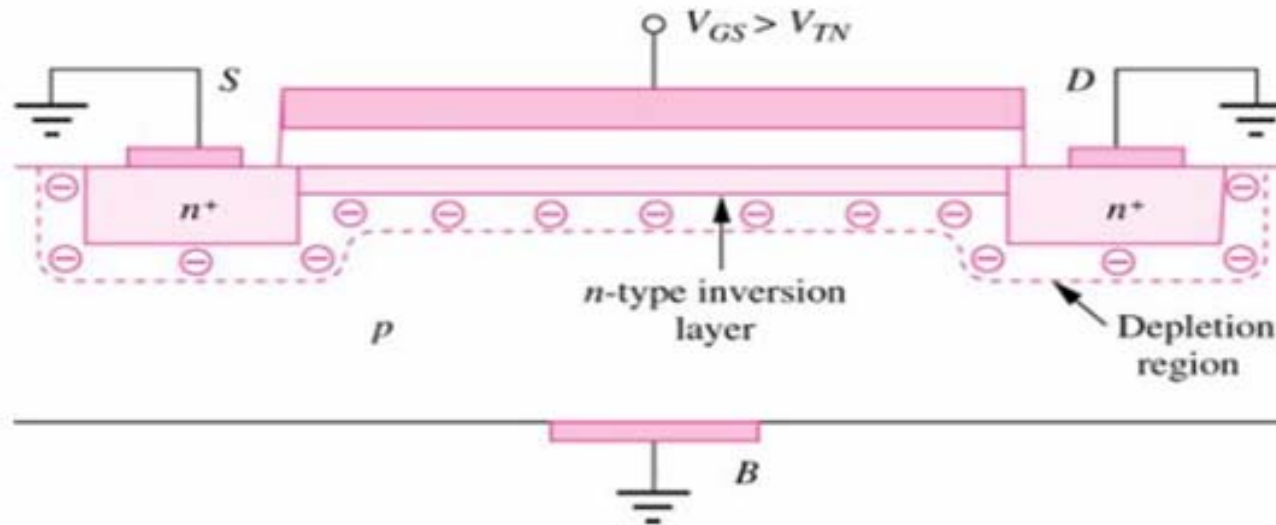


- Electrons (minorities in the p region) attracted by the electric field towards the gate, and stopped by the gate oxide
- A n-type inversion layer formed underneath the gate oxide when V_{GS} reaches a certain value, called **threshold voltage** (V_t , or V_{TN} for NMOS)
- The channel connects the S and D and now currents can flow between them





Linear (Triode) Mode of Operation

 - When $v_{GS} > V_t$ and a small v_{DS} is applied
 - Current flows from D to S (Electrons flow from S to D)
 - $i_{DS} \propto v_{DS}$
- Increasing v_{GS} above V_t increases the electron density in the channel, and in turn increases the conductivity between D & S
- Such devices are called enhancement-type MOSFET
- In this mode, transistor = a voltage controlled resistor



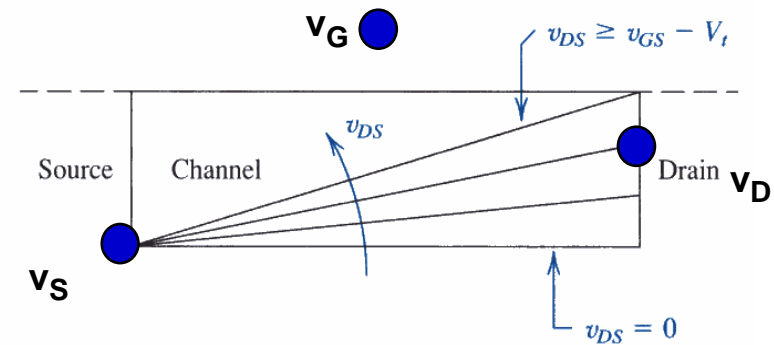
 
Increase Drain Voltage: Channel Pinch-Off



- Increase $v_{DS} \rightarrow$ Decrease $v_{GD} \rightarrow$ less electrons at the drain side of the channel
- When $v_{DS} \geq v_{GS} - V_t$
 $\rightarrow V_{GD} \leq V_t$
 \rightarrow no channel exists at the drain side. The channel “*pinches-off*”




Saturation Mode of Operation

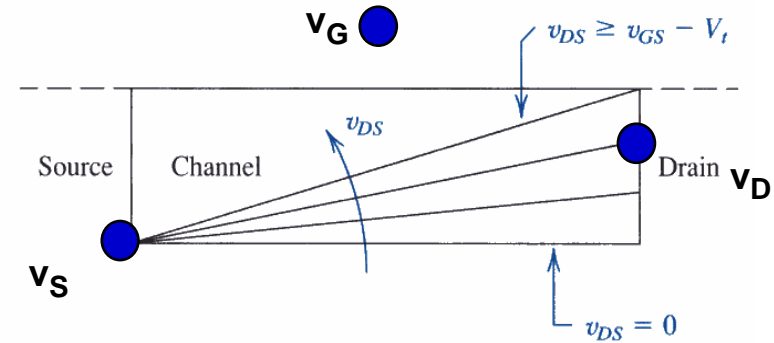 

- When channel pinches off, electrons still flows from S to D
 - Electrons are diffused from the channel to the depletion region near D, where they are drifted by the lateral E -field to the D
 - Similar to a reverse-biased B-C junction in a BJT
- Further increase of $v_{DS} \rightarrow$ no effect on the channel \rightarrow current is “saturated” and the transistor is in “**Saturation Mode**”
- In this mode, transistor = a voltage controlled current source



Qualitative I-V Characteristic

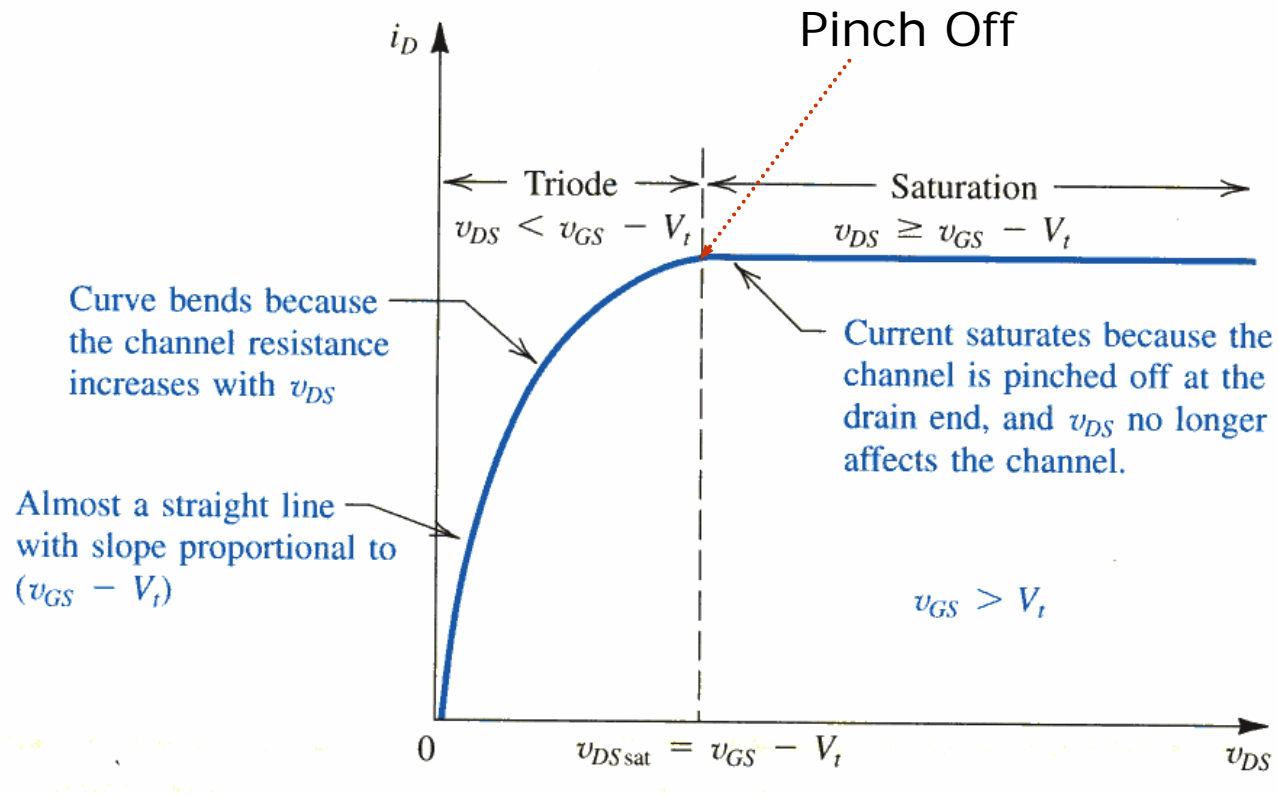

I-V Characteristics

- In the Linear region, drain current depends on
 - How much charge is in the channel
 - How fast the charge is moving

$$I \equiv \frac{dQ}{dt} = \frac{\text{amount of charge in the channel}}{\text{time it takes the carriers to get across the channel}}$$



Amount of Channel Charge



- MOS structure looks like a parallel plate capacitor
- V_{GC} is composed of two components
 - V_t to form the channel
 - $(V_{GC} - V_t)$ to accumulate negative charges in the channel

$$Q_{channel} = CV$$

$$C = \epsilon_{ox} \frac{WL}{t_{ox}} = C_{ox} WL \quad \text{where } C_{ox} = \epsilon_{ox} / t_{ox}$$

$$V = V_{GC} - V_t = \underbrace{(v_{GS} - v_{DS} / 2)}_{\text{Average gate-channel voltage}} - V_t$$

Average gate-channel voltage

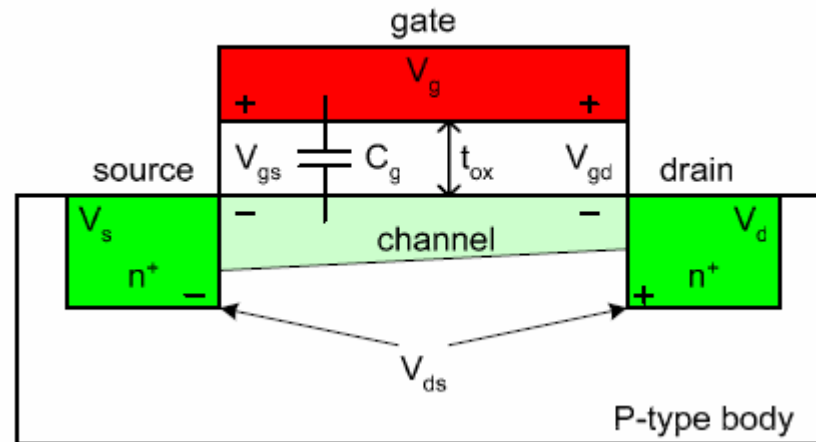 

Ref: G.-Y. Wei, notes ES154, Harvard University



Carrier Velocity

- Charge is carried by electrons.
- Carrier velocity v is proportional to the lateral E-field between source and drain

$$v = \mu_n E \quad \text{where } \mu_n \text{ is the mobility}$$

$$E = v_{DS} / L$$

- Time for carriers to cross the channel is

$$t = L / v = \frac{L}{\mu_n E} = \frac{L^2}{\mu_n v_{DS}}$$



I-V Behavior: Linear Mode

- Combine the channel charge and velocity to find the current flow
 - Current = amount of charge in the channel / time it takes the carriers to get across the channel

$$\begin{aligned}i_D &= \frac{Q_{channel}}{t} = C_{ox}WL(v_{GS} - V_t - v_{DS}/2) \frac{\mu_n v_{DS}}{L^2} \\ &= \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_t - v_{DS}/2) v_{DS} \\ &= K_n (v_{GS} - V_t - v_{DS}/2) v_{DS} \quad \text{where } K_n = \mu_n C_{ox} \frac{W}{L}\end{aligned}$$

$$i_D = (\mu_n C_{ox}) \frac{W}{L} \left[(v_{GS} - V_t) v_{DS} - \frac{1}{2} v_{DS}^2 \right]$$

- $(\mu_n C_{ox})$ is a constant determined by the processing technology, and is denoted by K'_n
- W/L is a main design parameter in integrated circuit design.



I-V Behavior: Saturation Mode

- If $v_{GD} \leq V_t$, channel pinches off near the drain
 - When $v_{DS} \geq V_{dsat} = v_{GS} - V_t$
- Now, drain voltage no longer increases with v_{DS}
- Putting $v_{DS} = v_{GS} - V_t$ to the equation:

$$i_D = (\mu_n C_{ox}) \frac{W}{L} \left[(v_{GS} - V_t) v_{DS} - \frac{1}{2} v_{DS}^2 \right]$$

→
$$i_D = \frac{1}{2} (\mu_n C_{ox}) \frac{W}{L} (v_{GS} - V_t)^2$$
 for $v_{GS} > V_t$ and $v_{DS} \geq v_{GS} - V_t$

- i_D independent of v_{DS} .



Summary of NMOS I-V Characteristics

Region	Cutoff	Triode	Saturation
Conditions	$v_{GS} < V_t$	$v_{GS} \geq V_t$	
		$v_{DS} < v_{GS} - V_t$	$v_{DS} \geq v_{GS} - V_t$
I-V relation	$i_D = 0$	$i_D = K'_n \frac{W}{L} \left[(v_{GS} - V_t)v_{DS} - \frac{1}{2}v_{DS}^2 \right]$	$i_D = \frac{1}{2} K'_n \frac{W}{L} (v_{GS} - V_t)^2$

➔ Cutoff region $v_{GS} < V_t$

➔ Triode region

$$v_{GS} \geq V_t \quad \text{and}$$

$$v_{DS} < v_{GS} - V_t$$


➔ Saturation region

$$v_{GS} \geq V_t \quad \text{and}$$


$$v_{DS} \geq v_{GS} - V_t$$

$$K'_n = \mu_n C_{ox}$$

Voltage ↑

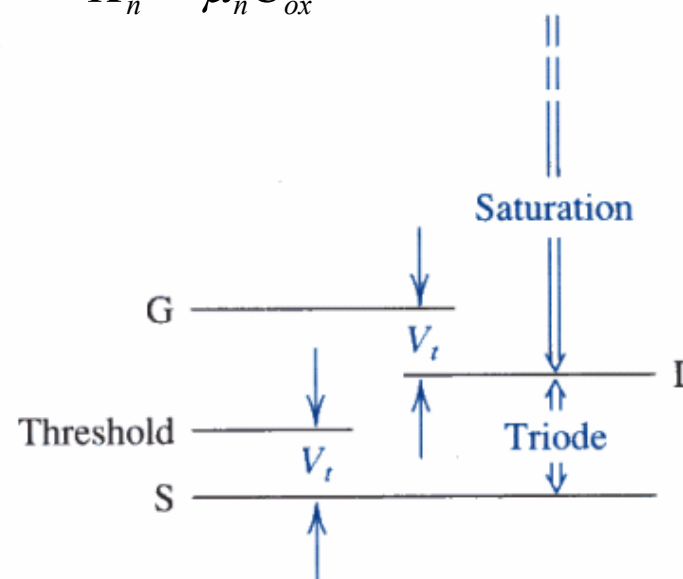

Ideal Square Law Model: I_D vs V_{GS}

 



In saturation mode:

$$i_D = \frac{1}{2} (\mu_n C_{ox}) \frac{W}{L} (v_{GS} - V_t)^2$$

- MOS vs. BJT
 - Current is quadratic with voltage in MOS vs.
 - exponential relationship in BJT
- Saturation mode of MOS corresponds to active mode of BJT



Ideal Square-Law Model: I_D vs V_{DS}

  

NMOS



Topics to cover ...

- Common-Collector Amplifier
- MOS Field Effect Transistor
 - Physical Operation and I-V Characteristics of n-channel devices
 - Non-ideal effects
 - P-channel devices and other types




Non-ideal Effects

- Channel length modulation
- Body effect
- Temperature influence
- Breakdown




Channel-Length Modulation

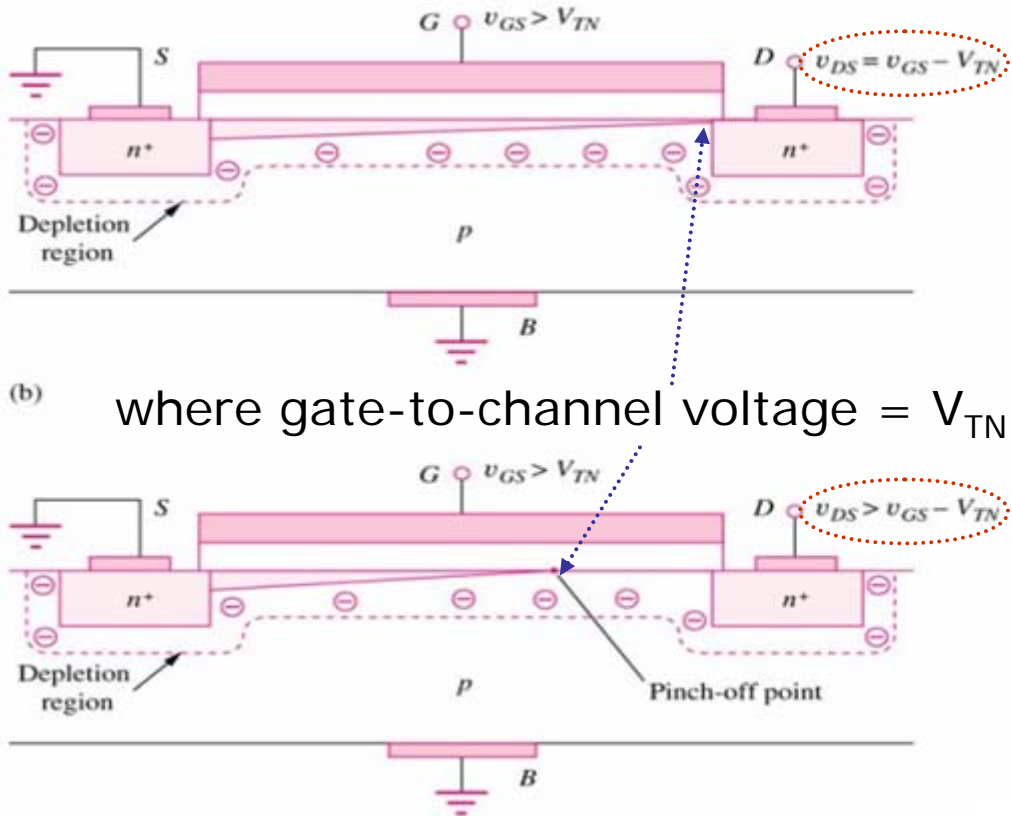


- At $v_{DS} = v_{GS} - V_{TN} = V_{DSsat}$
 - Channel pinch-off
- As v_{DS} increases beyond v_{DSsat} , the pinch off point moves away from D towards S
 - The effective channel length L is reduced by ΔL
 - I_D increases
 - An effect similar to Early effect in BJT
 
$$i_D = \frac{K'_n W}{2 L} (v_{GS} - V_{TN})^2$$



Channel-Length Modulation

 


- This effect is modeled by adding a term $(1+\lambda v_{DS})$ to the I-V equation:

$$i_D = \frac{K'_n W}{2 L} (v_{GS} - V_{TN})^2 (1 + \lambda v_{DS})$$

λ = channel length modulation parameter




Body Effect

 

- Channel-body can be regarded as a pn junction
- If channel-body junction is reverse-biased,
 - Depletion layer beneath the gate oxide becomes wider
 - Since the amount of negative charges in the (channel + depletion) layer = amount of positive charges in the gate (Constant for a fixed gate-source voltage)
 - Channel depth is reduced
 - This is equivalent to an increase in the threshold voltage



Body Effect

 

- Non-zero v_{SB} changes threshold voltage:

$$V_{TN} = V_{TO} + \gamma \left(\sqrt{v_{SB} + 2\phi_F} - \sqrt{2\phi_F} \right)$$

where

V_{TO} = zero substrate bias for V_{TN} (V)

γ = body-effect parameter (\sqrt{V})

$2\phi_F$ = surface potential parameter (V)

It follows that the body voltage controls i_D .

This phenomenon is known as the **body effect**.




Effects of Temperature

- V_t and mobility μ are sensitive to temperature:
 - V_t decreases by 2mV for every 1°C rise in temperature
 - mobility μ decreases with temperature
- Overall, increase in temperature results in lower drain currents




Avalanche Breakdown

 

- As V_D is increased, the drain-body junction becomes reversed biased
→ Breakdown occurs at voltages of 20 to 150V
→ Rapid increase in the drain current
- Normally, no permanent damage to the device




Punch-through Breakdown

 

- When V_D is increased to a point, \rightarrow the depletion region surrounding D extends to the S \rightarrow Punch-through breakdown (about 20 V)
- Occurs in devices with short channels
- Normally, no permanent damage to the device




Gate Oxide Breakdown

 

- When V_{GS} exceeds about 30 V (or lower in modern IC technology) → Gate oxide breaks down like in the case of a capacitor
- Results in permanent damage to the device



Input Protection

 

- Since the MOSFET has a very small input capacitance and a very high input resistance, a small amount of static charges accumulating on the gate can cause the gate voltage to exceed the breakdown level
 - e.g., Electrostatic Discharge (ESD) from human body
- Clamping diodes can be used in the I/O pins to protect the circuit from gate-oxide breakdown






Topics to cover ...

- Common-Collector Amplifier
- MOS Field Effect Transistor
 - Physical Operation and I-V Characteristics of n-channel devices
 - Non-ideal effects
 - P-channel devices and other types



P-channel MOSFET (PMOS)

   
- Similar to NMOS, but doping and voltages reversed
 - Body tied to highest voltage (V_{dd}) to prevent forward-biasing pn junctions
 - Source typically tied to V_{dd} too
 - Gate voltage high: transistor is OFF
 - Gate voltage low: transistor is ON when $V_{GS} < V_t$ (threshold voltage)
 - Inverted channel of positively charged holes
 - v_{GS} and v_{DS} are negative and V_t is also negative



Symbols



PMOS I-V Characteristics

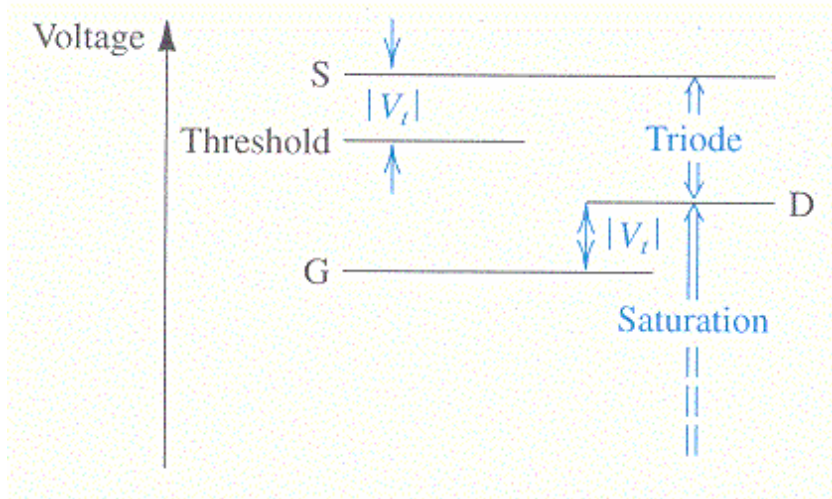

V_t , v_{GS} and v_{DS} are negative.

→ Cutoff region $|v_{GS}| < |V_t|$

→ Triode region

$$|v_{GS}| \geq |V_t| \quad \text{and}$$

$$|v_{DS}| < |v_{GS} - V_t|$$

→ Saturation region

$$|v_{GS}| \geq |V_t| \quad \text{and}$$

$$|v_{DS}| \geq |v_{GS} - V_t|$$


Cutoff	Triode/Linear	Saturation
$i_D = 0$	$i_D = K_p \left[(v_{GS} - V_t)v_{DS} - \frac{1}{2}v_{DS}^2 \right]$	$i_D = \frac{1}{2}K_p (v_{GS} - V_t)^2$

where $K_p = K_p' \frac{W}{L}$, $K_p' = \mu_p C_{ox}$

μ_p is 2 or 3-times lower than μ_n



Complementary MOS (CMOS) Technology

 




PMOS transistor is fabricated in the **n well**

Complementary MOS or CMOS integrated-circuit technologies provide both NMOS and PMOS on a same IC




Depletion-mode MOSFET

   
- A depletion-type MOSFET has a built-in channel by fabrication
 - It is ON when no gate-source voltage is applied
 - Must apply a negative v_{GS} to turn off device
- V_t is negative for NMOS




MOSFET Circuit Symbols

 


(a) NMOS enhancement-mode device

 


(b) PMOS enhancement-mode device

 


(c) NMOS depletion-mode device

 


(d) PMOS depletion-mode device

 


(e) Three-terminal NMOS transistors

 


(f) Three-terminal PMOS transistors

 

 
(g) Shorthand notation—NMOS enhancement-mode device



 (h) Shorthand notation—NMOS depletion-mode device



 (i) Shorthand notation—PMOS enhancement-mode device



(j) Shorthand notation—PMOS depletion-mode device

- (g) and (i) are the most commonly used symbols in VLSI logic design.
- MOS devices are symmetric.
- In NMOS, n^+ region at higher voltage is the drain.
- In PMOS p^+ region at lower voltage is the drain

