

Chapter 7

Series-Parallel Circuits

The Series-Parallel Network

- Branch
 - Part of a circuit that can be simplified into two terminals
- Components between these two terminals
 - Resistors, voltage sources, or other elements

The Series-Parallel Network

- Complex circuits
 - May be separated both series and/or parallel elements
- Other circuits
 - Combinations which are neither series nor parallel


3

The Series-Parallel Network

- To analyze a circuit
 - Identify elements in series and elements in parallel
- In this circuit
 - R_2 , R_3 , and R_4 are in parallel
- This parallel combination
 - Series with R_1 and R_5

4


The Series-Parallel Network

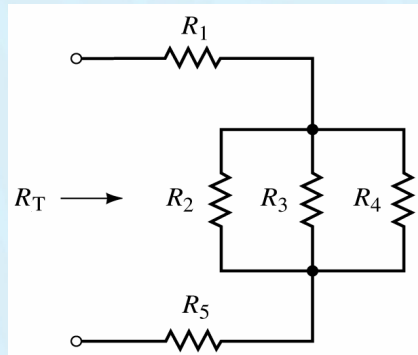

5

The Series-Parallel Network

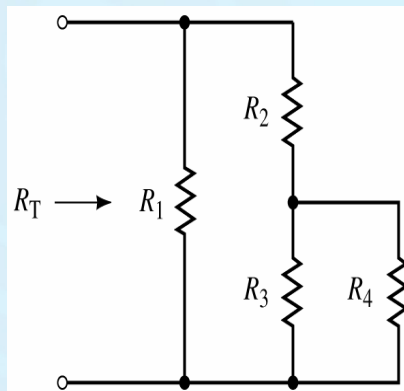- In this circuit
 - R_3 and R_4 are in parallel
 - Combination is in series with R_2
- Entire combination is in parallel with R_1



6

Analysis of Series-Parallel Circuits

- Rules for analyzing series and parallel circuits still apply
- Same current occurs through all series elements

7

Analysis of Series-Parallel Circuits

- Same voltage occurs across all parallel elements
- KVL and KCL apply for all circuits
 - Whether they are series, parallel, or series-parallel

8

Analysis of Series-Parallel Circuits

- Redraw complicated circuits showing the source at the left-hand side
- Label all nodes

9

Analysis of Series-Parallel Circuits

- Develop a strategy
 - Best to begin analysis with components most distant from the source
- Simplify recognizable combinations of components

10

Analysis of Series-Parallel Circuits

- Determine equivalent resistance R_T
- Solve for the total current
- Label polarities of voltage drops on all components

11

Analysis of Series-Parallel Circuits

- Calculate how currents and voltages split between elements in a circuit
- Verify your answer by taking a different approach (when feasible)


12

Analysis of Series-Parallel Circuits

- Combining R_2 and R_3 in parallel
 - Circuit reduces to a series circuit
 - Use Voltage Divider Rule to determine V_{ab} and V_{bc} .
 - Note that $V_{bc} = V_2$ is the voltage across R_2 and R_3
 - Calculate all currents from Ohm's Law.

13


Analysis of Series-Parallel Circuits

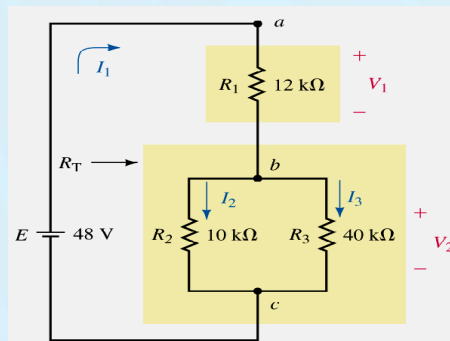

14

Analysis of Series-Parallel Circuits

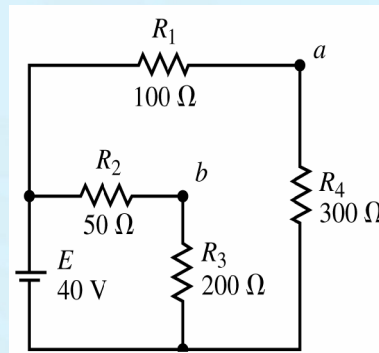- To find voltage V_{ab}
 - Redraw circuit in simple form
- Original circuit
 - Two parallel branches




15

Analysis of Series-Parallel Circuits

- V_{ab}
 - Determined by combination of voltages across R_1 and R_2 , or R_3 and R_4
- Use Voltage Divider Rule to find two voltages
- Use KVL to find V_{ab}

16

Analysis of Series-Parallel Circuits

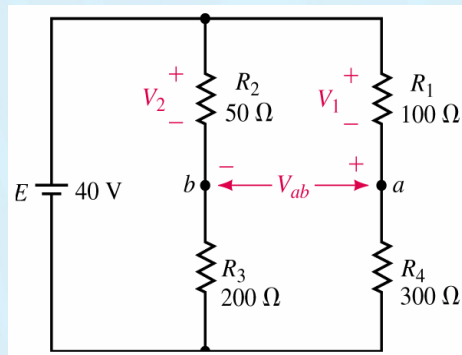


17

Analysis of Series-Parallel Circuits

- To find currents in the circuit
 - First redraw the circuit
 - Move source branch all the way to left
- Reduce circuit to a series circuit

18

Analysis of Series-Parallel Circuits

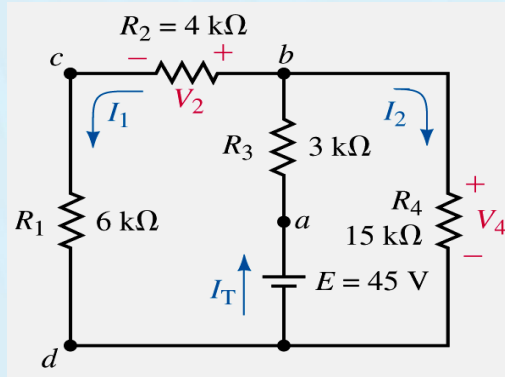


19

Analysis of Series-Parallel Circuits

- Voltages
 - Use Ohm's Law or Voltage Divider Rule
- Currents
 - Use Ohm's Law or Current Divider Rule

20


Analysis of Series-Parallel Circuits

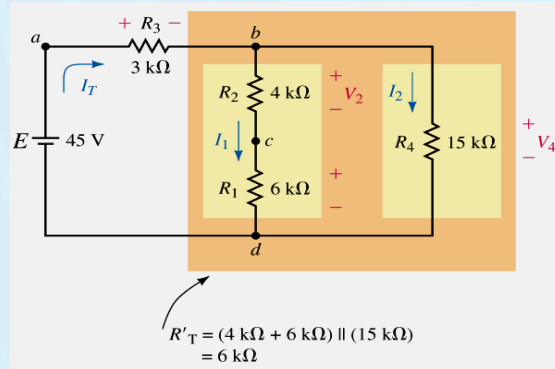

21

Bridge Circuit

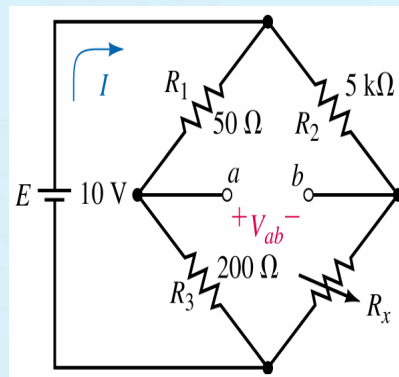
- Circuit has $R_x = 15 \text{ k}\Omega$
- Determine V_{ab}
- Redraw circuit as shown on slide



22

Bridge Circuit

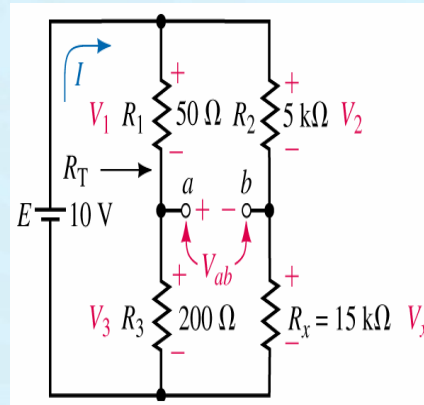
- Voltage Divider Rule
 - Determine V_a and V_b .
- Ground reference point
 - Take at bottom of circuit
- $V_{ab} = 0.5 \text{ V}$



23

Bridge Circuit

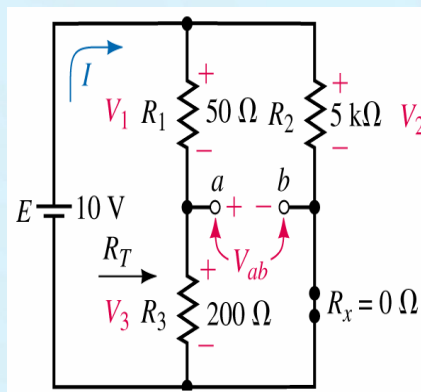
- R_x is a short circuit (0Ω)
- Voltage Divider Rule
 - Determine V_{R_1}
- $V_{R_2} = 10 \text{ V}$
- $V_{ab} = 8 \text{ V}$



24

Bridge Circuit

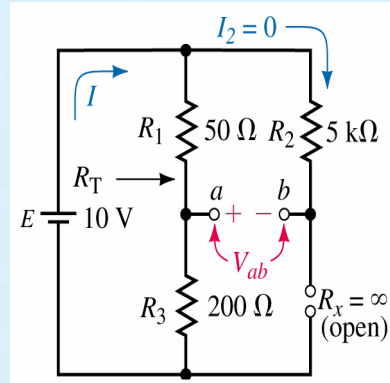- R_x is open
- Find V_{R_1}
- We know $V_{R_2} = 0\text{ V}$
 - No current through it
- $V_{ab} = -2\text{ V}$




25

Transistor Circuit

- Transistor
 - Device that amplifies a signal
- Operating point of a transistor circuit
 - Determined by a dc voltage source
- We will determine some dc voltages and currents

26


Transistor Circuit

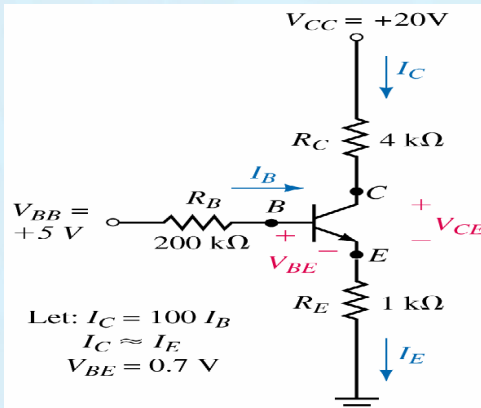

27

Transistor Circuit

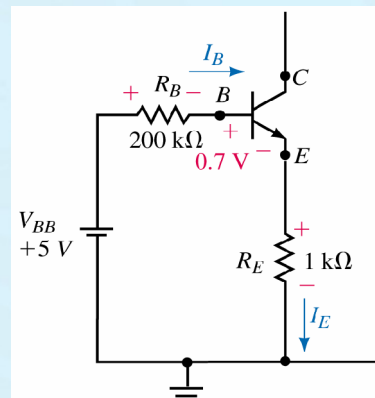- Apply KVL:
 $V_{BB} = R_B I_B + V_{BE} + R_E I_E$
- Using $I_E = 100 I_B$, we find $I_B = 14.3 \mu\text{A}$.
- Other voltages and currents can be determined




28

Potentiometers

- Example of variable resistor used as potentiometer
 - Volume control on a receiver
- Moveable terminal is at uppermost position
 - $V_{bc} = 60 \text{ V}$
- At the lowermost position
 - $V_{bc} = 0 \text{ V}$

29


Potentiometers

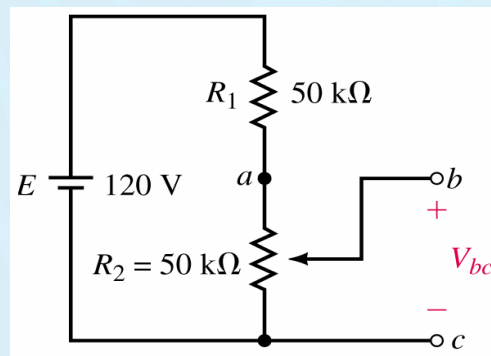

30

Potentiometers

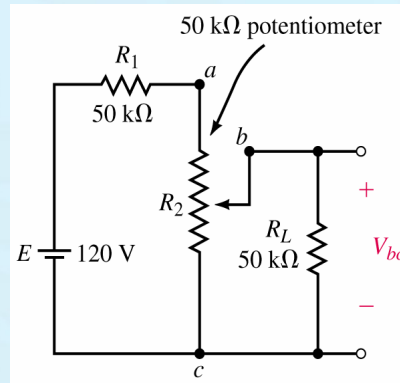- V_{bc} changes
 - If load is added to circuit
 - At upper position
 - $V_{bc} = 40\text{ V}$
 - At the lower position
 - $V_{bc} = 0\text{ V}$



31

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.