

Chapter 16

R,L, and C Elements and the Impedance Concept

Introduction

- To analyze ac circuits in the time domain is not very practical
- It is more practical to:
 - Express voltages and currents as phasors
 - Circuit elements as impedances
 - Represent them using complex numbers

Introduction

- AC circuits
 - Handled much like dc circuits using the same relationships and laws

3

Complex Number Review

- A complex number has the form:
 - $a + jb$, where $j = \sqrt{-1}$ (mathematics uses i to represent imaginary numbers)
 - a is the real part
 - jb is the imaginary part
 - Called rectangular form

4

Complex Number Review

- Complex number
 - May be represented graphically with a being the horizontal component
 - b being the vertical component in the complex plane

5

Conversion between Rectangular and Polar Forms

- If $\mathbf{C} = a + jb$ in rectangular form, then $\mathbf{C} = C \angle \theta$, where

$$a = C \cos \theta$$

$$b = C \sin \theta$$

$$C = \sqrt{a^2 + b^2}$$

$$\theta = \tan^{-1} \frac{b}{a}$$

6

Complex Number Review

- $j^0 = 1$
- $j^1 = j$
- $j^2 = -1$
- $j^3 = -j$
- $j^4 = 1$ (Pattern repeats for higher powers of j)
- $1/j = -j$

7

Complex Number Review

- To add complex numbers
 - Add real parts and imaginary parts separately
- Subtraction is done similarly

8

Review of Complex Numbers

- To multiply or divide complex numbers
 - Best to convert to polar form first
- $(A\angle\theta)\cdot(B\angle\phi) = (AB)\angle(\theta + \phi)$
- $(A\angle\theta)/(B\angle\phi) = (A/B)\angle(\theta - \phi)$
- $(1/C\angle\theta) = (1/C)\angle-\theta$

9

Review of Complex Numbers

- Complex conjugate of $a + jb$ is $a - jb$
- If $C = a + jb$
 - Complex conjugate is usually represented as C^*

10

Voltages and Currents as Complex Numbers

- AC voltages and currents can be represented as phasors
- Phasors have magnitude and angle
 - Viewed as complex numbers

11

Voltages and Currents as Complex Numbers

- A voltage given as $100 \sin (314t + 30^\circ)$
 - Written as $100 \angle 30^\circ$
- RMS value is used in phasor form so that power calculations are correct
- Above voltage would be written as $70.7 \angle 30^\circ$

12

Voltages and Currents as Complex Numbers

- We can represent a source by its phasor equivalent from the start
- Phasor representation contains information we need except for angular velocity

13

Voltages and Currents as Complex Numbers

- By doing this, we have transformed from the time domain to the phasor domain
- KVL and KCL
 - Apply in both time domain and phasor domain

14

Summing AC Voltages and Currents

- To add or subtract waveforms in time domain is very tedious
- Convert to phasors and add as complex numbers
- Once waveforms are added
 - Corresponding time equation of resultant waveform can be determined

15

Important Notes

- Until now, we have used peak values when writing voltages and current in phasor form
- It is more common to write them as RMS values

16

Important Notes

- To add or subtract sinusoidal voltages or currents
 - Convert to phasor form, add or subtract, then convert back to sinusoidal form
- Quantities expressed as phasors
 - Are in phasor domain or frequency domain

17

$R, L,$ and C Circuits with Sinusoidal Excitation

- $R, L,$ and C circuit elements
 - Have different electrical properties
 - Differences result in different voltage-current relationships
- When a circuit is connected to a sinusoidal source
 - All currents and voltages will be sinusoidal

18

$R, L,$ and C Circuits with Sinusoidal Excitation

- These sine waves will have the same frequency as the source
 - Only difference is their magnitudes and angles

19

Resistance and Sinusoidal AC

- In a purely resistive circuit
 - Ohm's Law applies
 - Current is proportional to the voltage

20

Resistance and Sinusoidal AC

- Current variations follow voltage variations
 - Each reaching their peak values at the same time
- Voltage and current of a resistor are in phase

21

Inductive Circuit

- Voltage of an inductor
 - Proportional to rate of change of current
- Voltage is greatest when the rate of change (or the slope) of the current is greatest
 - Voltage and current are not in phase

22

Inductive Circuit

- Voltage leads the current by 90° across an inductor

23

Inductive Reactance

- X_L , represents the opposition that inductance presents to current in an ac circuit
- X_L is frequency-dependent
- $X_L = V/I$ and has units of ohms

$$X_L = \omega L = 2\pi fL$$

24

Capacitive Circuits

- Current is proportional to rate of change of voltage
- Current is greatest when rate of change of voltage is greatest
 - So voltage and current are out of phase

25

Capacitive Circuits

- For a capacitor
 - Current leads the voltage by 90°

26

Capacitive Reactance

- X_C , represents opposition that capacitance presents to current in an ac circuit
- X_C is frequency-dependent
 - As frequency increases, X_C decreases

27

Capacitive Reactance

- $X_C = V/I$ and has units of ohms

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

28

Impedance

- The opposition that a circuit element presents to current is impedance, Z
 - $Z = V/I$, is in units of ohms
 - Z in phasor form is $Z \angle \theta$
 - θ is the phase difference between voltage and current

29

Resistance

- For a resistor, the voltage and current are in phase
- If the voltage has a phase angle, the current has the same angle
- The impedance of a resistor is equal to $R \angle 0^\circ$

30

Inductance

- For an inductor
 - Voltage leads current by 90°
- If voltage has an angle of 0°
 - Current has an angle of -90°
- The impedance of an inductor
 - $X_L \angle 90^\circ$

31

Capacitance

- For a capacitor
 - Current leads the voltage by 90°
- If the voltage has an angle of 0°
 - Current has an angle of 90°
- Impedance of a capacitor
 - $X_C \angle -90^\circ$

32

Capacitance

- Mnemonic for remembering phase
 - Remember ELI the ICE man
- Inductive circuit (L)
 - Voltage (E) leads current (I)
- A capacitive circuit (C)
 - Current (I) leads voltage (E)

33

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.