

Chapter 18

AC Series-Parallel Circuits

AC Circuits

- Rules and laws developed for dc circuits apply equally well for ac circuits
- Analysis of ac circuits requires vector algebra and use of complex numbers
- Voltages and currents in phasor form
 - Expressed as RMS (or effective) values

Ohm's Law

- Voltage and current of a resistor will be in phase
- Impedance of a resistor is: $\mathbf{Z}_R = R\angle 0^\circ$

$$I = \frac{V\angle\theta}{R\angle 0^\circ} = I\angle\theta$$

3

Ohm's Law

- Voltage across an inductor leads the current by 90° (ELI the ICE man)

$$\mathbf{Z}_L = X_L\angle 90^\circ$$

$$I = \frac{V\angle\theta}{X_L\angle 90^\circ}$$

$$I = I\angle(\theta - 90^\circ)$$

4

Ohm's Law

- Current through a capacitor leads the voltage by 90° (ELI the ICE man)

$$Z_C = X_C \angle -90^\circ$$

$$I = \frac{V \angle \theta}{X_C \angle -90^\circ}$$

$$I = I \angle (\theta + 90^\circ)$$

5

AC Series Circuits

- Current everywhere in a series circuit is the same
- Impedance used to collectively determine how resistance, capacitance, and inductance impede current in a circuit

6

AC Series Circuits

- Total impedance in a circuit is found by adding all individual impedances vectorially

7

AC Series Circuits

- Impedance vectors will appear in either the first or the fourth quadrants because the resistance vector is always positive
- When impedance vector appears in first quadrant, the circuit is inductive

8

AC Series Circuits

- If impedance vector appears in fourth quadrant
 - Circuit is capacitive

9

Voltage Divider Rule

- Voltage divider rule works the same as with dc circuits
- From Ohm's law:

$$I_x = I_T$$
$$\frac{V_x}{Z_x} = \frac{V_T}{Z_T}$$
$$V_x = \frac{Z_x}{Z_T} V_T$$

10

Kirchhoff's Voltage Law

- KVL is same as in dc circuits
- Phasor sum of voltage drops and rises around a closed loop is equal to zero

11

Kirchhoff's Voltage Law

- Voltages
 - May be added in phasor form or in rectangular form
- If using rectangular form
 - Add real parts together
 - Then add imaginary parts together

12

AC Parallel Circuits

- Conductance, G
 - Reciprocal of the resistance
- Susceptance, B
 - Reciprocal of the reactance

13

AC Parallel Circuits

- Admittance, Y
 - Reciprocal of the impedance
- Units for all of these are siemens (S)

14

AC Parallel Circuits

- Impedances in parallel add together like resistors in parallel
- These impedances must be added vectorially

15

AC Parallel Circuits

- Whenever a capacitor and an inductor having equal reactances are placed in parallel
 - Equivalent circuit of the two components is an open circuit

16

Kirchhoff's Current Law

- KCL is same as in dc circuits
- Summation of current phasors entering and leaving a node
 - Equal to zero

17

Kirchhoff's Current Law

- Currents must be added vectorially
- Currents entering are positive
- Currents leaving are negative

18

Current Divider Rule

- In a parallel circuit
 - Voltages across all branches are equal

$$\begin{aligned}V_x &= V_T \\I_x Z_x &= I_T Z_T \\I_x &= \frac{Z_T}{Z_x} I_T\end{aligned}$$

19

Series-Parallel Circuits

- Label all impedances with magnitude and the associated angle
- Analysis is simplified by starting with easily recognized combinations

20

Series-Parallel Circuits

- Redraw circuit if necessary for further simplification
- Fundamental rules and laws of circuit analysis must apply in all cases

21

Frequency Effects of *RC* Circuits

- Impedance of a capacitor decreases as the frequency increases
- For dc ($f = 0$ Hz)
 - Impedance of the capacitor is infinite

22

Frequency Effects of RC Circuits

- For a series RC circuit
 - Total impedance approaches R as the frequency increases
- For a parallel RC circuit
 - As frequency increases, impedance goes from R to a smaller value

23

Frequency Effects of RL Circuits

- Impedance of an inductor increases as frequency increases
- At dc ($f = 0$ Hz)
 - Inductor looks like a short
 - At high frequencies, it looks like an open

24

Frequency Effects of RL Circuits

- In a series RL circuit
 - Impedance increases from R to a larger value
- In a parallel RL circuit
 - Impedance increases from a small value to R

25

Corner Frequency

- Corner frequency is a break point on the frequency response graph
- For a capacitive circuit
 - $\omega_C = 1/RC = 1/\tau$
- For an inductive circuit
 - $\omega_C = R/L = 1/\tau$

26

RLC Circuits

- In a circuit with R , L , and C components combined in series-parallel combinations
 - Impedance may rise or fall across a range of frequencies
- In a series branch
 - Impedance of inductor may equal the capacitor

27

RLC Circuits

- Impedances would cancel
 - Leaving impedance of resistor as the only impedance
- Condition is referred to as resonance

28

Applications

- AC circuits may be simplified as a series circuit having resistance and a reactance
- AC circuit
 - May be represented as an equivalent parallel circuit with a single resistor and a single reactance

29

Applications

- Any equivalent circuit will be valid only at the given frequency of operation

30

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.