

## Chapter 22

### Filters and the Bode Plot

## Gain

- Power gain is ratio of output power to input power

$$A_P = \frac{P_{\text{out}}}{P_{\text{in}}}$$

## Gain

- Voltage gain is ratio of output voltage to input voltage

$$A_v = \frac{V_{out}}{V_{in}}$$

3

## Gain

- Any circuit in which the output signal power is greater than the input signal
  - Power is referred to as an amplifier
- Any circuit in which the output signal power is less than the input signal power
  - Called an attenuator

4

## Gain

- Gains are very large or very small
  - Inconvenient to express gain as a simple ratio

5

## The Decibel

- Bel is a logarithmic unit that represents a tenfold increase or decrease in power

$$A_{P(\text{bels})} = \log_{10} \frac{P_{\text{out}}}{P_{\text{in}}}$$

6

## The Decibel

- Because the bel is such a large unit, the decibel (dB) is often used

$$A_{P(\text{dB})} = 10 \log_{10} \frac{P_{\text{out}}}{P_{\text{in}}}$$

7

## The Decibel

- To express voltage gain in decibels:

$$A_{P(\text{dB})} = 10 \log_{10} \frac{P_{\text{out}}}{P_{\text{in}}}$$

$$A_{P(\text{dB})} = 10 \log_{10} \frac{V_{\text{out}}^2 / R}{V_{\text{in}}^2 / R}$$

$$A_{P(\text{dB})} = 10 \log_{10} \left( \frac{V_{\text{out}}}{V_{\text{in}}} \right)^2$$

$$A_{P(\text{dB})} = 20 \log_{10} \frac{V_{\text{out}}}{V_{\text{in}}} = A_{v(\text{dB})}$$

8

## Multistage Systems

- To find total gain of a system having more than one stage, each with a gain of  $A_n$ 
  - Multiply gains together
  - $A_T = A_1 A_2 A_3 \cdots$

9

## Multistage Systems

- If gains are expressed in decibels (which are logarithmic)
  - Gains will add instead of multiplying
  - $A_{T(\text{dB})} = A_{1(\text{dB})} + A_{2(\text{dB})} + A_{3(\text{dB})} \cdots$

10

## Voltage Transfer Functions

- Ratio of output voltage phasor to input voltage phasor for any frequency
- Amplitude of transfer function is voltage gain

11

## Voltage Transfer Functions

- Phase angle  $\theta$ 
  - Represents phase shift between input and output voltage phasors
- If the circuit contains capacitors or inductors
  - Transfer function will be frequency dependent

12

## Transfer Functions

- To examine the operation of a circuit over a wide range of frequencies
  - Draw a frequency response curve
- Any circuit which is said to pass a particular range of frequencies
  - Called a filter circuit

13

## Transfer Functions

- By passing a range of frequencies
  - Filter output response is high enough at these frequencies to be usable
- Common types of filters
  - Low-pass, high-pass, band-pass, and band-reject filters

14

## Low-Pass Filter

- Has a greater gain at low frequencies
  - At higher frequencies the gain decreases
- Cutoff frequency
  - Occurs when gain drops to  $\frac{1}{2}$  power point
  - This is 0.707 of the maximum voltage gain
- At cutoff
  - Voltage gain is  $-3\text{dB}$ ; phase angle is  $-45^\circ$

15

## Bode Plots

- A Bode plot is a straight-line approximation to the frequency response of a particular filter
- Abscissa will be the frequency in Hz on a logarithmic scale (base 10)

16



## Bode Plots

- Ordinate will be gain in dB on a linear scale
- Asymptotes
  - Actual response will approach the straight lines of the Bode approximation

17

## Bode Plots

- A decade represents a tenfold increase or decrease in frequency
- An octave represents a two-fold increase or decrease in frequency

18

## Bode Plots

- Slopes are expressed in either dB/decade or dB/octave
- A simple  $RC$  or  $RL$  circuit will have a slope of 20 dB/decade or 6 dB/octave

19

## Writing Voltage Transfer Functions

- A properly written transfer function allows us to easily sketch the frequency response of a circuit
- First, determine voltage gain when  $\omega = 0$  and  $\omega \rightarrow \infty$  (approaches infinity)

20

## Writing Voltage Transfer Functions

- Use voltage divider rule to write the general expression for transfer function in terms of the frequency

21

## Writing Voltage Transfer Functions

- Simplify results into a form containing only terms of  $j\omega\tau$  or  $(1 + j\omega\tau)$
- Determine break frequencies at  $\omega = 1/\tau$

22

## Writing Voltage Transfer Functions

- Sketch straight-line approximation by separately considering the effects of each term of transfer function
- Sketch actual response freehand from the approximation

23

## The *RC* Low-Pass Filter

- A series *RC* circuit with output taken across capacitor is a low-pass filter
- At low frequencies
  - Reactance is high
  - Output voltage is essentially equal to input

24

## The $RC$ Low-Pass Filter

- At high frequencies
  - Output voltage approaches zero

25

## The $RC$ Low-Pass Filter

- By applying voltage divider rule
  - Determine transfer function

$$V_{\text{out}} = \frac{X_C}{R + X_C} V_{\text{in}}$$

$$TF = \frac{1}{1 + j\omega RC}$$

26

## The *RC* Low-Pass Filter

- The cutoff frequency is

$$\omega_C = \frac{1}{RC}$$

27

## The *RL* Low-Pass Filter

- Low-pass filter may be made up of a resistor and an inductor
  - Output taken across the resistor
- Transfer function is

$$TF = \frac{R}{R + X_L} = \frac{R}{R + j\omega L}$$

28

## The $RL$ Low-Pass Filter

- Cutoff frequency is

$$\omega_c = \frac{R}{L}$$

29

## The $RC$ High-Pass Filter

- Simple  $RC$  circuit with output taken across resistor is a high-pass filter
- Transfer function is given by

$$TF = \frac{R}{R + Z_c} = \frac{j\omega RC}{1 + j\omega RC}$$

30

## The *RC* High-Pass Filter

- Phase shift is  $\theta = 90^\circ - \tan^{-1}(\omega/\omega_c)$
- Cutoff frequency is

$$\omega_c = \frac{1}{RC}$$

31

## The *RL* High-Pass Filter

- *RL* circuit is a high-pass filter if output is taken across the inductor
- Transfer function is

$$TF = \frac{Z_L}{R + Z_L} = \frac{j\omega L}{R + j\omega L}$$

32



## The *RL* High-Pass Filter

- Cutoff frequency is

$$\omega_c = \frac{R}{L}$$

33

## The Band-Pass Filter

- Permits frequencies within a certain range to pass from input to output
- All frequencies outside this range will be attenuated

34

## The Band-Pass Filter

- One way to build a band-pass filter is to cascade a low-pass filter with a high-pass filter
- A band-pass filter can also be constructed from an *RLC* circuit

35

## The Band-Reject Filter

- Passes all frequencies except for a narrow band
- Can be constructed from an *RLC* series circuit
  - Taking output across the inductor and capacitor

36

## The Band-Reject Filter

- Can also be constructed from a circuit containing a  $RC$  parallel combination in series with a resistor
  - Taking output across the resistor

37

This document was created with Win2PDF available at <http://www.daneprairie.com>.  
The unregistered version of Win2PDF is for evaluation or non-commercial use only.