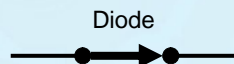


## Chapter 27

### Diode Theory and Application

## Diode Models

- Ideal model is a switch
- Forward-biased ideal model
  - Short Circuit
  - $V_D = 0$
  - $R_D = 0$



## Diode Models


- Reverse-biased ideal model
  - Open Circuit
  - $V_D = \text{Supply Voltage}$
  - $R_D = \infty$



3
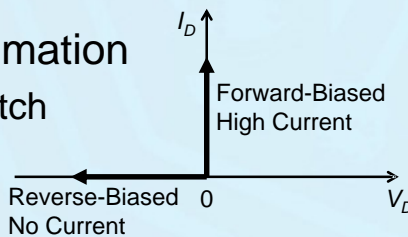
## Diode Models


- Characteristic curve shows Current vs Voltage
- 1<sup>st</sup> approximation
  - Ideal Switch



4

## Diode Models


- Circuit model – Ideal Diode

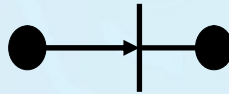

5
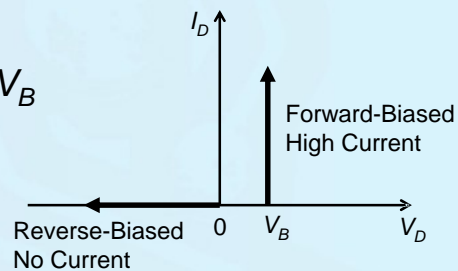
## Diode Models


- 2<sup>nd</sup> approximation
  - Ideal Switch
  - Barrier potential,  $V_B$ 
    - Si  $\approx$  0.7 volts
    - Ge  $\approx$  0.3 volts



6
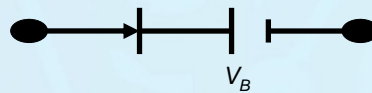
## Diode Models


- Circuit Model
  - Ideal Diode
  - $V_B$



7
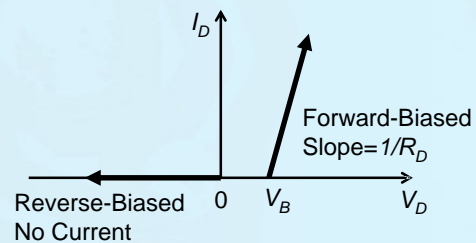
## Diode Models


- 3<sup>rd</sup> approximation
  - Barrier potential,  
 $V_B$
  - $V_B$
  - Internal  
Resistance



8
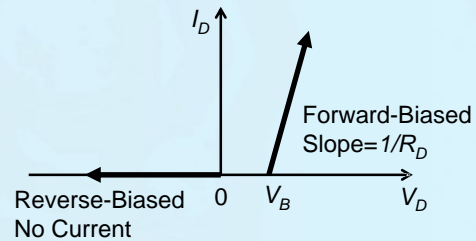
## Diode Models

- Circuit Model
  - Ideal Diode
  - $V_B$
  - $R_D$



9

## Diode Characteristic Curve

- Regions of a real diode curve
- Forward Region
  - Conduction
  - Knee
  - High resistance

10


## Diode Characteristic Curve

- Reverse Region
  - High resistance blocking
  - Diode breakdown

11

## Diode Characteristic Curve

- Real Diode I/V  
curve

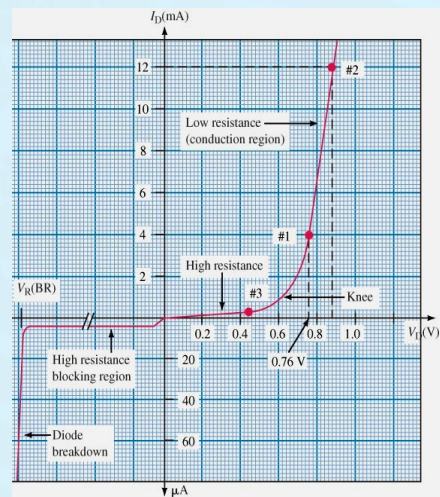

12

## Diode Characteristic Curve

- Forward region
  - Conduction region
  - Dynamic resistance is  $\frac{\Delta V}{\Delta I}$

13

## Diode Characteristic Curve

- Reverse region
  - Small reverse voltages yield very small currents (uA)
  - Reverse breakdown voltage,  $V_{R(BR)}$
  - Peak Inverse Voltage (PIV), Peak Reverse Voltage (PRV) or  $V_{R(max)}$

14

## Diode Data Sheets

- Manufacturer specifications (specs)
- Describe product electrical characteristics
  - Recommended operating conditions
  - Maximum ratings (PIV, power =  $I^2R$ )
  - ac
  - dc

15

## Diode Data Sheets

- Part number with 1N prefix

16



## Diode Data Sheets

- Two sections
  - Maximum ratings: limits that must not be exceeded
  - Electrical Characteristics: typical and max values during operation
    - Forward voltage drop
    - Reverse voltage

17

## Diode Data Sheets

- Always need a safety margin
  - At least 20% more  $I$  or  $V$  than your circuit
  - e.g., if PIV expected in your circuit is 150 V, choose diode with PIV of >180 V

18

# Diode Data Sheets

- Many manufacturers
- Many diode types (e.g. bridge, high-speed switching, small signal, Varactor, Zener)
- Data sheets on Internet

19

# Diode Data Sheets

- Example

**1N4001, 1N4002, 1N4003,  
1N4004, 1N4005, 1N4006,  
1N4007**

1N4004 and 1N4007 are Preferred Devices

**Axial Lead Standard Recovery Rectifiers**

This data sheet provides information on administrative size, axial lead mounted rectifiers for general-purpose low-power applications.

**Mechanical Characteristics**

- Case: Epoxy Moulded
- Weight: 0.4 gram (approximately)
- Finish: All Exposed Surfaces Corrosion Resistant and Terminal Leads are Readily Solderable
- Lead and Mounting Surface Temperature for Soldering Purposes: 230°C Max. for 10 Seconds, 110° from case
- Shipped in plastic bags, 1000 per bag.
- Available: Top and Reel, 5000 per reel, by adding a "RL" suffix to the part number
- Available in Fan Fold Packaging, 3000 per box, by adding a "FF" suffix to the part number
- Polarity: Cathode Indicated by Polarity Band
- Marking: 1N4001, 1N4002, 1N4003, 1N4004, 1N4005, 1N4006, 1N4007

**MAXIMUM RATINGS**

Rating	Symbol	1N4001	1N4002	1N4003	1N4004	1N4005	1N4006	1N4007	Unit
Peak Repetitive Reverse Voltage Working Peak Reverse Voltage DC Blocking Voltage	V <sub>RRM</sub> V <sub>WRM</sub> V <sub>WM</sub>	50	100	200	400	600	800	1000	Volts
Non-Repeatable Peak Reverse Voltage (Half-wave, single pulse, 50 Hz)	V <sub>RRM</sub>	60	120	240	480	720	1000	1200	Volts
RRM Reverse Voltage	V <sub>RRM</sub>	35	70	140	280	420	560	700	Volts
Average Rectified Forward Current (single phase, resistive load, 50 Hz, T <sub>c</sub> = 75°C)	I <sub>o</sub>	1.0							
Non-Repeatable Peak Surge Current (single pulse, resistive load, 1000 Hz)	I <sub>FSM</sub>	30 (for 1 cycle)							
Operating and Storage Junction Temperature Range	T <sub>j</sub> T <sub>stg</sub>	-65 to +175							

Reference JEDEC Registered Data


**ORDERING INFORMATION**

See standard ordering and shipping information on page 2 of this data sheet

Preferred devices are recommended choices for future use and most current values


© Semiconductor Components Industries, LLC 2003  
January, 2003 - Rev. 6

Publication Order Number:  
1N4001/D




ON Semiconductor®  
http://onsemi.com

**LEAD MOUNTED RECTIFIERS  
50-1000 VOLTS  
DIFFUSED JUNCTION**



CASE 20-16  
AXIAL LEAD  
PLASTIC

**MARKING DIAGRAM**



AL = Assembly Location  
N4004 = Device Number  
= D, S, A, R, W or F  
YY = Year  
WW = Week

20

## Diode Data Sheets

- Reverse Voltage
  - dc
  - Repetitive sinusoidal
    - Full-wave
    - Half-wave
- Forward Current
  - Average
  - Surge

21

## Diode Data Sheets

- Maximum Instantaneous Forward Voltage Drop,  $V_F$
- Maximum Full-Cycle Average Voltage Drop,  $V_{F(AV)}$
- Temperature Derating
  - $I^2R$  in diode generates heat
  - Derating curve

22

## Diode Data Sheets

- Parameter Shifts
- Temperature increase Forward Region
  - Generates more  $e^-$  - *hole* pairs
  - Changes Barrier Potential,  $V_B$
  - $V_B$  decreases  $\approx 2.5mV$  per  $1^\circ$  C increase

23

## Diode Data Sheets

- Temperature increase Reverse Region
  - More minority carriers
  - Reverse current,  $I_S \approx \text{doubles per } 10^\circ$  C increase

24

## Diode Data Sheets

- Reverse Recovery Time
  - Switching time
  - From On to Off state
  - $t_{rr}$
  - Nanoseconds for switching diodes
  - Microseconds for rectifier diodes

25

## The Zener Diode

- Special purpose diode
- Operates in reverse-bias region
- Breakover voltage called Zener Voltage,  
 $V_Z$

26


## The Zener Diode

- $V_Z$  is close to constant
  - From knee current,  $I_{ZK}$
  - To maximum rated current,  $I_{ZM}$
- $V_Z$  is set by amount of doping used

27

## The Zener Diode

- Symbol:

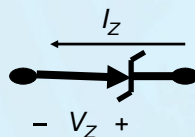


- Available with  $\sim 2.4 V < V_Z < \sim 200 V$
- Forward direction – like a standard diode
- Reverse direction – sharp breakdown region

28

## The Zener Diode

- Characteristic curve

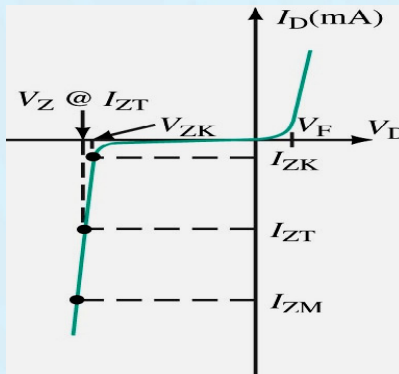

29

## The Zener Diode

- Zener Specification Sheet
  - Zener test current,  $I_{ZT}$
  - Nominal Zener Voltage,  $V_Z$  (measured at  $I_{ZT}$ )
  - Maximum Zener current,  $I_{ZM}$
  - Knee current,  $I_{ZK}$

30

## The Zener Diode

- Zener impedance,  $Z_Z @ I_{ZT}$ 
  - Dynamic  $Z = \frac{\Delta V}{\Delta I}$
  - 2 – 45  $\Omega$
  - Almost constant in operating region

31

## The Zener Diode

- Power Rating
  - Maximum dc power dissipation,  $P_{Dmax}$
  - $P_{Dmax} = V_Z * I_{ZM}$  watts
  - $.25 W < P_{Dmax} < 50 W$
- Power Derating
  - Factor such as  $6.67 mW \text{ per } ^\circ C$
  - Graph


32




## The Zener Diode

- Modeling

- Ideal

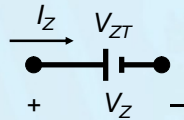

- 2<sup>nd</sup> approximation

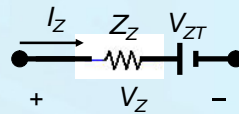

- Open circuit if  $I_Z < I_{ZT}$

33

## The Zener Diode

- Applications

- Use ideal model
- Commercial Tolerance,  $\pm 5\%$  to  $10\%$  for  $V_Z$


- Design

- Determine limits imposed by  $I_{ZK}$  and  $I_{ZM}$
- Design circuit well within these limits

34

## The Zener Diode

- Voltage regulator

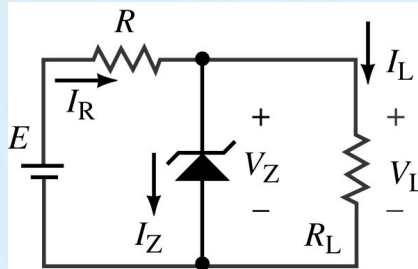

35

## The Zener Diode

- Current divider between Zener and Load
- $I_{ZK} < I_Z < I_{ZM}$
- Input regulation
  - Limits input voltage:  $E_{min} < E_{in} < E_{max}$
- Load regulation
  - Limits load resistance:  $R_{Lmin} < R_L < R_{Lmax}$

36

## The Zener Diode

- Clippers
  - Limit amplitude of input ac waveform
    - Single sided
    - Dual sided
- Clampers
  - If  $V_{in} \geq V_Z$  then  $V_{out} = V_Z$

37


## The Zener Diode

- Transient suppression
  - Greater power capability
  - Use Back-to-Back Zeners


38
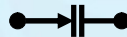
## The Varactor Diode

- Also called varicap, epicap, or tuning diode
- Voltage variable capacitor
- Symbols:



or

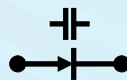

39

## The Varactor Diode

- Nonlinear  $V$  vs  $C$  curve
- Increase reverse Voltage decrease  $C$ 
  - Reverse biased
  - Increase voltage decreases diode junction
  - Capacitance inversely proportional to distance between plates

40

## The Varactor Diode

- Normal diode operation when forward biased

41

## The Varactor Diode

- Specs
  - Nominal capacitance,  $C_T$  (given at a specific voltage)
  - Reverse breakdown voltage
  - Temperature coefficient

42

## The Varactor Diode

- Specs
  - Figure of Merit,  $Q$
  - Capacitance ratio (tuning ratio)
  - $C_R$  e.g. if  $5 \text{ pF} < C < 30 \text{ pF}$ ,  $C_R = 6$  ( $30 \text{ pF}/5 \text{ pF} = 6$ )

43

## Half-Wave and Full-Wave Rectifier Circuits

- Half-Wave rectification
  - Sine Wave input with no dc component
  - Single diode

44


## Half-Wave and Full-Wave Rectifier Circuits

- Half-Wave output
  - Upper  $\frac{1}{2}$  of sine wave
    - Diode in forward direction
  - Lower  $\frac{1}{2}$  of sine wave
    - Diode in reverse direction
  - dc value =  $.318 V_m$  (not counting  $V_B$ )
- $PIV \approx 2 * E_m$

45

## Half-Wave and Full-Wave Rectifier Circuits

- Full-Wave Bridge

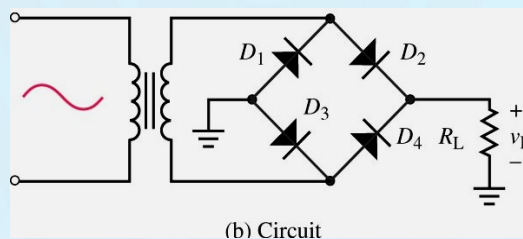

46

## Half-Wave and Full-Wave Rectifier Circuits

- Full-Wave rectification
  - Sine Wave input with no dc component
  - Center-tap transformer with two diodes
  - Full-Wave Bridge with four diodes

47

## Half-Wave and Full-Wave Rectifier Circuits

- Full-Wave output
  - Upper  $\frac{1}{2}$  of sine wave and inverted lower half of sine wave
  - dc value =  $.637 V_m$  (not counting  $V_B$ )
- $PIV \approx E_m$
- Bridge rectifier package (4 matched diodes)

48



## Power Supply Filtering

- Parallel RC circuit with half-wave rectified input
  - Capacitor charges during first  $\frac{1}{4}$  cycle
  - Capacitor holds during rest of cycle

49

## Power Supply Filtering

- Output
  - Less ripple
  - Closer to steady dc
- Larger capacitor yields less ripple

50

## Power Supply Filtering

- Parallel RC circuit with full-wave input

$$V_{dc} = \frac{V_m}{1 + \frac{T}{2R_L C}}$$

- $T$  = Period of Sinusoid
- $R_L$  = Load resistance
- $C$  = Filter capacitance

51

## Power Supply Filtering

- Ripple
  - Expressed in rms volts
  - Ripple factor

$$r = \frac{\text{rms ripple voltage}}{\text{dc voltage}}$$

$$r = \frac{T}{2\sqrt{3}R_L C}$$

52

## Power Supply Filtering

- Diode Forward Current
  - Repetitive surge currents
  - Maximum listed on many rectifier data sheets
- Unregulated power supplies
  - Output dc voltage varies with input voltage
- Regulated power supplies
  - Simplest regulator is a Zener diode

53

This document was created with Win2PDF available at <http://www.daneprairie.com>.  
The unregistered version of Win2PDF is for evaluation or non-commercial use only.