

Chapter 28


Basic Transistor Theory

Transistor Construction

- Bipolar Junction Transistor (BJT)
 - 3 layers of doped semiconductor
 - 2 p - n junctions
 - Layers are: Emitter, Base, and Collector
 - Can be *NPN* or *PNP*
 - Emitter and Collector both P or both N type

Transistor Construction


- Structure and Electronic Symbol

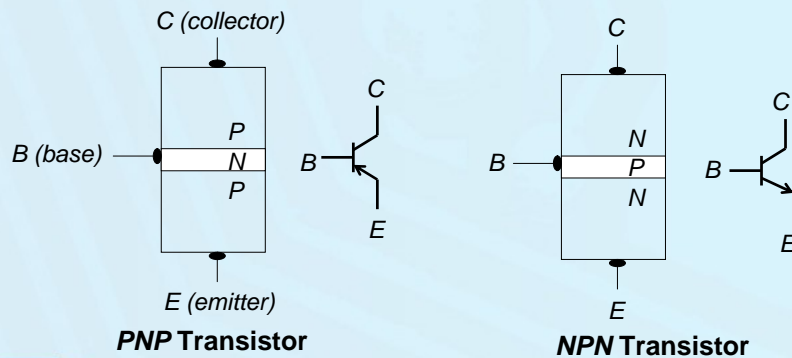

3

Transistor Operation

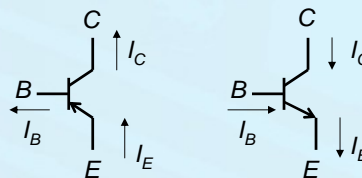- Amplifier
 - B - E junction forward biased
 - $V_{BE} \approx 0.7$ V for Si
 - C - B junction reverse biased
 - KCL: $I_E = I_C + I_B$



4

Transistor Operation

- Transistor Bias Circuits

5

Transistor Operation

- dc Beta (β_{dc})
 - $I_E = I_C + I_B$
 - $I_B \ll I_E$
 - $I_C \approx I_E$
 - $40 < \beta_{dc} < 400$

$$\beta_{dc} = \frac{\Delta I_C}{\Delta I_B}$$

6

Transistor Operation

- 2N3904 NPN transistor spec
 - $100 < \beta_{dc} < 300$
- β_{dc} dependent on
 - Operating point
 - Temperature

7

Transistor Operation

- dc Alpha (α_{dc})
 - $\alpha < 1$
- α - β Relationship

$$\alpha_{dc} = \frac{I_C}{I_E}$$

$$\alpha = \frac{\beta}{\beta + 1}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

8

Transistor Specifications

- Maximum voltage between *C* & *E* with Base open, V_{CEO}
- Maximum reverse voltage between *C* & *B* with Emitter open, V_{CBO}
- Maximum reverse voltage between *E* & *B* with Collector open, V_{EBO}

9

Transistor Specifications

- Maximum collector current, I_C
- Maximum power dissipated, P_D

$$P_D = I_C * V_{CE}$$

10

Transistor Specifications

- Minimum $C-E$ voltage for breakdown,
 $V_{(BR)CEO}$
- Carefully examine absolute max ratings
- dc current gain
 - variable
 - $\beta = h_{FE}$ in specs

11

Collector Characteristic Curves

- Saturation region
 - I_C increases rapidly for small values of V_{CE}
 - BJT behaves like closed switch

12

Collector Characteristic Curves

- Active region
 - *BJT* acts as a signal amplifier
 - B-E junction is forward biased & C-B junction is reverse biased

13

Collector Characteristic Curves

- β_{dc} not constant
- β_{dc} dependent on dc operating point
- Quiescent point = operating point
- Active region limited by
 - Maximum forward current, $I_{C(MAX)}$
 - Maximum power dissipation, P_D

14


dc Load Line

- Drawn on characteristic curves
- Component values in a bias circuit
 - Determine quiescent point, Q
 - Q is between saturation and cutoff
- Best Q for a linear amplifier
 - Midway between saturation and cutoff

15

DC Load Line

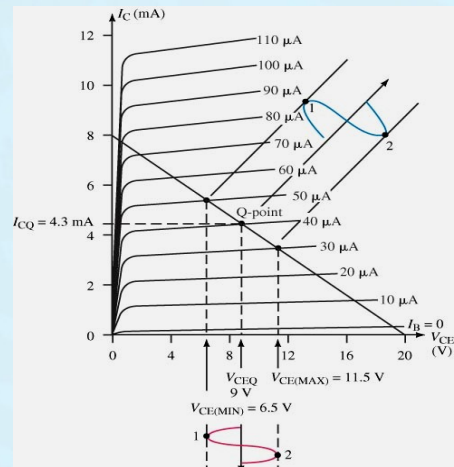
- Characteristic curve with Load Line
- Q-point, and current gain



16

Transistor Biasing

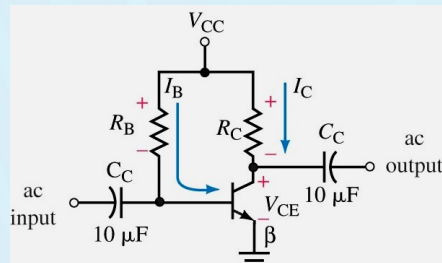- Fixed-Bias Circuit
 - Single power supply
 - Coupling capacitors



17

Transistor Biasing

- Equations for Fixed-Bias circuit

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_C = \beta I_B$$

$$V_{CE} = V_{CC} - I_C R_C$$

18

Transistor Biasing

- Fixed Bias Circuit highly dependent on β_{dc}
- Emitter-Stabilized Bias Circuit
 - Add emitter resistor
 - Greatly reduces effect of change of β
 - Equations

19

Transistor Biasing

$$V_{CC} = R_B I_B + V_{BE} + R_E I_E$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + R_E (\beta + 1)}$$

$$V_{CE} = V_{CC} - (R_C + R_E) I_C$$

20

Transistor Biasing

- Universal-Bias circuit
 - Sometimes referred to as voltage divider bias
 - Most stable
 - Equations:

$$I_B = \frac{V_{BB} - V_{BE}}{R_{BB} + R_E(\beta + 1)}$$

$$I_C = \beta I_B$$

$$V_{CE} = V_{CC} - (R_C + R_E)I_C$$

21

Transistor Biasing

- Universal-Bias circuit
 - Need $I_B \ll I_C$
 - Make $R_2 \leq \frac{1}{10} \beta R_E$
 - Simple Voltage divider between V_{CC} , Base, and ground

22

Transistor Biasing

$$I_E = \frac{V_E}{R_E} \equiv I_C$$

$$V_{CE} \cong V_{CC} - (R_C + R_E)I_C$$

23

Transistor Biasing

- Common Collector Circuit
 - Less common than CE circuit
 - Collector connected to ground
 - Similar analysis
 - Voltage gain < 1

24

Transistor Biasing

- Common Base Circuit
 - Least common
 - High frequency applications
 - Current gain < 1

25

The Transistor Switch

- *BJT* less used as amplifiers
 - IC amplifiers available
- Switching is a principal application of *BJT*'s
 - Current amplifier turn on LED's
 - Power amplifier to turn on small motors

26


The Transistor Switch

- A buffer has high input impedance and low output impedance

27

The Transistor Switch

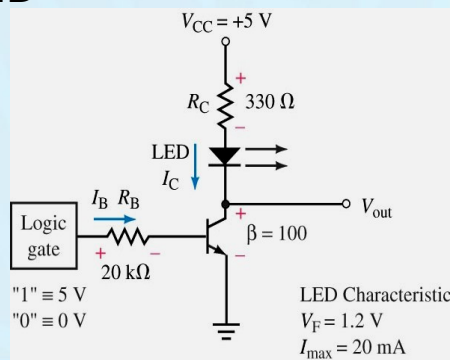- *BJT* as a buffer between digital input and LED



28

Testing a Transistor with a Multimeter

- Ohmmeter
 - dc voltage generates small current
- Test *CB* and *BE* junctions
 - Forward bias = small resistance
 - Reverse bias = large resistance

29

Testing a Transistor with a Multimeter

- Fail test
 - *BJT* will not operate correctly
- Pass test
 - Not a guarantee that *BJT* is good

30

Testing a Transistor with a Multimeter

- Six measurements required
- An O.C. between two terminals (both directions) means other terminal is *B*
- Only two low Ω readings if *BJT* is good

31


Testing a Transistor with a Multimeter

- Lower of the two low Ω readings is *C*
- Other one of low Ω readings is *E*

32

Junction Field Effect Transistor Construction and Operation

- Construction and symbols

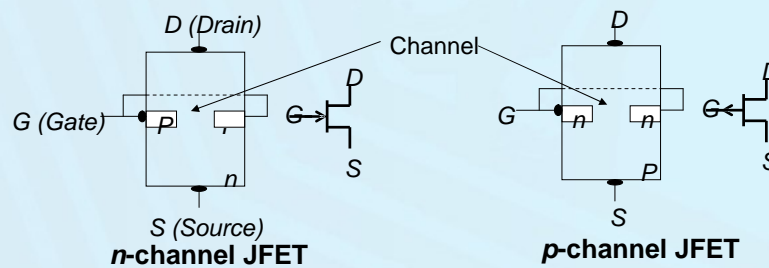

33

Junction Field Effect Transistor Construction and Operation

- **BJT**
 - Current amplification
 - *BE* junction forward biased
 - Input impedance (Common Emitter) low

34


Junction Field Effect Transistor Construction and Operation

- *JFET*
 - Voltage amplification
 - GS junction reverse biased
 - Input impedance very high

35

Junction Field Effect Transistor Construction and Operation

- Basic operation of an n-channel *JFET*

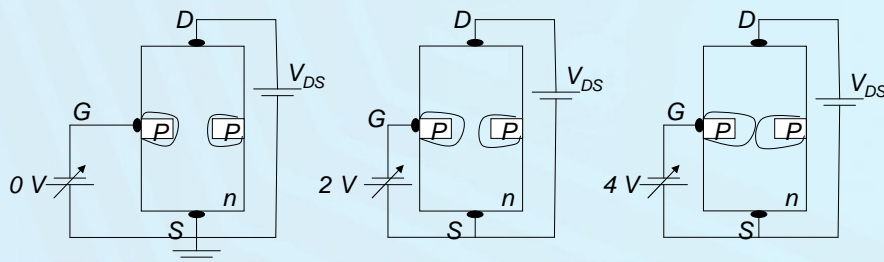

36

Junction Field Effect Transistor Construction and Operation

- $I_S = I_D$
- Decrease V_{GS} from 0 to -4
 - Decrease current flowing
 - Pinchoff voltage reached

37

Junction Field Effect Transistor Construction and Operation


- I_D vs V_{GS} (Transconductance curve)
described by Shockley's equation

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(OFF)}}\right)^2$$

38

Junction Field Effect Transistor Construction and Operation


- Self-bias circuit

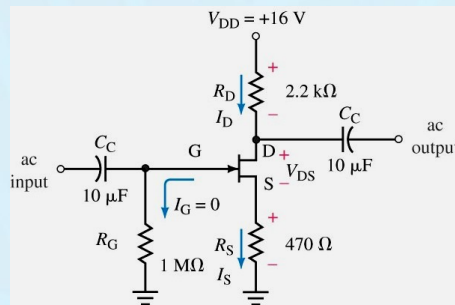

39

Junction Field Effect Transistor Construction and Operation

- Load line

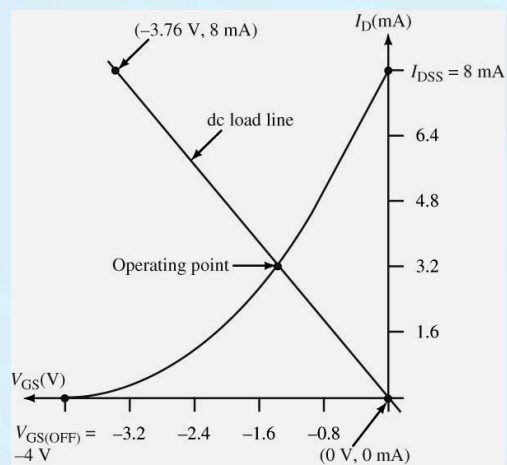

40

Junction Field Effect Transistor Construction and Operation

- Another biasing circuit: similar to universal bias circuit for *BJT*'s
 - Voltage divider
 - Resistor from from V_{DD} to the Gate
 - Resistor from Gate to ground

41

Junction Field Effect Transistor Construction and Operation

- Basic JFET circuit analysis: use
 - KVL and KCL
 - $I_G = 0$
 - $I_D = I_S$

42


MOSFETs

- Metal Oxide Semiconductor Field Effect Transistors
 - Small
 - Low power
 - Higher current capability, I_{DS}
 - Do not have to reverse bias the gate
 - Depletion or Enhancement types

43

MOSFETs

- Construction and symbols

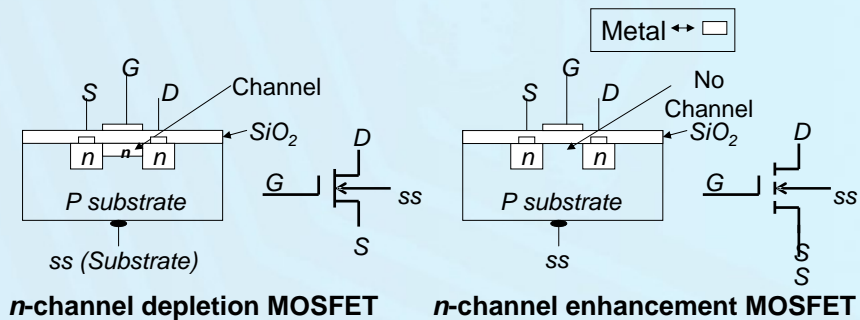

44

MOSFETs

- Depletion MOSFETs
 - Have a channel
 - Shockley's equation still valid
 - Depletion mode
 - Enhancement mode

45

MOSFETs

- Enhancement MOSFETs
 - No channel
 - Positive V_{GS} required prior to current
 - Enhancement mode only
 - No depletion mode
 - Shockley's equation no longer valid


46

MOSFETs

- Biasing
 - Voltage Divider
 - Drain-feedback circuit shown here

47

MOSFETs

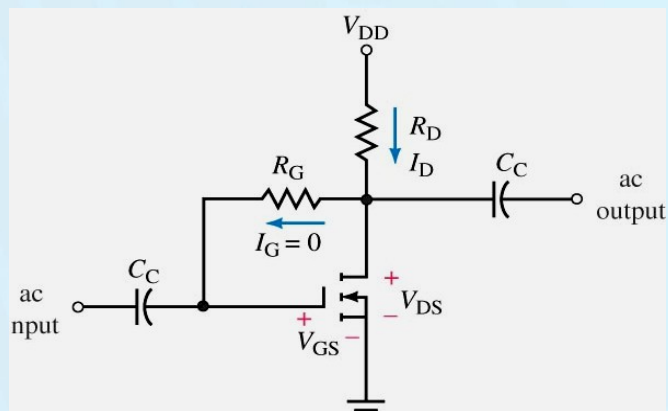

48

MOSFETs

- Handling precautions
 - Subject to damage by electrostatic charges
 - Packaged in static resistant bags
 - Handle at static safe workstation
 - Use grounded wrist strap

49

Troubleshooting a Transistor Circuit

- Ensure correct biasing
- Measure V_{BE}
- Determine V_{CEQ} and I_{CQ}
- Determine I_{BQ}
- Calculate β

50

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.