

Chapter 29

Transistor Amplifiers

Use of Capacitors in Amplifier Circuits

- Capacitor review
 - Store electrical charge
 - Impedance:

$$X_C = \frac{1}{2\pi fC} [\Omega]$$

- ∞ impedance at dc
- Impedance decreases at higher frequencies

Use of Capacitors in Amplifier Circuits


- Capacitors
 - Block dc between stages
 - Can be designed to readily pass ac

3

Use of Capacitors in Amplifier Circuits

- Coupling capacitors
 - At “high” frequencies
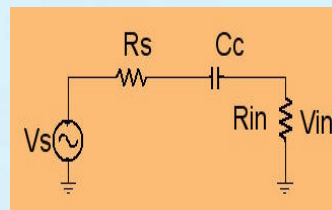
$$V_{in} = \left(\frac{R_{in}}{R_{in} + R_S} \right) V_S$$



- For $R = R_{in} + R_S$, select capacitor so $X_C \leq 0.1 R$
- Referred to as “stiff coupling”


4

Use of Capacitors in Amplifier Circuits

- Bypass capacitors
 - Emitter resistor, R_e used for biasing
 - C_e is a short circuit at high frequencies
 - R_e has no effect on amplification when C_e is present
 - Select $X_C \leq 0.1R$

5

Use of Capacitors in Amplifier Circuits

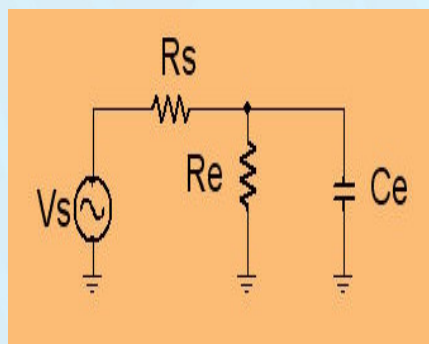

6

Use of Capacitors in Amplifier Circuits

- Capacitors
 - Couple desired ac signals between stages
 - Bypass unwanted ac signals to ground

7

Use of Capacitors in Amplifier Circuits

- Circuit analysis
 - If $X_C \leq 0.1R$
 - Replace C with O.C. to determine dc I and V
 - Replace C with S.C. to determine ac i and v

8

BJT Small-Signal Models

- T-Equivalent Model

- $i_e = i_b + i_c$

- $i_e = (\beta + 1)i_b$


- $r_e = \frac{26\text{ mV}}{I_{EQ}}$ at 25°C

- Simple

- Good enough for most applications

9

BJT Small-Signal Models

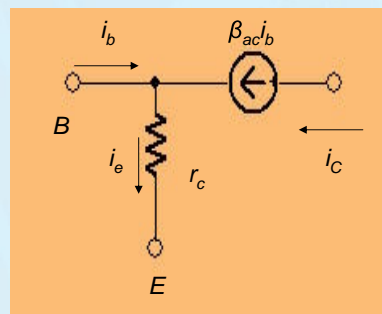

10


BJT Small-Signal Models

- Models
 - T -equivalent model simpler
 - h -parameter model more accurate
 - h_{fe} (h -model) = β_{ac} (T -model) [$\beta_{ac} \approx \beta_{dc}$]
 - h -parameters dependent on Q-point
 - BJT is a current amplifier (current source in both models)

11

BJT Small-Signal Models

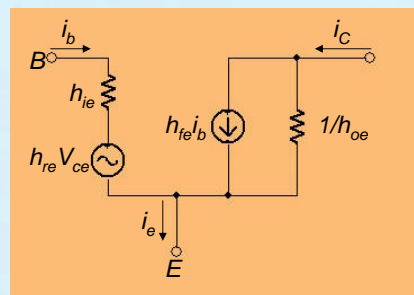- h -parameter model
 - More complex
 - Better for ac operation
 - Common Emitter model
 - h_{ie} = input impedance (Ω)
 - h_{re} = reverse voltage transfer ratio (unitless)
 - h_{fe} = forward current transfer ratio (unitless)
 - h_{oe} = output admittance (S)



12

Calculating A_v , z_{in} , z_{out} , and A_i of a Transistor Amplifier

- Voltage Gain, A_v
 - Output voltage divided by input voltage
- Input Impedance, z_{in}
 - Input voltage divided by input current

$$A_v = \frac{v_{out}}{v_{in}}$$

$$z_{in} = \frac{v_{in}}{i_{in}}$$

13

Calculating A_v , z_{in} , z_{out} , and A_i of a Transistor Amplifier

- Output Impedance, z_{out}

$$z_{out} = \frac{v_{out(OC)}}{i_{out(SC)}}$$

- Current Gain, A_i

$$A_i = \frac{i_{out}}{i_{in}}$$

- Power Gain, A_p

$$A_p = \frac{P_{out}}{P_{in}}$$

14


Common-Emitter Amplifier

- General BJT circuit analysis
 - Find operating point
 - Determine ac parameters (T - or h - models)
 - Remove dc V sources & replace with S.C.'s
 - Replace coupling & bypass C 's with S.C.'s
 - Replace BJT with circuit model
 - Solve resulting circuit

15

Common-Emitter Amplifier

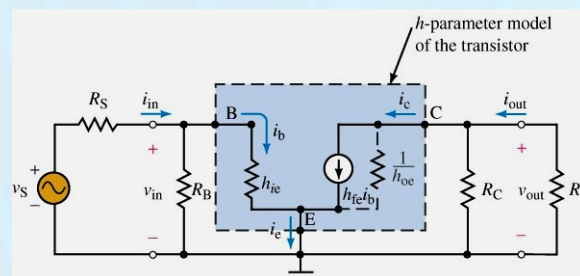- ac equivalent of fixed-bias CE amplifier using h -parameter model



16

Common-Emitter Amplifier

- Equations for h -parameter model for fixed-bias CE amplifier
 - Circuit voltage gain a function of
 - Model forward current transfer ratio, h_{fe}
 - Model input impedance, h_{ie}
 - Circuit collector resistance, R_C
 - Circuit load resistance, R_L

$$A_v = -\frac{h_{fe}(R_C \parallel R_L)}{h_{ie}}$$

17

Common-Emitter Amplifier

- Circuit current gain a function of
 - Same parameters, plus
 - Fixed bias resistance, R_B

$$A_i = \frac{h_{fe} R_B R_C}{(R_C + R_L)(R_B + h_{ie})}$$

18

Common-Emitter Amplifier

- Equations for h -parameter model for fixed-bias CE amplifier
 - Circuit input impedance a function of
 - Model forward current transfer ratio, h_{fe}
 - Model input impedance, h_{ie}

$$z_{in} = R_B \parallel h_{ie}$$

19

Common-Emitter Amplifier

- Circuit output impedance a function of
 - Collector resistance (model output admittance), h_{oe} very low $z_{out} = R_C$

20


ac Load Line

- Q-point is on dc load line
- ac load line determines maximum undistorted output
- Can calculate maximum power
- Q-point also on ac load line
- ac load line has different slope

21

ac Load Line


- CE amplifier circuit

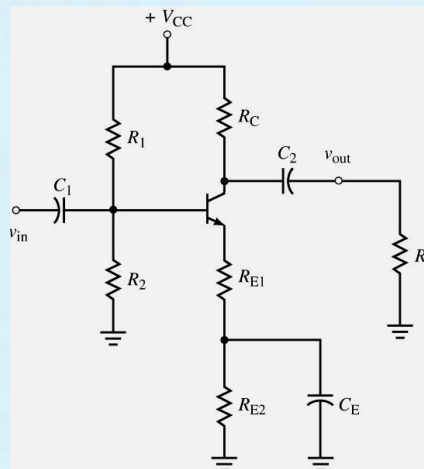

22

ac Load Line

- dc and ac load lines

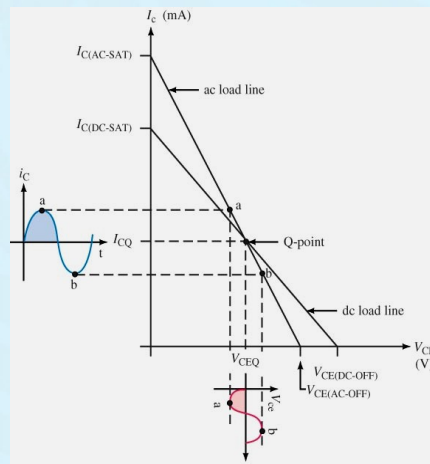

23

ac Load Line

- Equations of ac load line
- Consider
 - CE amplifier circuit
 - dc load line

$$v_{CE} = -i_c (r_C + r_E)$$

$$I_C = \frac{V_{CE}}{r_C + r_E}$$

$$i_c = I_{CQ} + i_c$$

$$v_{CE} = V_{CEQ} + v_{ce}$$

24

Common-Collector Amplifier

- Important characteristics
 - High input impedance
 - Low output impedance
 - v_{out} in-phase with v_{in}
 - $V_{out} \approx V_{in}$

25


Common-Collector Amplifier

- Important characteristics
 - Large current gain
 - Input voltage measured at base
 - Output voltage measured at emitter

26

Common-Collector Amplifier

- Common-Collector circuit

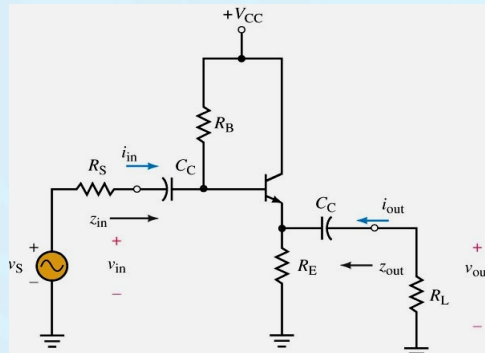

27

Common-Collector Amplifier

- Circuit gains and impedances

$$- A_v \approx 1$$

$$- z_{in} = R_B \parallel z_{in(Q)}$$


$$- A_i = -\frac{A_v z_{in}}{R_L} \quad \text{close to } h_{fe}$$

$$- z_{out(Q)} = \frac{R_S \parallel R_B}{h_{fe} + 1} = r_e \quad \text{very small}$$

28

FET Small-Signal Model

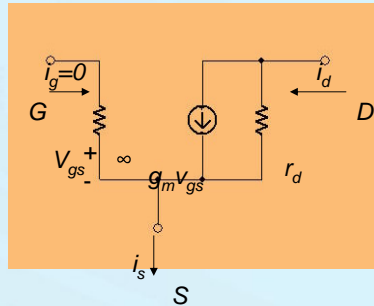
- Voltage controlled amplifier
- Small-signal model same for JFETs & MOSFETs
- High input impedance
- $i_s = i_d$



29

FET Small-Signal Model

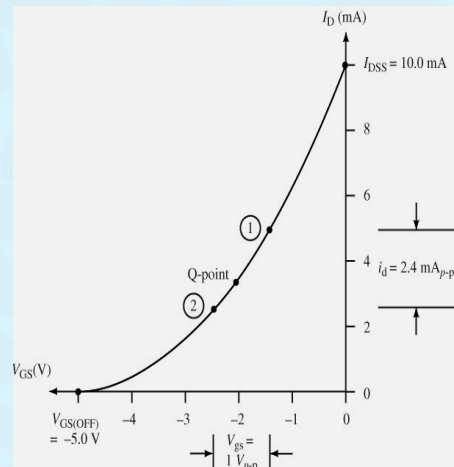- g_m is transconductance
- g_m is slope of transfer curve



30

FET Small-Signal Model

- Equations

- Definition $g_m = \frac{\Delta I_D}{\Delta V_{GS}}$

- Maximum $g_{m0} = \left| \frac{2I_{DSS}}{V_{GS(OFF)}} \right|$

- Measured $g_m = g_{m0} \left(1 - \frac{V_{GSQ}}{V_{GS(OFF)}} \right)$

31

Common-Source Amplifier


- Analysis

- Similar to BJT using h -parameter model
 - First determine bias
 - Find dc operating point (Q-point)
 - Determine g_m

32

Common-Source Amplifier

- A common-source circuit

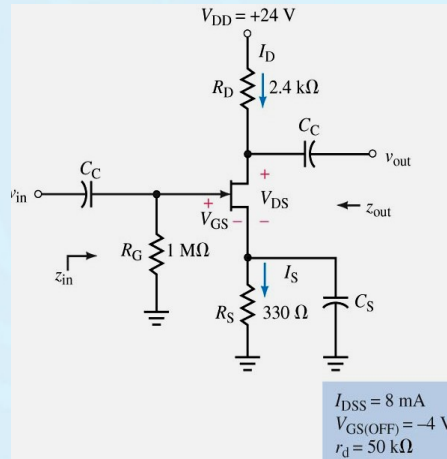

33

Common-Source Amplifier

- Equations
 - No current input
 - Voltage gain dependent on g_m and R_D
 - Input impedance is $R_G \parallel \infty$
 - Output impedance approximately drain resistance

$$A_V \approx -g_m R_D$$

$$z_{in} = R_G$$

$$z_{out} \approx R_D$$

34

Common-Source Amplifier

- D-MOSFETs
 - Analysis same as JFETs
 - Except operation in enhancement region

35

Common-Source Amplifier

- E-MOSFETs
 - Find I_{DSQ} , V_{GSQ} , and V_{DSQ} at Q-point
 - Solve for g_m of amplifier
 - Sketch ac equivalent circuit
 - Determine A_v , z_{in} , and z_{out} of amplifier

36

Common-Drain (Source Follower) Amplifier

- $A_v < 1$
- v_{out} in phase with v_{in}
- Input impedance very high
- Output impedance low
- Main application: Buffer

37

Troubleshooting a Transistor Amplifier Circuit

- Incorrect placement of electrolytic capacitors
 - Noisy output signal
 - Capacitor as an antenna
 - Generally 60 Hz added

38

Troubleshooting a Transistor Amplifier Circuit

- Correct placement
 - Check proper polarity
 - Replace faulty capacitors

39

Troubleshooting a Transistor Amplifier Circuit

- Faulty or incorrectly placed capacitor
 - Measured A_v different from theoretical A_v
 - Faulty capacitor behaves like an open circuit
 - Faulty capacitor can develop internal short

40

Troubleshooting a Transistor Amplifier Circuit

- Troubleshooting steps
 - Remove ac signal sources from circuit
 - Calculate theoretical Q-point
 - Measure to determine actual Q-point
 - Verify capacitors are correctly placed
 - Ensure connections, especially ground wires, as short as possible

41

Troubleshooting a Transistor Amplifier Circuit

- Distorted output signal usually the result of too large an input signal

42

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.